

Name: \_\_\_\_\_

Partners Approval: \_\_\_\_\_

Name \_\_\_\_\_

Partners Approval: \_\_\_\_\_

## EE114 Power Engineering I

### Assignment 01

#### Instructions:

1. This is an individual assignment.
2. Show all of your work.
3. **Reading:** Chapter 09, 10 and 11 from Electric Circuits by Nilsson and Reidal
4. **Due Date:**

- **Question 1:** A sinusoidal voltage is given by the expression

$$v = 100\cos(240\pi t + 45^\circ)mV \quad (1)$$

Find

1. frequency ( $f$ ) in hertz.
  2. Time constant ( $T$ ) in millisecond.
  3.  $V_m$ .
  4.  $v(0)$ .
  5.  $\phi$  in degree and radians.
  6. The smallest positive value of  $t$  at which  $v = 0$ .
  7. The smallest positive value of  $t$  at which  $dv/dt = 0$
- **Question 2: (30pts)** In a single graph  $v = 60\cos(\omega t + \phi)$  verse  $\omega t$  for  $\phi = -60^\circ, -30^\circ, 0^\circ, 30^\circ$  and  $60^\circ$ .
    1. State whether the voltage function is shifting to the right or left as  $\phi$  become more positive.
    2. What is the direction of shift if  $\phi$  changes from 0 to  $-30^\circ$ .
  - **Question 3:** Consider the sinusoidal voltage

$$v(t) = 170\cos(120\pi t - 60^\circ) \quad (2)$$

1. What is the maximum amplitude of the voltage ?
2. What is the frequency in hertz ?

3. What is the frequency in radians per second ?
  4. What is the phase angle in radians ?
  5. What is the phase angle in degrees ?
  6. what is the period in milliseconds ?
  7. what is the first time after  $t = 0$  that  $v = 170$  V ?
  8. The sinusoidal function is shifted 125/18 ms to the right along the axis. What is the expression for  $v(t)$  ?
  9. What is the minimum number of milliseconds that the function must be shifted to the right if the expression for  $v(t)$  is  $170\sin(120\pi t)$  V ?
  10. What is the minimum number of milliseconds that the function must be shifted to the left if the expression for  $v(t)$  is  $170\cos(120\pi t)$  V ?
- **Question 4:** Use the concept of the phasor to combine the following sinusoidal functions into a single trigonometric expression:
    1.  $y = 100\cos(300t + 45^\circ) + 500\cos(300t - 60^\circ)$
    2.  $y = 250\cos(377t + 30^\circ) - 150\sin(377t + 140^\circ)$
    3.  $y = 60\cos(100t + 60^\circ) - 120\sin(100t - 125^\circ) + 100\cos(100t + 90^\circ)$
    4.  $y = 100\cos(\omega t + 40^\circ) + 100\sin(\omega t + 160^\circ) + 100\cos(\omega t - 80^\circ)$
  - **Question 5:** A 40 kHz sinusoidal voltage has zero phase angle and a maximum amplitude of 2.5 mV. When this voltage is applied across the terminals of a capacitor, the resulting steady-state current has a maximum amplitude of 125.67  $\mu$ A.
    1. What is the frequency of the circuit in radians per second ?
    2. What is the phase angle of the current ?
    3. What is the capacitive reactance of the capacitor ?
    4. What is the capacitance of the capacitor in microfarads ?
    5. What is the impedance of the capacitor ?
  - **Question 6:** A 400  $\Omega$  resistor, 87.5 mH inductor and a 312.5 nF capacitor are connected in series. The series-connected elements are energized by a sinusoidal voltage source whose voltage is  $500\cos(8000t + 60^\circ)$  V.
    1. Draw the frequency-domain equivalent circuit.
    2. What is the phase angle of the current ?
    3. reference the current in the direction of the voltage rise across the source, and find the phasor current.
    4. Find the steady-state expression for  $i(t)$ .
  - **Question 7:**
    1. For the circuit in Fig.1, find the frequency (in radians per second) at which the impedance  $Z_{ab}$  is purely resistive.
    2. Find the value of  $Z_{ab}$  at the frequency of (1).

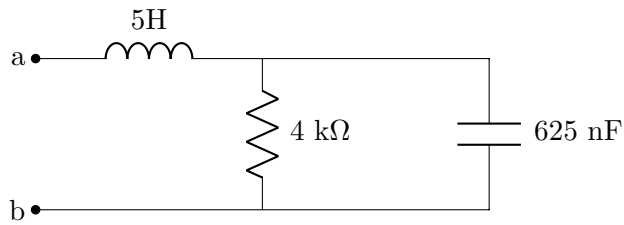


Fig.7

- **Question 8:** Find  $Z_{ab}$  for the circuit shown in Fig.2

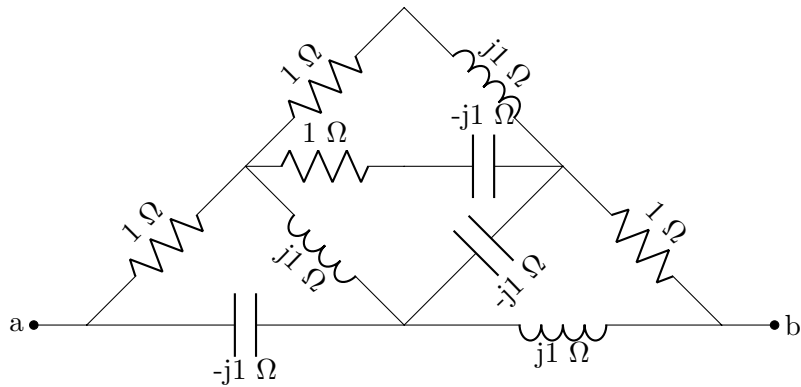


Fig.8

- **Question 9:** Find the Thevenin equivalent circuit with respect to the terminals a,b for the circuit shown in Fig.3

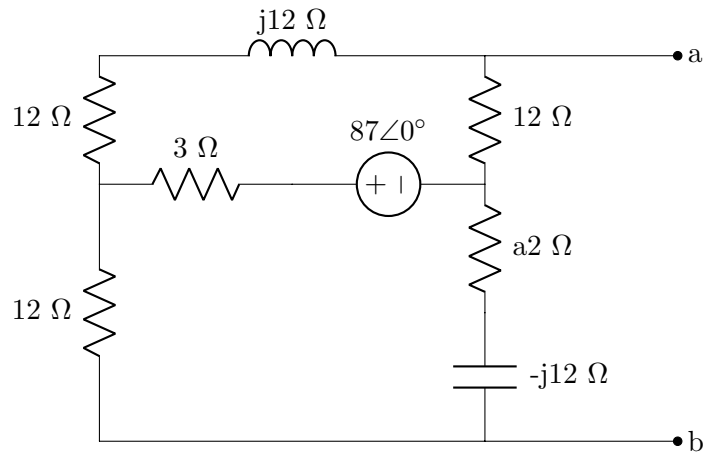


Fig.9

- **Question 10:** Find the Thevenin impedance seen looking into the terminals a,b of the circuit in Fig.9 if the frequency of operation is 25 krad/s.

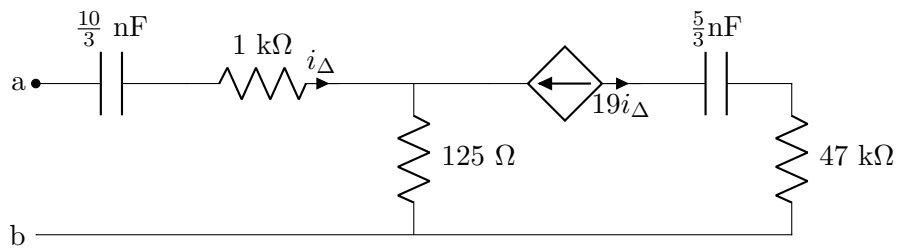


Fig.10

- **Question 11:** Use the node-voltage method to find the phasor voltage  $V_g$  in the circuit shown in Fig.5

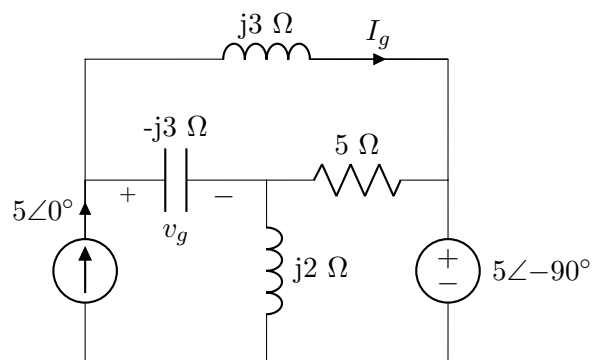


Fig.11