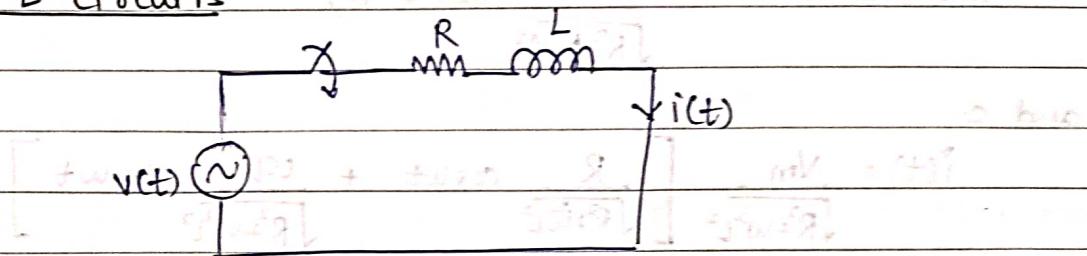


## PHASOR ANALYSIS

### ① R-L circuits



Using KVL,

$$v(t) = iR + L \frac{di}{dt}$$


$$V_m \cos \omega t = iR + L \frac{di}{dt} \quad mV = (3) \text{ I}$$

Assuming For the homogeneous system,  $L \frac{di}{dt} + iR = 0$

$$i = Ae^{-Rt/L}$$

Assuming the full solution as
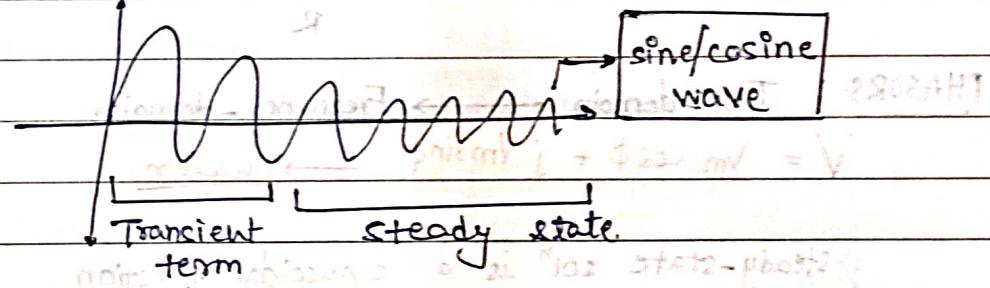
$$i(t) = Ae^{-Rt/L} + B \cos \omega t + C \sin \omega t$$



sudden opening/closing of a switch

$$V_m \cos \omega t = Ae^{-Rt/L} + BR \cos \omega t + L(-ARe^{-Rt/L} - B \sin \omega t + C \cos \omega t)$$

comparing co-efficients of cos and sine,

$$V_m = BR + \omega PL C \quad CR - BL \omega = 0$$

$$V_m = \frac{CR^2 + C(\omega L)}{\omega L} \quad BWL = CR$$

$$C = \left( \frac{\omega L}{R^2 + (\omega L)^2} \right) V_m \quad B = \left( \frac{R}{R^2 + (\omega L)^2} \right) V_m$$

A turns out to be  $\frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta)$

and so.


$$i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \left[ \frac{R}{\sqrt{R^2 + \omega^2 L^2}} \cos \omega t + \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} \sin \omega t \right] - \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta) e^{-Rt/L} + I_0 e^{-Rt/L}$$

$$v(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \left[ \cos(\omega t + \phi - \theta) - \cos(\phi - \theta) e^{-\frac{Rt}{L}} \right] + I_0 e^{-\frac{Rt}{L}}$$

*Steady state response*      *Transient response*

$$\tan \theta = \left( \frac{XL}{R} \right)$$
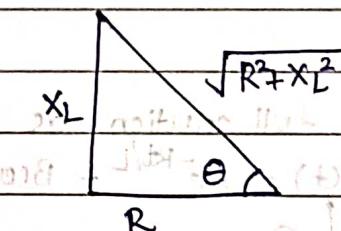
$$\cos \theta = \frac{R}{\sqrt{R^2 + \omega^2 L^2}}$$



PHASORS : Time-domain  $\rightarrow$  Frequency-domain

$$V = V_m \cos \phi + j V_m \sin \phi \rightarrow \text{phasor}$$

1) steady-state soln is a sinusoidal function

2) frequency of response signal is identical to frequency of source signal

3) max. amplitude of steady-state response is  $V_m$  and

max. amplitude of signal source is  $V_m$ .

4) Phase angle of voltage source:  $\phi$ ; response signal:  $\phi - \theta$

$$\theta = \tan^{-1} \left( \frac{XL}{R} \right)$$

### PHASORS


$$V = V_m \cos(\omega t + \phi)$$

$$= \operatorname{Re} (V_m e^{j\phi} \cdot e^{j\omega t})$$

$$\Rightarrow 1 \angle \phi = e^{j\phi}$$

$\cdot V_m e^{j\phi}$   
magnitude  
phase

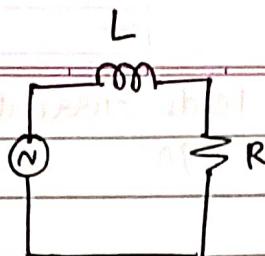Steady-state solution:  $\operatorname{Re}(A e^{j\phi} e^{j\omega t})$



$$I_{\text{steady-state}} = \operatorname{Re} \{ I_m e^{j\beta} e^{j\omega t} \}$$

$$L \frac{di}{dt} + iR = V$$

$$\operatorname{Re} \{ j\omega L I_m e^{j\beta} e^{j\omega t} \} + \operatorname{Re} \{ R I_m e^{j\beta} e^{j\omega t} \} = \operatorname{Re} \{ V_m e^{j\phi} e^{j\omega t} \}$$

$$\operatorname{Re} \{ (j\omega L + R) I_m e^{j\beta} e^{j\omega t} \} = \operatorname{Re} \{ V_m e^{j\phi} e^{j\omega t} \} \quad \text{--- (1)}$$

if instead we would have used sine in the analysis

i.e.  $V = V_m \sin(\omega t + \phi)$ , we have  $\operatorname{Re} \{ V_m e^{j\phi} e^{j\omega t} \} = V_m \sin(\omega t + \phi)$

$$\operatorname{Im} \{ (j\omega L + R) I_m e^{j\beta} e^{j\omega t} \} = \operatorname{Im} \{ V_m e^{j\phi} e^{j\omega t} \} \quad \text{--- (2)}$$

From (1) and (2)

$$(j\omega L + R) I_m e^{j\beta} = V_m e^{j\phi} \quad \text{--- (3)}$$

$$|I_m e^{j\beta}| = \frac{V_m e^{j\phi}}{(R + j\omega L)}$$

### (A) RESISTOR

$$V = iR$$

$$V = R (\operatorname{Im} \cos(\omega t + \theta_i))$$

↓ Phasor Transformation

$$V = R I_m e^{j\theta_i} = R \operatorname{Im} \angle \theta_i$$

$$V = R I$$

$$I \Sigma = V$$

in-phase

no phase-shift b/w the current and voltage across a resistor

### (B) INDUCTOR

$$i = \operatorname{Im} \cos(\omega t + \theta_i)$$

$$V = L \frac{di}{dt} = L \operatorname{Im} \omega (-\sin(\omega t + \theta_i))$$

$$V = -WL \operatorname{Im} \cos(\omega t + \theta_i - 90^\circ)$$

$$V = -WL I_m e^{j(\theta_i - 90^\circ)} = -WL I_m e^{j\theta_i} e^{-j\pi/2} = (j\omega L)(e^{j\theta_i} \operatorname{Im})$$

$$V = (j\omega L) I$$

(phasor voltage) =  $(j\omega L) \times$  (phasor current)

$$V = (wL \angle 90^\circ) (Im \angle 0^\circ)$$

$$V = wL Im \angle (0^\circ + 90^\circ)$$

Voltage leads current by  $90^\circ$ .

Phase shift of  $90^\circ \rightarrow$  Time shift of  $(T/4)$ .

### C CAPACITOR

$$V = V_m \cos(\omega t + \theta_i)$$

$$\text{Q} \quad V = \frac{1}{C} \int i \cdot dt = \frac{1}{C} \int (A + jB) dt =$$

$$i = C \frac{dV}{dt} = C \theta_m \omega \cdot (-\sin(\omega t + \theta_i))$$

$$i = C \omega V_m \cos(\omega t + \theta_i + 90^\circ)$$

$$I = wC \downarrow e^{j(90^\circ)} (e^{j\theta_i} V_m)$$

$$V = \left( \frac{1}{jwC} \right) I$$

$$V = \frac{1}{wC} Im \angle \theta_i - 90^\circ$$

i.e.

$$V = \frac{I \cdot (V_m)}{jwC} e^{-j(90^\circ)}$$

$$V = \frac{Im}{wC} \angle \theta_i - 90^\circ$$

$$V = \frac{Im}{wC} \angle -90^\circ$$

### IMPEDANCE & REACTANCE

$$V = Z I$$

Impedance = ratio of phasor voltage to its current phasor.

$\Rightarrow$  Kirchoff's Law in Frequency Domain.

$V_1, \dots, V_n$  represent voltages around a closed path in a circuit.

If the circuit is in a sinusoidal steady state:

$$V_1 + V_2 + \dots + V_n = 0$$

$$\text{i.e. } V_{m1} \cos(\omega t + \theta_1) + V_{m2} \cos(\omega t + \theta_2) + \dots + V_{mn} \cos(\omega t + \theta_n) = 0$$

$$\operatorname{Re} \left\{ (V_{m1} e^{j\theta_1} + V_{m2} e^{j\theta_2} + \dots + V_{mn} e^{j\theta_n}) e^{j\omega t} \right\} = 0$$

$$\operatorname{Re} \left\{ (V_1 + V_2 + \dots + V_n) e^{j\omega t} \right\} = 0 \text{ as } e^{j\omega t} \neq 0$$


$$V_1 + V_2 + \dots + V_n = 0 \quad \leftarrow \text{KVL in frequency domain}$$

$$I_1 + I_2 + \dots + I_n = 0 \quad \leftarrow \text{KCL in frequency domain}$$

### COMBINING impedances in SERIES and PARALLEL

⇒ Series :-

Same phasor current  $I$  is carried

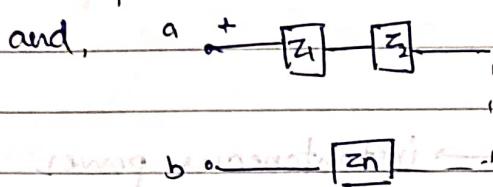

$$V_{ab} = Z_1 I + Z_2 I + \dots + Z_n I$$

$$ZI = (Z_1 + Z_2 + \dots + Z_n) I$$

$$Z = Z_1 + \dots + Z_n$$

IMP. identities

$$Z = a + j b = (\sqrt{a^2 + b^2}) \angle \tan^{-1}(b/a)$$

$$\frac{1}{a + j b} = \frac{1}{\sqrt{a^2 + b^2}} \angle -\tan^{-1}(b/a)$$

$$\frac{a \angle b^\circ + j w}{k \angle m^\circ} = \frac{(a)}{k} + j \frac{(b-w)}{k} = (a \angle b^\circ)(k \angle m^\circ) = (ak) \angle (b+m)$$

⇒ Parallel :-

$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n} \quad \text{conductance: } Y = \frac{1}{Z}$$

using  $I = I_1 + \dots + I_n$

$$\frac{N}{Z_{eq}} = \frac{V}{Z_1} + \frac{V}{Z_2} + \dots + \frac{V}{Z_n}$$

Q:)

$$i_s = 8 \cos(200,000t) \text{ A}$$

$$i_1 = 40 \angle -37^\circ = 4 \angle -37^\circ$$

A:)

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

$$i_2 = 40 \angle -37^\circ = 4 \angle -90^\circ$$

$$Z_1 = 10 \quad Z_2 = 6 + 8j \quad Z_3 = -5j \quad i_3 = 40 \angle -37^\circ = 8 \angle 53^\circ$$

$$\frac{1}{Z} = \frac{10}{100} + \frac{6-8j}{100} + \frac{20j}{100} = 16 + 12j$$

$$Z = \frac{100}{400} (16 - 12j) = 4 - 3j$$

$$Z = 5 \angle -37^\circ$$

$$V = ZI = 40 \angle -37^\circ$$

$$I = 8 \angle 0^\circ$$

### Adding cosines with Phasors

$$Y_1 = 20 \cos(\omega t - 30^\circ) \quad Y_2 = 40 \cos(\omega t + 60^\circ)$$

$$= 20 \angle -30^\circ \quad Y_2 = 40 \angle 60^\circ$$

$$\bullet 17.32 - 10j + 20 + 34.64j$$

$$Y = 37.32 + 24.64j$$

$$Y = 44.72 \angle 33.43^\circ$$

### POWER



$P = Vi$  → instantaneous power

④ dir^n of current is dir^n of voltage drop → +

$$V = V_m \cos(\omega t + \theta_v) \quad i = I_m \cos(\omega t + \theta_i)$$

$$\Rightarrow V = V_m \cos(\omega t + \theta_v - \theta_i) \quad i = I_m \cos(\omega t)$$

$$P = V_m I_m \cos(\omega t + \theta_v - \theta_i) \cos(\omega t)$$

$$= \frac{V_m I_m}{2} [ \cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v - \theta_i) ]$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos 2\omega t \cos(\theta_v - \theta_i)$$

$$- \frac{V_m I_m}{2} \sin 2\omega t \sin(\theta_v - \theta_i)$$

$$\rightarrow f = 2 \times \text{frequency}$$

Pinst. may be -ve for a portion of each cycle, even if the network bw the terminals is passive.

↓  
energy stored in inductors/capacitors → extracted.

### AVERAGE and REACTIVE POWER

$$P = P + P \cos 2\omega t - Q \sin 2\omega t$$

$$(Average \ Power) \quad P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$(Reactive \ Power) \quad Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} p \cdot dt = \frac{1}{T} \int_0^T p \cdot dt$$


$$\langle \sin 2\omega t \rangle = 0 \quad \langle \cos 2\omega t \rangle = 0 \quad (\text{over one } T)$$

$$\text{so, Avg. } P = \frac{V_m I_m (\cos \phi)}{2}$$

### (1) Purely Resistive circuits

$$p = P + P \cos 2\omega t$$

instantaneous real power

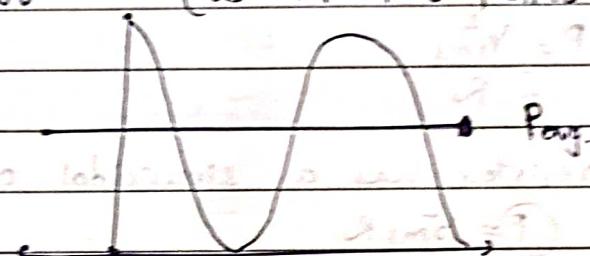

$p$  is never -ve  $\rightarrow$  power can't be extracted but is only dissipated as heat.

### (2) Purely inductive circuits


$$\theta_V - \theta_i = 90^\circ \quad \cos 90^\circ = 0 \quad \sin 90^\circ = 1$$

(reactive power)  $Q(\text{VA}_r)$

$$p = -Q \sin 2\omega t$$

$$P \Rightarrow \text{avg. power} = 0$$

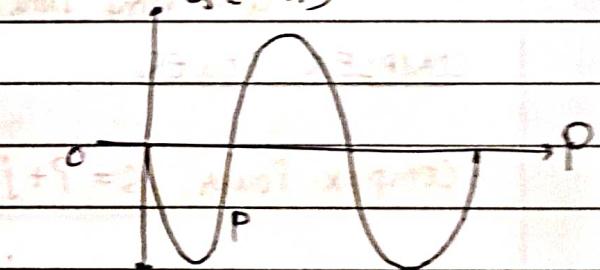$\rightarrow$  power is continuously exchanged by inductor ( $E = 2\omega L$ )




### (3) Purely capacitive circuits

$$\theta_V - \theta_i = -90^\circ$$

$$p = Q \sin 2\omega t$$

$\rightarrow$  not a true load  $\rightarrow$   $P=0$

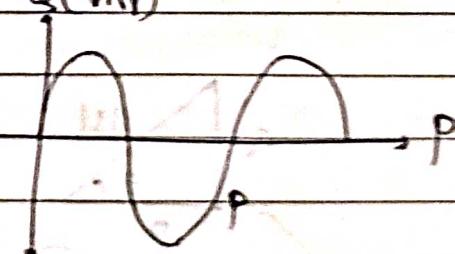$P=0 \rightarrow$  No transform of energy



### POWER FACTOR

$$\text{pf angle} \rightarrow \text{pf} = \cos(\theta_V - \theta_i)$$

$$\text{rf pf} = \sin(\theta_V - \theta_i)$$

lagging pf / reading pf  $\rightarrow$  current leads voltage

$(\theta > 0)$   $\downarrow$  large current  $\downarrow$  large voltage  $\downarrow$  load  $\downarrow$  load

inductive load

capacitive load

$Q > 0$ : inductors  $\rightarrow$  demand/absorb magnetizing Vars  
 $Q \neq 0 < 0$ : capacitors  $\rightarrow$  furnish/deliver magnetizing Vars.

### RMS POWER

tot T

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi_v) \cdot dt$$

$$P = \frac{V_{rms}^2}{R}$$

if resistor has a sinusoidal current ( $I = I_m \cos(\omega t + \phi_i)$ ),

$$\textcircled{P} = I_{rms}^2 R$$

effective value

100V DC delivers same ~~power~~ energy in T seconds as a 100V<sub>rms</sub> AC

$$\boxed{P = (V_{rms} I_{rms}) \cos(\phi_v - \phi_i)}$$


$$\boxed{Q = (V_{rms} I_{rms}) \sin(\phi_v - \phi_i)}$$

### COMPLEX POWER

Complex Power,  $S = P + jQ$ , Unit  $\Rightarrow$  VA

can be found from V and I phasors directly.
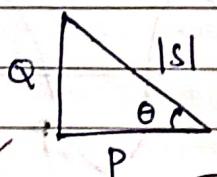
$$P = \text{Re}(S) \quad Q = \text{Im}(S)$$



$\theta$  is the Pf angle.

$$\text{as } Q = \tan(\phi_v - \phi_i) = \tan \theta$$

if any two of

P, Q, |S|,  $\theta \rightarrow$  known  $\Rightarrow$  all ④ Known.

$$\text{apparent power} \Rightarrow |S| = \sqrt{P^2 + Q^2} \text{ VA}$$

VA capacity required to supply the average power

unless  $\theta(Pf) = 0^\circ$ ,  $|S| > P \rightarrow (\text{VA capacity required}) \rightarrow (\text{avg. power})$

Q1.) 240 V<sub>rms</sub>, P<sub>avg.</sub> = 8 kW, lagging P.f. of 0.8

a) S = ? b) Z = ?

A1.) a) Q is +ve (lagging Pf)

$$\cos \phi = \frac{4}{5} \quad \tan \phi = \frac{3}{4} = \frac{Q}{P}$$

$$Q = +6 \text{ kVA}$$

$$S = (8+6j) \text{ kW}$$

$$b) P = V_{rms} I_{rms} \Rightarrow 8000 \times \frac{100}{\sqrt{3}} = 240 \text{ A}_{rms}$$

$$I_{rms} = \frac{100}{\sqrt{3}}$$

$$\frac{3}{4} = \frac{Z_1}{R}$$


$$Z_1 = \frac{3R}{4}$$

$$Z = 5R = \sqrt{\left(\frac{240}{100}\right)^2 + 3^2} = 5\sqrt{10} \Omega$$

$$P = V_{rms} I_{rms} \cos \phi \Rightarrow 100 \times 41.67 \cos \phi = 41.67 \text{ Amp}$$

$$|Z| = \frac{240}{41.67} = 5.76 \quad \phi = +37^\circ$$

(lagging)

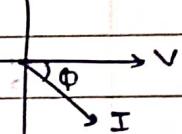

$$Z = 5.76 \angle -37^\circ$$

## X POWER CALCULATIONS

$$S = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + j \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

$$= \frac{V_m I_m}{2} [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)]$$

$$= \frac{V_m I_m}{2} [e^{j(\theta_v - \theta_i)}] = \frac{1}{2} V_m I_m \angle(\theta_v - \theta_i)$$

$$S = V_{rms} I_{rms} \angle(\theta_v - \theta_i)$$

complex power  $\rightarrow$  product of same phasor voltage and conjugate of same phasor current.

$$S = V_{rms} I_{rms} e^{j\theta_v} e^{-j\theta_i} = V_{eff} I_{eff}^*$$

$$S = V_{eff} I_{eff}^* ((V, I) \rightarrow \text{phasor})$$

$$S = \frac{1}{2} V I^*$$

$$V_{eff} Z_{load}$$

( $V_{eff} \rightarrow$  phasor, RMS)

$$S = Z I_{eff} \cdot I_{eff}^* = Z |I_{eff}|^2$$

$$= |I_{eff}|^2 (R + jX)$$

$$= |I_{eff}|^2 R + j |I_{eff}|^2 X$$

$$P = |I_{eff}|^2 R = \frac{1}{2} I_m^2 R$$

$$S = Z |I_{eff}|^2$$

$$Q = |I_{eff}|^2 X = \frac{1}{2} I_m^2 X$$

$$S = V_{eff} \left( \frac{V_{eff}}{Z} \right)^* = \frac{|V_{eff}|^2}{Z^*} = P + jQ$$

if  $Z$  is purely resistive  $\rightarrow Z$  is purely reactive

$$P = |V_{eff}|^2$$


$$P = |V_{eff}|^2$$

R

2001TA1021AD 83009

X

Q:

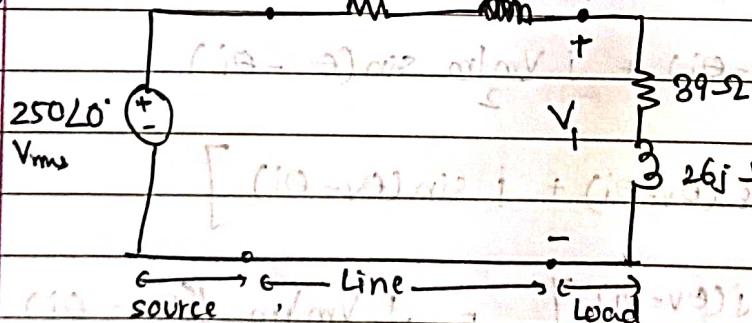

$$Z_{load} = (39 + 26j) \Omega$$

$$Z_{line} = (1 + 4j) \Omega$$

$$(V_{mw})_{source} = 250$$

A)

$I_L$  and  $V_L$

$$Z_{net} = Z_{line} + Z_{load}$$

$$Z_{net} = (40 + 30j) \Omega$$

$$= 50 \angle 37^\circ$$

$$I_L = \frac{V_i}{Z} = \frac{250 \angle 0^\circ}{50 \angle 37^\circ} = 5 \angle -37^\circ$$

$$L, (I_{Im})$$

$$V_L = I_L Z = (5 \angle -37^\circ) (13\sqrt{13} \angle \tan^{-1}(2/3))$$


$$V_L = 234.3 \angle -3.18^\circ$$

b)  $S = |I_{\text{line}}|^2 Z = |I_L|^2 Z$   
 $\Rightarrow (25)(89 + 26j) = 975 + 650j \text{ VA}$

c)  $S_{\text{line}} = |I_{\text{line}}|^2 Z = 25(1 + 4j) = 25 + 100j \text{ VA}$   
 $Q = 100 \text{ VA}, P = 25 \text{ W}$

d)  $S_{\text{source}} = |I_L|^2 Z_{\text{net}} = 25(40 + 30j) \text{ VA}$   
 $P = 1000 \text{ W}, Q = 750 \text{ VA}$

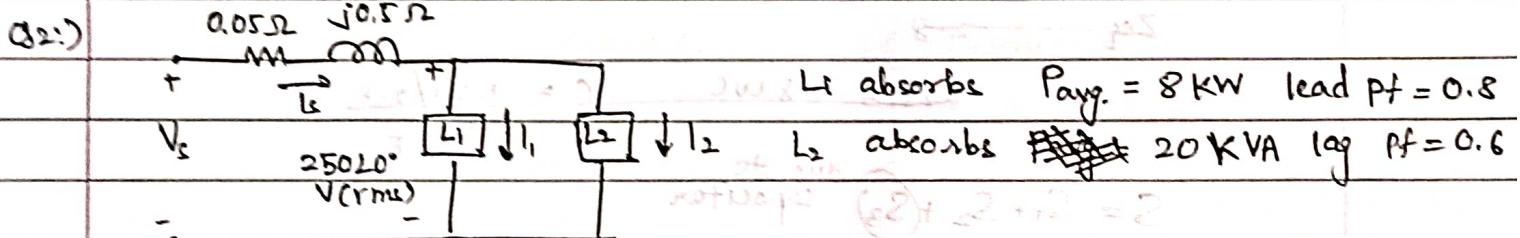$S_s = -V_s I_L^*$  current reference is in the dir' of  $i$   
voltage sense



A2)  $S_1 = 8000 + j6000 = (8 + j6) \text{ kW}$

$S = (250 \angle 0^\circ)(I_s^*) = 250 I_1^* + 250 I_2^* = S_1 + S_2$

$S = S_1 + S_2$  | sum the complex powers geometrically

$\frac{3}{P} = \frac{S}{P}$   $S_1 = 8000 + j6000 = (8 + j6) \text{ kW}$

$S_2 = (12 + j16) \text{ kW}$   $P^2 + 16P^2 = \frac{4}{9}P^2 = \frac{4}{9} \text{ KVA}$

$\frac{S}{P} = \frac{4}{3}$

$S = 20 + 10j = 250(I_s^*)$

$I_s^* = 20 + 10j$   $I_s^* = (20 - 10j) \times 1000$

$I_s = 80 - 40j$   $V_s = 250$

$Z = 250 \angle 0^\circ$   $= 2.8 \angle 26.56^\circ$

$\theta = 26.56^\circ$

$Pf = 26.56^\circ \rightarrow \cos(26.56^\circ) = 0.894 \text{ lagging}$

$S = 22.3 \angle 26.56^\circ$   $|S| = 29.44 \text{ A}$   $P = 20000 \text{ VA}$

$(P_{\text{loss}})_{\text{line}} = |I_L|^2 R = (89.44)^2 \times 0.05 = 4000 \text{ W}$

$$Z = 2.8 \angle 26.56^\circ = (2.5) + j1.25$$

$$(Z_L = 2.45 + j0.75)$$

$$j25 - j1.25 \rightarrow \frac{1}{j\omega C} = 1.25$$

$$Z_{\text{NET}} = (0.05 + j0.5) + Z_L \quad Z = \frac{1}{(120\pi) \times 1.25} = 2.1 \text{ mF}$$

$$\frac{1}{Z_{\text{eq}}} = \frac{1}{Z_1} + \frac{1}{Z_{\text{cap}}} \quad \frac{1}{Z_{\text{eq}}} = \frac{1}{Z_L} + \frac{1}{Z_C}$$

$$\frac{1}{2.5 + j1.25} + \frac{1}{j\omega C} = 2.45 - j0.75 + j\omega C$$

$$\frac{1}{Z_{\text{eq}}} = \frac{2.5 - j1.25}{2.8} + j\omega C \quad 0.75 = 2.5 - j\omega C$$

$$1.25 = 2.8 - j\omega C$$

$$S = S_1 + S_2 + (S_3) \text{ due to capacitor}$$

$$\text{so, } Q_{\text{cap}} = -0.10 \text{ KVAR} = Z_C |V_2|^2$$


$$3.14 \times 3.1 \times 10^3 = Z (250)^2$$

$$Z_C = -6.25 \Omega$$

$$\frac{1}{j\omega C} = \frac{1}{6.25} \quad (C = 424.41 \mu F)$$

It will make the pf=1

### # Power (Apparent) in Series

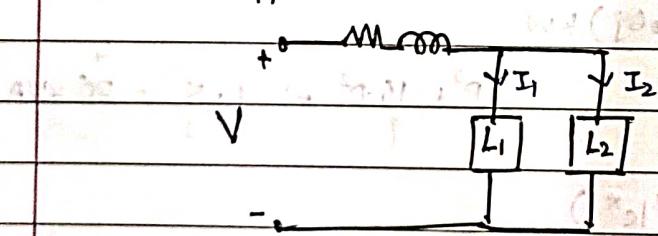

$$S = V_{\text{rms}} I_{\text{rms}}^* = V_{\text{rms}} (I_1 + I_2)^*$$


$$= V_{\text{rms}} I_1^* + V_{\text{rms}} I_2^*$$

$$S = S_1 + S_2 \quad (\text{L}_1, \text{L}_2 \text{ are in parallel})$$

combined pf → Find S and use  $\tan \phi = \underline{Q}$

Power supplied =  $\text{Re}(S) [\text{avg. P}] + [\text{Pavg. lost in the transmission lines}]$

$$Q = |V_{\text{eff}}|^2 / X \quad (V_{\text{eff}} \cdot P_S) = 0.8^2 \cdot 1.1 = 0.64 (0.8)$$

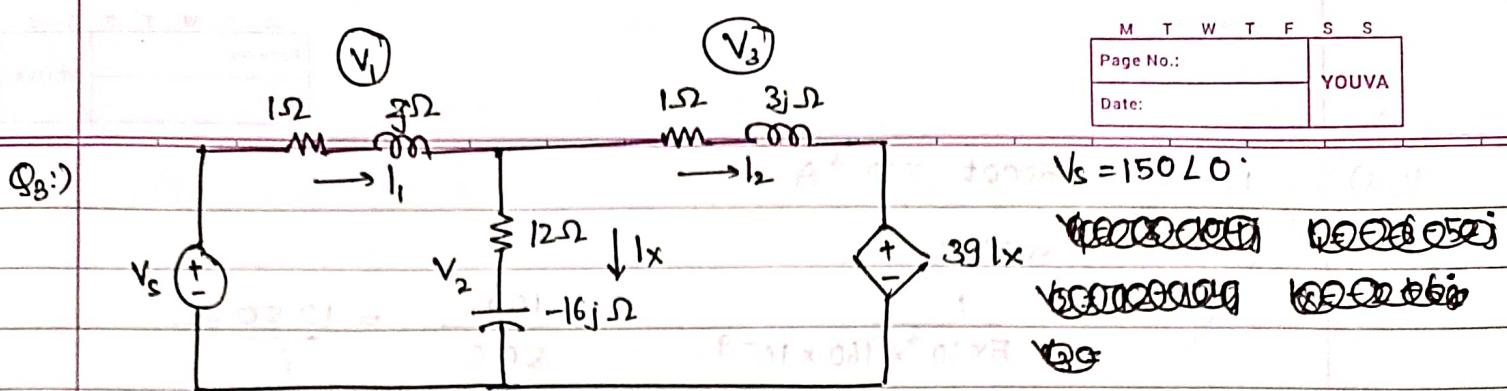

$$\textcircled{1} \quad V_1 = 78 - 104j \quad I_1 = -26 - 52j \quad V_2 = 72 + 104j \quad I_2 = -2 + 6j$$

$$V_3 = 150 - 130j \quad I_3 = -24 - 58j$$

$$\textcircled{2} \quad \text{① } Z = 1 + 2j \quad (\text{I} = \frac{\sqrt{26^2 + 52^2}}{\sqrt{2}}) \rightarrow \text{RMS}$$

~~$$= \text{116.27 VA}$$~~

$$S_1 = \frac{1}{2} VI^* = \frac{1}{2} (-26 + 52j)(78 - 104j)$$

$$= 1690 + 3380j \text{ VA}$$

$$S = \frac{1}{2} VI^*$$

If V, I given in complex forms

$$S_2 = \frac{1}{2} (72 + 104j)(-2 - 6j) = 240 - 320j$$

$$S_3 = \frac{1}{2} (150 - 130j)(-24 - 58j) = 1970 + 5910j$$

\textcircled{2}

$$V_s$$

$$V_2$$

$$V_s - V_2 = V_1$$

$$V_s = V_1 + V_2 = 150 - 130j = S$$

$$I_s = I_1 = -26 - 52j$$

$$S_{s1} = \frac{1}{2} (150)(-26 + 52j) = (1950 + 3900j) \text{ VA}$$

$$V_2 - 39I_x = V_3 \quad V_{s2} = V_2 - V_3 = 72 + 104j - 150 + 130j$$

$$V_{s2} = -78 + 234j$$

$$S_{s2} = \frac{1}{2} V_{s2} I_2 = (-5850 - 5070j) \text{ VA}$$

$$\textcircled{3} \quad (P)_{\text{delivered}} = 1690 + 1970 + 240 + 1950 \\ = 5850 = (P)_{\text{absorbed}}$$

$$(Q)_{\text{delivered}} = 3380 + 5910 \quad (Q)_{\text{abs}} = 5070 + 3900 + 320 \\ = 9290 \text{ VA} \quad (= 9290 \text{ Var})$$