



Indian Institute of Technology, Bombay
Department of Electrical Engineering
Power Engineering-I (EE-114)

Friday
March 31 2023

Time: 0.5 hour

Quiz 01

Maximum Marks: 25

1. Determine the phasor form for the following voltages:


1. $v_1(t) = 1500\sin(1885.2t - \pi/3)$

2. $v_2(t) = 50\sin(314.2t) + 86.60\cos(314.2t)$

3. $v_3(t) = 10\sin(377t) + 17.32\cos(314.2t)$

[5]

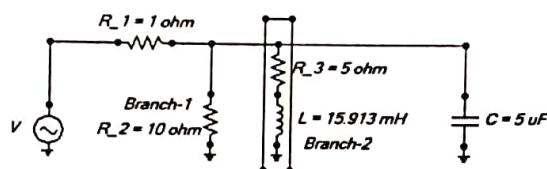2. Consider the single phase circuit show in Figure and answer the following questions. $V = 600\angle 0$ V. The frequency of the voltage source is 50 Hz.



1. What is the impedance seen by the source?
2. What is the current in branch 1 ?
3. What is the current in branch 2 ?
4. What are the various powers in branch 1?
5. What are the various powers in branch 2?
6. What is the power factor of the source?
7. Sketch a neat phasor diagram for the circuit.
8. Determine reduction in losses if capacitor of $5 \mu\text{F}$ is added in parallel with the two branches.

[20]

Student's name:

End of exam