
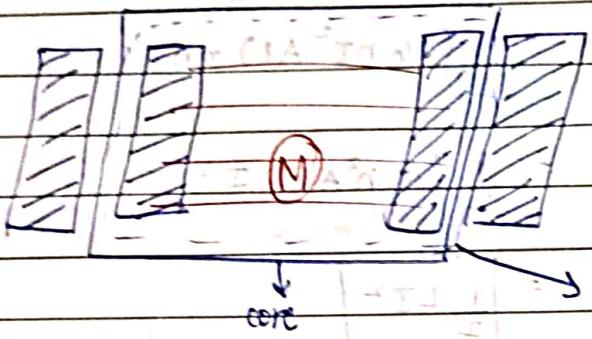

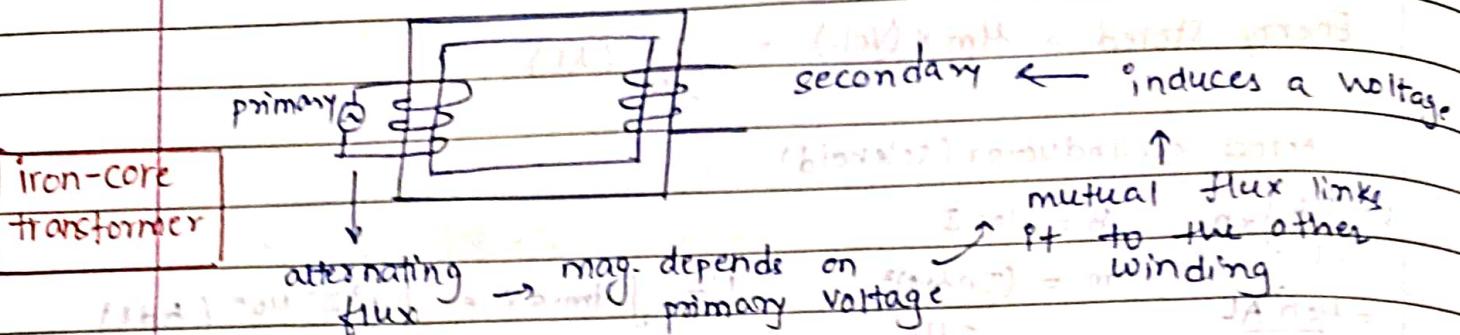
## TRANSFORMERS


⇒ two or more windings coupled by mutual magnetic flux.



windings also produce an additional flux: leakage flux

links one winding without linking the other.

### NO-LOAD CONDITIONS

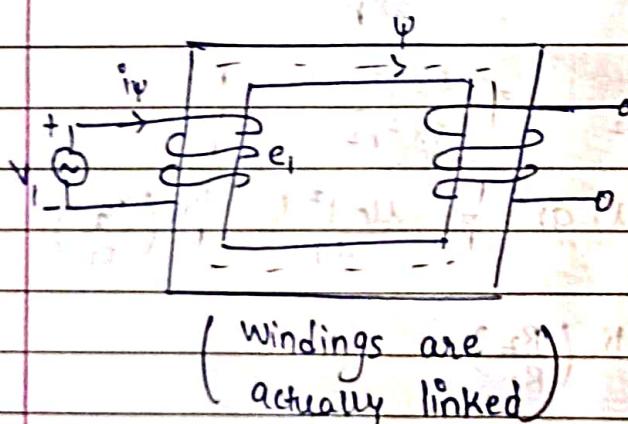

a small steady state current,  $i\phi \rightarrow$  exciting current flows in primary and establishes an alternating flux in the magnetic circuit

The flux induces an EMF in primary.  $e_1 = N_1 \frac{d\phi}{dt} = N_1 \frac{d\lambda}{dt}$

$$e_1 = N_1 \frac{d\phi}{dt}$$

$$V_1 = R_1 i\phi + e_1$$

$\lambda$ : flux linkage  
 $\phi$ : flux in core  
linking windings  
 $N_1$ : turns

(leakage flux)  
is ignored

$$\mathcal{E} = \frac{d\Phi}{dt}$$

$$(\mathcal{E} = \omega N_i \Phi_{max} \sin(\omega t + 90^\circ))$$

M T W T F S S  
Page No.:

YOUVA  
Date:

IF,  $\Phi = \Phi_{max} \sin \omega t$  (assumed)

$$e_i = N_i \Phi_{max} \omega \cos \omega t \rightarrow \text{leads } \Phi \text{ by } 90^\circ$$

rms value,  $E_i = \frac{2\pi f N_i \Phi_{max}}{\sqrt{2}}$   $E_i = \sqrt{2\pi f N_i \Phi_{max}}$

if  $N_i = E_i$  ( $R \rightarrow 0$ )

$$\Phi_{max.} = \frac{V_i}{\sqrt{2\pi f N_i}}$$

core flux depends SOLELY on the applied voltage.

If resistance and leakage-inductance voltage drops are negligible  $\rightarrow$  core flux depends on applied voltage.

$\Rightarrow$  Because of non-linear magnetic properties of iron  $\rightarrow$  waveform of exciting current is diff. from that of flux.

$i_\phi$  analyzed by Fourier series  $\rightarrow$  Fundamental + Odd Harmonics

Fourier series

in phase with EMF  $\rightarrow$  lagging the EMF by  $90^\circ$

core-loss component

magnetizing current

(The) supplies the power absorbed by hysteresis & eddy-current losses

(core-loss component of exciting current.)

fundamental lag component

(exciting current) - (core-loss component) = magnetizing current

$\Rightarrow$


exciting current = sinusoidal current with same  $\omega$ , RMS value as the exciting current & produces same avg. power

core-loss,

$$P_c = E_i i_\phi \cos \theta_c$$

$i_m \rightarrow$  equivalent sine wave current, in-phase with the flux, having the same RMS value as magnetizing current

### SECONDARY CURRENT IDEAL TRANSFORMER

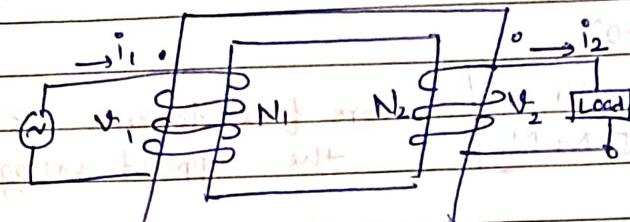

positive secondary  $\rightarrow$  out of the winding

#### IDEAL

- 1) Winding  $R \rightarrow 0$  MMF opp. to created by the primary current.
- 2)  $\phi$  confined to core
- 3) all  $\phi$  links both windings (leakage flux  $\rightarrow 0$ )
- 4)  $u$  is so high  $\rightarrow$  negligible exciting MMF to establish the flux.

$$\frac{V_1}{(\text{Applied})} = e_1 = N_1 \frac{d\phi}{dt} \quad V_2 = e_2 = N_2 \frac{d\phi}{dt}$$

$$\boxed{\frac{V_1}{V_2} = \frac{N_1}{N_2}} \rightarrow \text{Transforms voltage directly in ratio of no. of turns}$$

For a load in secondary, current  $i_2$ , MMF  $N_2 i_2$

core flux  $\rightarrow$  primary voltage ONLY  $\therefore$  independent of load.  
 won't change as  $u \rightarrow \infty$  ( $R \rightarrow 0$ ) ( $E \rightarrow 0$ )

core flux is unchanged by presence of a load at secondary


$$\hookrightarrow \text{exciting MMF} = (N_1 i_1 - N_2 i_2) = 0$$

$$\Rightarrow N_1 i_1 = N_2 i_2$$

$$\boxed{i_1 = N_2} \\ \boxed{i_2 = N_1}$$

any change in secondary MMF as a result of a load  $\Rightarrow$  accompanied by a change in the primary MMF

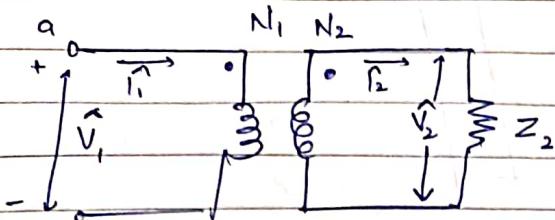Also,  $V_1 i_1 = V_2 i_2$  (Net power balance;  $\text{losses} = 0$ )



Voltage across a dot-marked to an unmarked terminal will be of the same instantaneous polarity for primary and secondary.

$\hat{i}_1$  and  $\hat{i}_2$  are in-phase  
 into dotted terminal  $(N_1 i_1 = N_2 i_2)$  out of the dotted terminal.  $\hat{V}_1$  and  $\hat{V}_2$  are in-phase  
 IMP.

$$\hat{V}_1 = \left(\frac{N_1}{N_2}\right) \hat{V}_2$$

$$\hat{V}_2 = \left(\frac{N_2}{N_1}\right) \hat{V}_1$$

$$\hat{i}_1 = \left(\frac{N_2}{N_1}\right) \hat{i}_2$$

$$\hat{i}_2 = \left(\frac{N_1}{N_2}\right) \hat{i}_1$$

$$\frac{\hat{V}_1}{\hat{i}_1} = \left(\frac{N_1}{N_2}\right)^2 \frac{\hat{V}_2}{\hat{i}_2} \Rightarrow Z_1 = \left(\frac{N_1}{N_2}\right)^2 Z_2$$

an impedance  $Z_2$  in secondary circuit

# can be replaced by equivalent  $Z_1$  in primary circuit

⇒ Voltages → direct ratio; currents → inverse ratio  
 impedances → direct ratio squared; power (V.A.) → unchanged.


### ACTUAL TRANSFORMER

winding resistances; leakage fluxes; finite exciting currents  
 $\mu_b + \mu_{ab}$  (finite permeability)

equivalent-circuit method

theory of magnetically-coupled coils

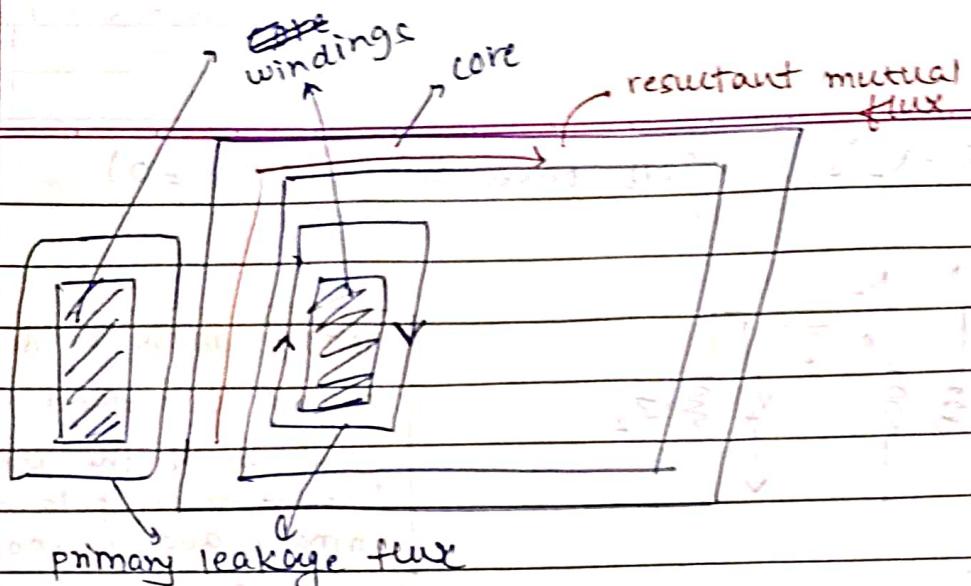Primary → Total flux linking the primary winding = (resultant mutual flux (iron core)) + primary leakage flux



→ Induces voltage in the  $\rightarrow$  adds to that produced by the primary flux.

→ As large part of leakage flux is in AIR


FLUX and Voltage induced vary linearly with  
represented as primary leakage inductance  $L_1$

$$L_1 = \frac{\Delta\Phi}{I_1} \rightarrow \text{leakage-flux linkage}$$

$\downarrow$

$I_1 \rightarrow \text{primary current}$

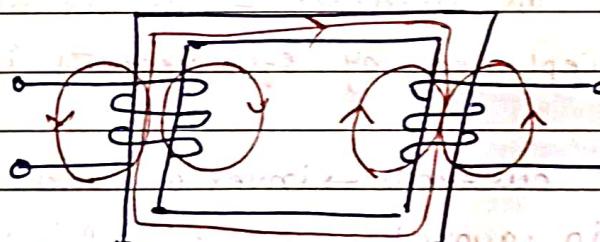primary leakage reactance,  $X_1 = 2\pi f L_1$  + Voltage drop across resistance  $R_1$



(leakage flux adds to)  
primary flux

CONSIDERING ① COIL ONLY

$$\Phi_1 = \Phi_{1K1} + \Phi_{12}$$

$$\Delta_1 = N_1 \Phi_1 = N_1 \Phi_{1K1} + N_1 \Phi_{12} = \Delta_{1K1} + \Delta_{12}$$

$$\text{So, } \frac{d\Delta_1}{dt} = \frac{d\Delta_{1K1}}{dt} + \frac{d\Delta_{12}}{dt}$$

$$L_{self} = \frac{d\Delta_{1K1}}{dt} + \frac{d\Delta_{magnetizing}}{dt}$$

(self inductance) = (leakage inductance) + (magnetizing inductance)

considering both the coils :-

$$(\Phi_{\text{net}})_1 = \Phi_{1K-1} + \Phi_{12} + \Phi_{21}$$

$$(\Phi_{\text{net}})_2 = \Phi_{1K-2} + \Phi_{21} + \Phi_{12}$$

self inductance      mutual inductance

$$\Phi_{1K-1} = \frac{N_1 i_1}{R_{1K-1}}$$

$$\Phi_{\text{core}} = \frac{N_1 i_1}{R_{\text{core}}} = \frac{N_1 i_1 \mu_{\text{core}}}{l_{\text{core}}}$$

$$(\Phi_{\text{net}})_1 = \Phi_{\text{magnetizing}} + (\Phi)_{\text{leakage}}$$

depends on  $i_1$  (primary) current ONLY

$$(\lambda_{\text{net}})_1 = \lambda_{1K-1} + \lambda_{11} + \lambda_{12}$$

$$= i_1 L_{\text{self}} + i_2 M$$

$$(\lambda_{\text{net}})_1 = i_1 \left( \frac{\mu_0 N_1^2 A_{\text{air}}}{l_{1K-1}} + \frac{\mu_0 N_1^2 A_c}{l_{\text{core}}} \right) + \left( \frac{\mu_0 N_1 N_2 A_c}{l_{\text{core}}} \right) i_2$$

and similarly,

$$(\lambda_{\text{net}})_2 = i_2 \left( \frac{\mu_0 N_2 A_{\text{air}}}{l_{1K-2}} + \frac{\mu_0 N_2 A_c}{l_{\text{core}}} \right)$$

$$Hl = Ni \quad \lambda = N\phi = NAB \quad V = d\lambda = d(NAB)$$


$$V = NA \left( \frac{dB}{dt} \right)$$

$$B(t) = \frac{1}{NA} \int V(t) \cdot dt$$

$$\text{primary leakage reactance, } X_L = (2\pi f)^2 L_1$$

$$L = \lambda_1 \rightarrow \begin{array}{l} \text{leakage flux} \\ \text{linkage} \\ i_1 \rightarrow \text{primary current} \end{array}$$

EQUIVALENT PRIMARY CIRCUIT :-

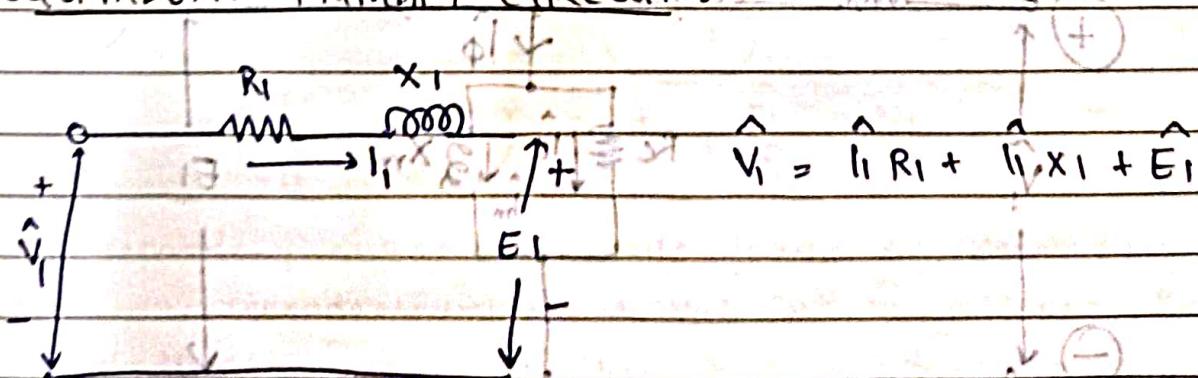

resultant mutual flux  $\rightarrow$  links both primary & secondary windings & is created by combined MMF.

primary  $\rightarrow$  produce MMF to produce resultant mutual flux  
 current  $\rightarrow$  counteract effect of secondary to demagnetize core  
 $\hookrightarrow$  (supply current to the load of the secondary)

$$I_{\text{primary}}, \hat{I}_1 = I_\phi + I_L' \quad \xrightarrow{\text{load component } (I_2')}$$

(producing no change in flux due to primary current)

produce the core magnetic flux (NON-SINUSOIDAL)  $\rightarrow$  component current in primary to counteract the MMF of the secondary current is

$$N_1 I_\phi = N_1 I_1 - N_2 I_2 \\ = N_1 (I_\phi + I_2') - (N_2 I_2)$$


$$\frac{I_2'}{N_2} = \frac{N_1}{N_2} I_2$$

load component of primary = secondary current referred to primary of ideal transformer

$I_\phi \rightarrow$  resolve into  $\hat{I}_m + \hat{I}_c$

lag by  $90^\circ$  in phase with  $E_1$  (core-loss resistance)

$$X_m = 2\pi f l_m$$

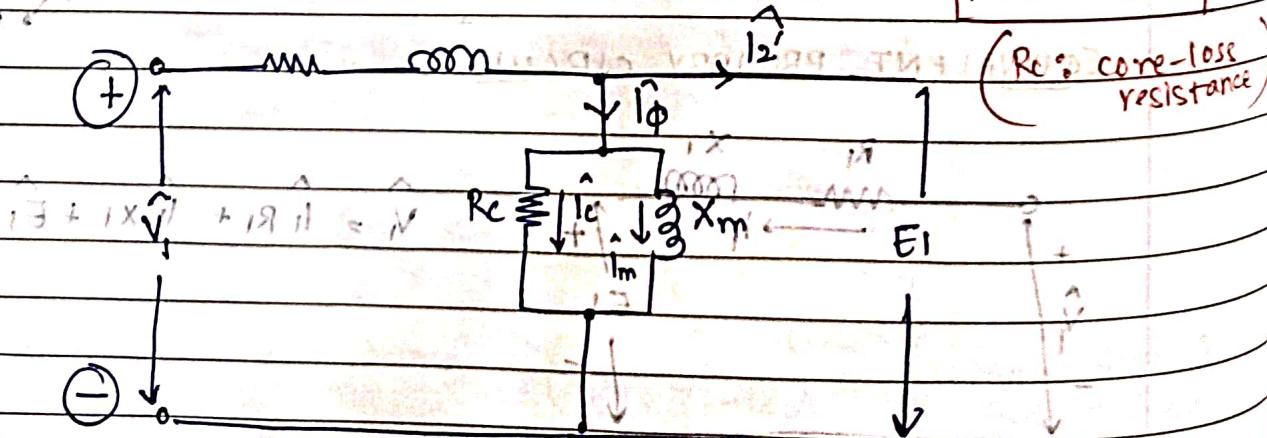

The power, +  $\frac{E_1^2}{R_c}$   $\rightarrow$  core-loss (due to the resultant mutual flux).

$R_c \rightarrow$  magnetizing resistance / core-loss resistance

II impedance of  $R_c$  and  $X_m \Rightarrow$  exciting impedance ( $Z_p$ )

$\Rightarrow$  if  $R_c = \text{constt.}$

$$\text{loss} \propto E_1^2 \propto \Phi_{\max}^2 f^2 \quad (\text{sinusoidal waves})$$

(max value of the resulting mutual flux.)

$X_m \rightarrow$  varies with saturation of iron

if  $X_m = \text{constt.} \Rightarrow I_m$  is independent of 'f' and  
( $I_m \propto$  resultant mutual flux)


### SECONDARY

(Fluxing two windings - T)

resultant mutual flux,  $\Phi$ , induces an EMF,  $\hat{E}_2$  in the secondary and since this flux links both windings,

$$\frac{\hat{E}_1}{\hat{E}_2} = \frac{N_1}{N_2} \quad (\Phi: \text{links both windings})$$

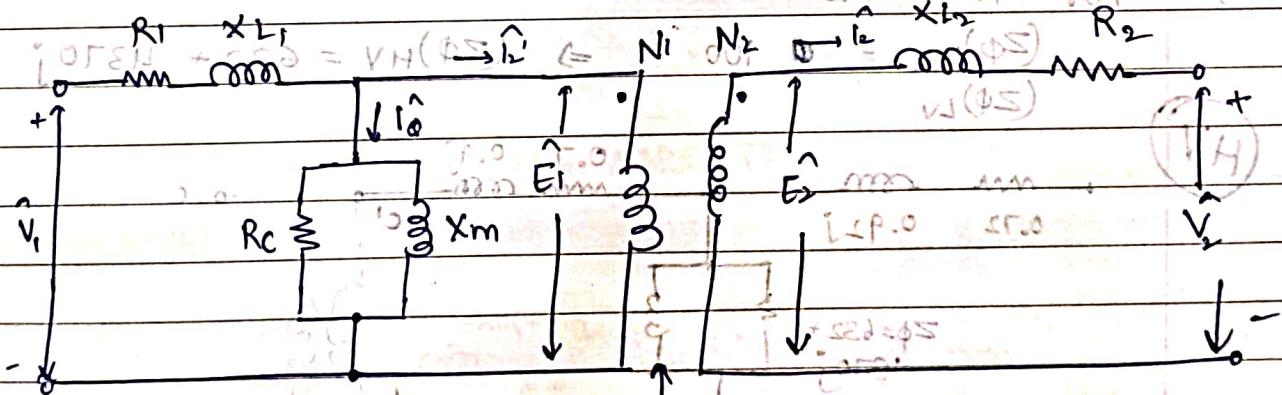$\rightarrow$  just as an ideal transformer.



$$\left( \frac{I_2}{I_1} = \frac{N_2}{N_1} \right) \text{ and } \left( \frac{\hat{E}_1}{\hat{E}_2} = \frac{N_1}{N_2} \right)$$


$\Rightarrow$  The secondary current  $I_2$  also forms a secondary leakage flux  $\rightarrow$  secondary terminal voltage  $V_2$  differs from the induced voltage  $\hat{E}_2$  by voltage drops due to secondary resistance  $R_2$  and secondary reactance (leakage),  $X_{L2} = 2\pi f L_2$ .

so, (Actual transformer) = (Ideal transformer) + (External impedances)

$$X_{L2}' = \left(\frac{N_1}{N_2}\right)^2 X_{L2} \quad R_2' = \left(\frac{N_1}{N_2}\right)^2 R_2$$

(impedances shifted)
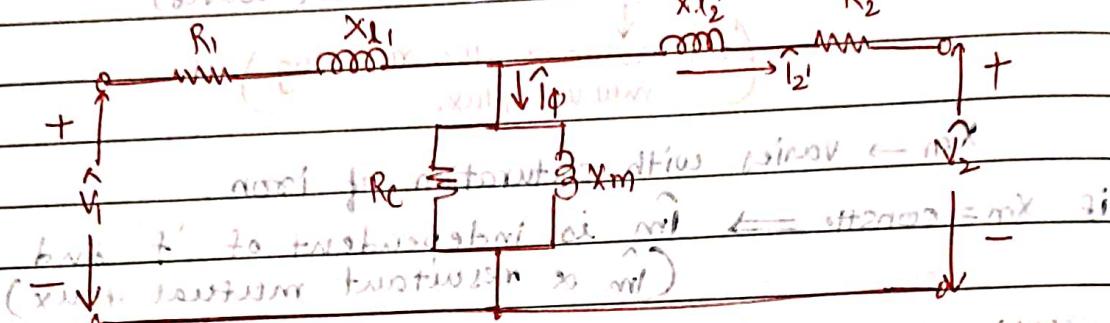
$$V_2' = \left(\frac{N_1}{N_2}\right) V_2$$




(T-equivalent circuit)

e.g., 50 kVA, 2400 : 240 V, 60 Hz, transformer, bus numbers  
leakage impedance =  $0.72 + 0.92j \Omega$  in H.V. winding,  $0.007 + 0.009j$  in L.V.  
impedance of exciting branch,  $Z_\phi = 6.32 + 43.7j \Omega$  viewed from L.V. side


A) For H.V. side

$$(Z_\phi)_{HV} = 100 \Omega \Rightarrow (Z_\phi)_{HV} = 632 + 4370j$$

**HV**

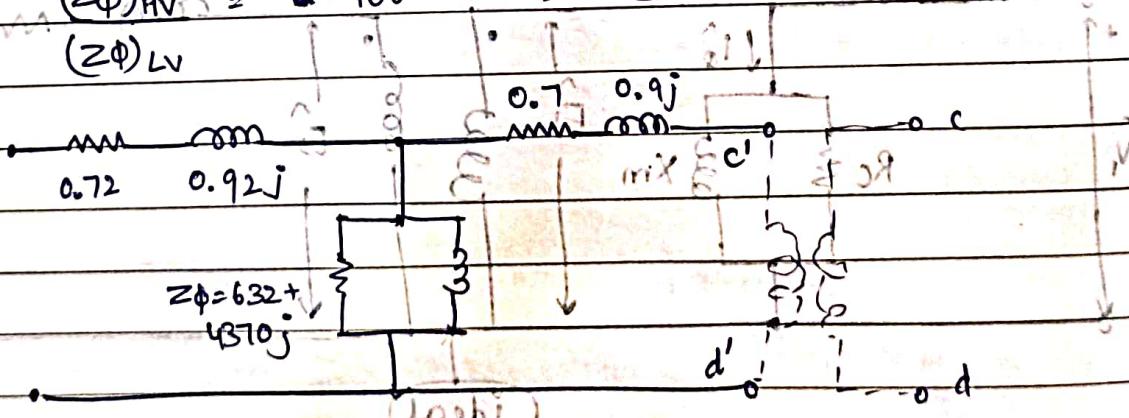

**LV**

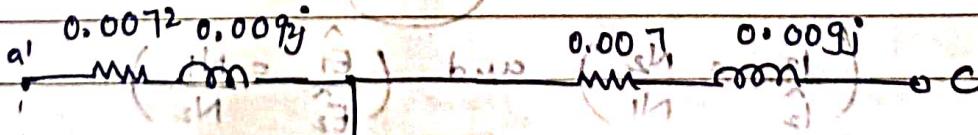

$$Z_\phi = 6.32 + 43.7j$$

Let  $2400 \angle 0^\circ$  be applied on HV side

so, we should get  $2400 \angle 0^\circ$  on LV side referred to HV side


So,

$$\frac{V - 2400}{-0.72 + 0.92j} + \frac{V - 2400}{0.7 + 0.9j} + \frac{V}{632 + 4370j} = 0$$

(neglect)

$$\textcircled{a} \quad V - 2400 \left( \frac{\angle -51.95^\circ}{+16} + \frac{\angle -65.32^\circ}{1.14} \right) = 0$$
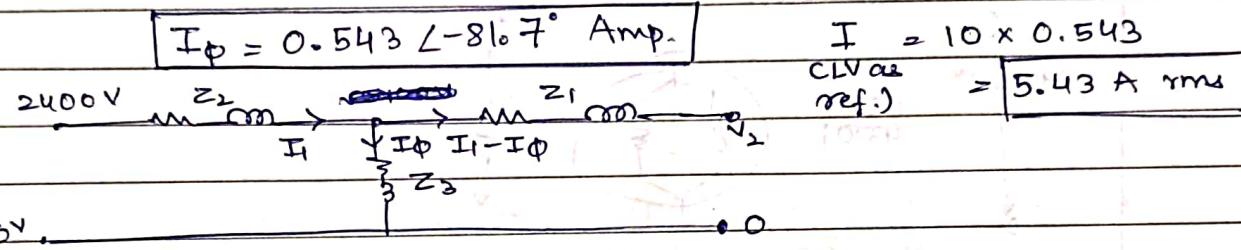
$$\frac{2400}{(632 + 4370j)} = \frac{2400}{4415 \angle 81.7^\circ} = 0.543 \angle -81.7^\circ \text{ Amp.}$$



$$I = 10 \times 0.543$$

$$\text{CLV as ref.)} = 5.43 \text{ A rms}$$

$$2400 - I_1 Z - I_\phi Z_2 = 0$$

$$V_2 + (I_1 - I_\phi) Z_1 - I_\phi Z_3 = 0$$

$$2400 - I_1 Z - (I_1 - I_\phi) Z_1 = 0$$

Variables  $\Rightarrow V_2, I_1, I_\phi$


3 eqn, 3 variables

solve

$$\text{regulation} = \left( \frac{V_2 - V_1}{V_1} \right) \times 100\%,$$

## ENGINEERING ASPECTS


### APPROXIMATIONS

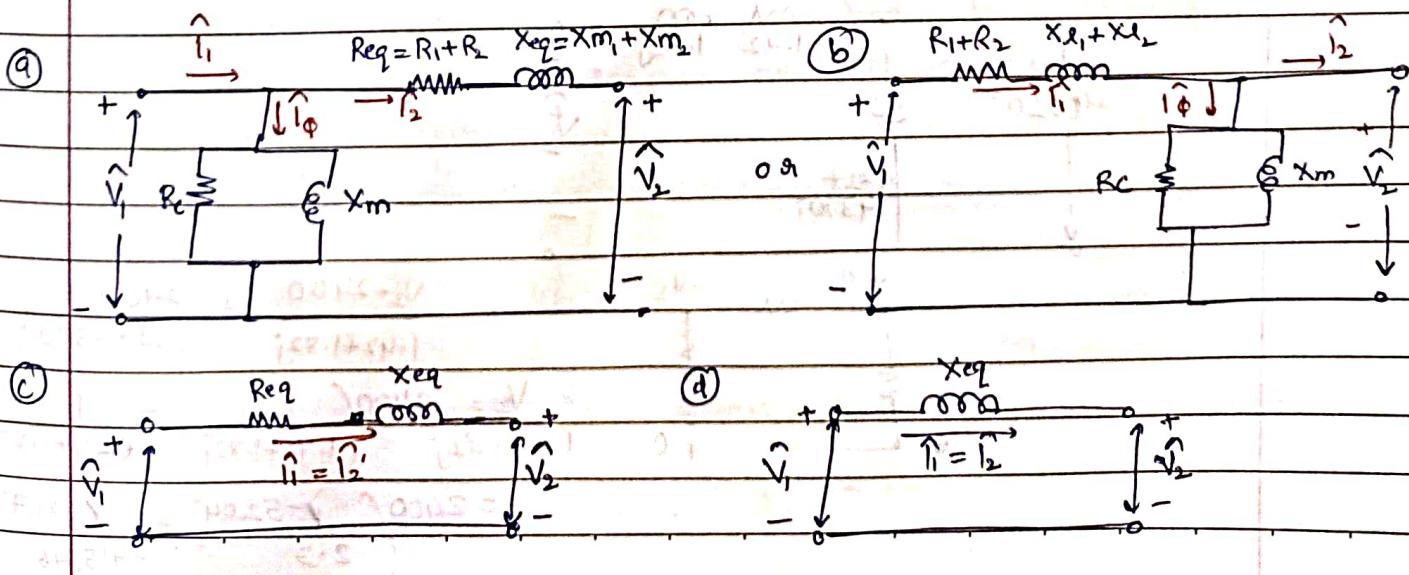

(a) and (b) → move exciting current out of middle to either the primary or secondary side  
 ↳ series resistance is the combined leakage reactance and resistance, referred on same side


e.g.- Use earlier data, Using LV terminal O.C. and 2400 V at the HV terminal, find voltage at LV using (a) and (b) equivalent circuits.

Ans.) (a) ⇒ referred on HV side

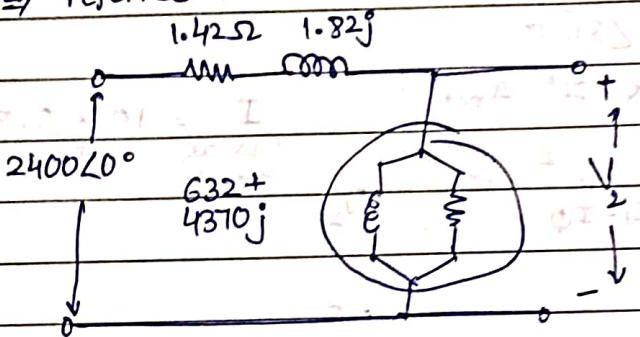

$$\begin{aligned}
 V_2 &= 2400 \\
 &\times ((1.42 + j1.82) + (632 + j4370)) \\
 &= 2400 \times (633.42 + j4371.82) \\
 &= 2400 \times 4415 \angle 81.7^\circ \\
 &= 4417.46 \angle 81.75^\circ \\
 &= [2398.66 \angle -0.05^\circ]
 \end{aligned}$$

(b) ⇒ referred on HV side

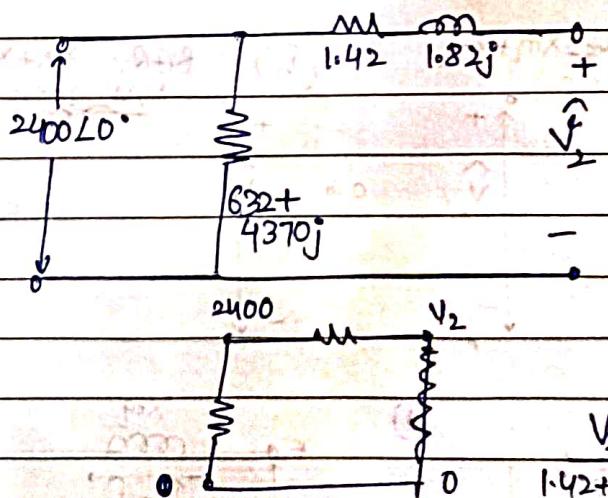

$$\begin{aligned}
 V_2 &= 2400 \left( \frac{1}{1.42 + j1.82} - \frac{1}{632 + j4370} \right) \\
 &= 2400 \left( \frac{1}{2.3} - \frac{1}{4415.46} \right) \\
 &= 2400 \left( \angle -52.04^\circ - \angle -31.7^\circ \right)
 \end{aligned}$$

$$\begin{aligned}
 V_2 &= 2400 \left( 1 - \frac{1.42 + j1.82}{632 + 4370j} \right) = 2400 \left( 1 - \frac{2.3 \angle 52^\circ}{4415.46 \angle 81.7^\circ} \right) \\
 &= 2400 \left( 1 - 5.2 \times 10^{-4} \angle -30^\circ \right) \\
 &= 2400 (0.9995 + j2.6 \times 10^{-4}) \\
 &= \boxed{2398.8 \angle 0.014^\circ}
 \end{aligned}$$

⇒ Some more approximations


↳ Neglect the exciting current (several hundred kVA or more)



also  $R_{eq}$  can be neglected w.r.t.  $X_{eq}$ .

⇒ in ideal cases → neglect everything.

⇒ Using ④ and ⑤ → we can determine  $R_{eq}$ ,  $X_{eq}$  using one single test ONLY → **SHORT-CIRCUIT ONE TERMINAL**

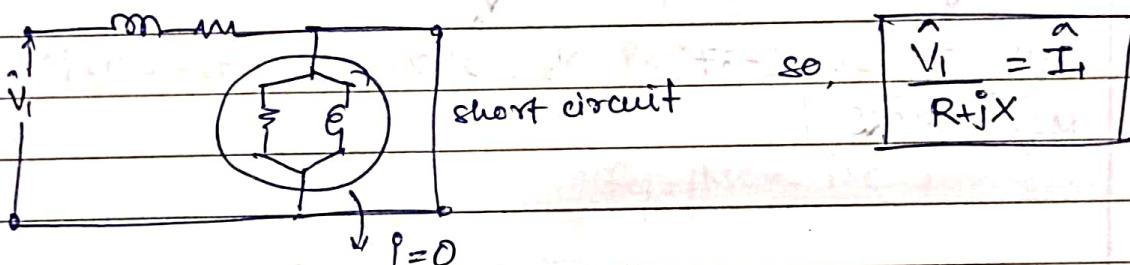


eg. 2.5) For same values as earlier eg., 50 kVA, 2400 - 240 V transformer is used to step-down voltage at load end of a feeder with  $Z = 0.3 + j1.6$ .  $V_{SRC}$  (leading end) = 2400 V

↳ Find voltage at secondary when load draws rated current from transformer at  $pf = 0.8$  lag.

(Neglect exciting current voltage drop).

∴

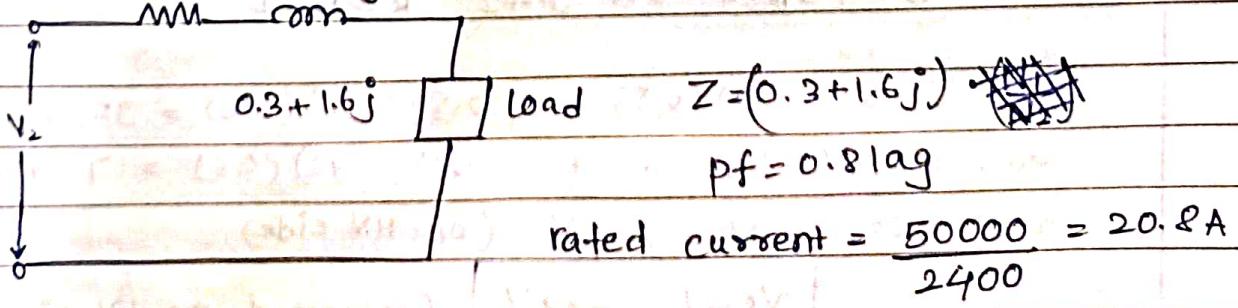

$$I_{load} = 20.8 \angle -37^\circ$$

$$pf = 0.8 \text{ lag}$$

$$\text{rated current} = \frac{50000}{2400} = 20.8 \text{ A}$$

$$I = 20.8 \angle -37^\circ \quad Z = 0.3 + 1.6j$$

$$V = IZ \Rightarrow (20.8 \angle -37^\circ)(0.3 + 1.6j) \angle -79.38^\circ$$

$$V = 33.904 \angle 42.38^\circ$$

$$(Z_{\text{load}}) \text{ on HV side} = (0.3 + 1.6j) \times 100$$

$$= 30 + 160j$$

$$I = 20.8 \angle -37^\circ$$

$$Z = 162.79 \angle 79.38^\circ$$

$$\therefore V =$$

$$P_2 \frac{1}{|V|^2}$$

$$|V|^2 = (50000 \angle 0^\circ) (1.62 \angle 79.38^\circ)$$

$$V = 235.29 \angle 79.38^\circ$$

$$\text{load current on HV side} = \frac{50000}{2400} = 20.8 \text{ A rms}$$

(rated)


$$\text{feeders + leakage} = 0.3 + 1.6j$$

$$+ (1.42 + 1.82j)$$

$$2400 \text{ V} \rightarrow I = 1.72 + 3.42j$$

$$M1) \quad I = 20.8 \angle -37^\circ \quad V_2 = 2400 - I(1.72 + 3.42j)$$

M2) **PHASORS**

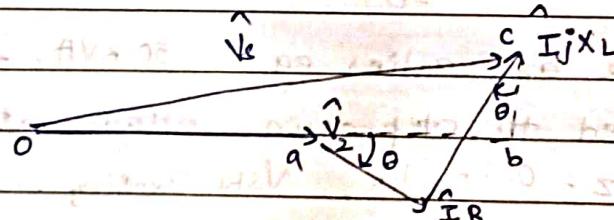

$$ob = \sqrt{V_2^2 - (bc)^2} \quad \text{and} \quad V_2 = 0.8b - ab$$

$$bc = IX \cos \theta - IR \sin \theta \quad ab = IR \cos \theta + IX \sin \theta$$

$$\theta = +37.87^\circ \quad X = 3.42 \quad R = 1.72$$


$$bc = (20.8)(3.42)(0.8) - (20.8)(1.72)(0.6) = 35.5V$$

$$ab = (20.8)(1.72)(0.8) + (20.8)(3.42)(0.6) = 71.4V$$

$$\text{and } \theta = 80^\circ, \quad V_2 = 233V \quad (\text{on HV side})$$

$$V_{\text{load}} = 233V \quad (\text{referred on LV side})$$

if pf = 0.8 leading

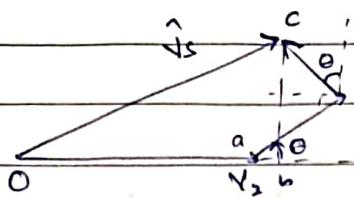

$$ab = IR \cos\theta - IX \sin\theta \quad \text{(exchange signs)}$$

$$bc = IX \cos\theta + IR \sin\theta \quad \text{(signs)}$$

$$Ob = \sqrt{V_s^2 - (bc)^2} \quad Ob = V_2 + ab$$


$$V_2 = Ob - ab$$

### SHORT-CIRCUIT TEST

Find  $R_{eq} + jX_{eq}$

→ short-circuit on the secondary and voltage applied on primary.

(referred on primary side)

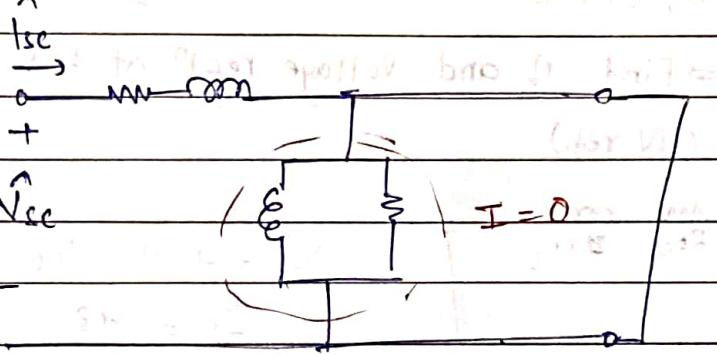

$$Z_{sc} = (R_1 + R_2) + j(X_1 + X_2) = R_{eq} + jX_{eq}$$

Instruments → measure  $V_{sc}$ ,  $I_{sc}$ ,  $P_{sc}$

$$|Z_{eq}| = |Z_{sc}| = N_{sc} \frac{|I_{sc}|}{|I_{sc}|}$$

$$R_{eq} = R_{sc} = \frac{P_{sc}}{I_{sc}^2}$$

$$X_{sc} = \sqrt{|Z_{sc}|^2 - R_{sc}^2}$$

and assume  $R_1 = R_2 = \frac{R_{eq}}{2}$  and  $X_1 = X_2 = \frac{X_{eq}}{2}$


(for all impedances referred on one side)

### OPEN CIRCUIT TEST

→ secondary open-circuited and rated voltage on primary.

LV SIDE (taken as primary)

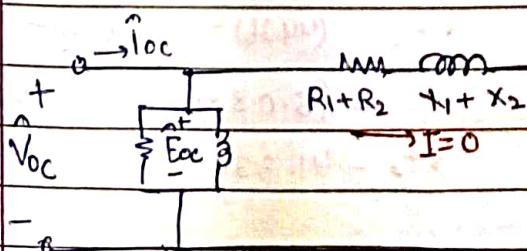magnetizing reactance will be operating at a flux level close to which will exist under normal operating conditions.



$$V_{oc} \approx E_{oc} \quad (\text{EMF induced by core flux})$$

$$I_{oc}^2 R_1 \rightarrow 0 \quad (\text{negligible loss due to exciting current})$$

$$P_{oc} = \frac{E_{oc}^2}{R_c} \quad Z_{oc} = \frac{R_c(jX_m)}{(R_c + jX_m)}$$

$$R_c = \frac{V_{oc}}{I_{oc}} \quad |Z_{op}| = \frac{|V_{oc}|}{|I_{oc}|} \quad X_m = \frac{1}{\sqrt{\left(\frac{1}{|Z_{op}|}\right)^2 - \left(\frac{1}{R_c}\right)^2}}$$

eg.- LV side short-circuited, instruments on the HV side open-circuit test, LV side energized, readings on LV side  
 48V, 20.8A, 617W 240V, 5.41A, 186W

⇒ Find  $\eta$  and voltage reg'n at full load, 0.8 pf lag.

Ans) S.C. test (HV ref.)

$R_{eq}$   $X_{eq}$

$$V_{sc} = 48V \quad I_{sc} = 20.8A$$

$$Z_{sc} = \frac{48}{20.8} = 2.31 \Omega$$

$$P = |I|^2 R_{eq} \quad R_{eq} = \frac{617}{(20.8)^2} = 1.43 \Omega$$

$$X_{eq} = 1.81 \Omega$$

O.C. test (LV ref.)

$$V_{oc} = 240 \quad I_{oc} = 5.41A \quad P = 186W$$

$$|Z| = \frac{240}{5.41} = 44.36$$

$$P = I_{oc}^2 R_{oc}$$

$$R_{oc} = 186 = 6.36 \Omega \quad (\text{LV})$$


$$X_m = 6.42 \Omega \quad (\text{LV})$$

$$|Z|^2 = \frac{1}{R^2} + \frac{1}{X^2}$$

$$\frac{1}{X^2} = \frac{1}{(44.36)^2} - \frac{1}{(6.36)^2}$$

$$= (5.08 \times 10^{-4}) - (0.0247)$$

$$X^2 = -41.336$$

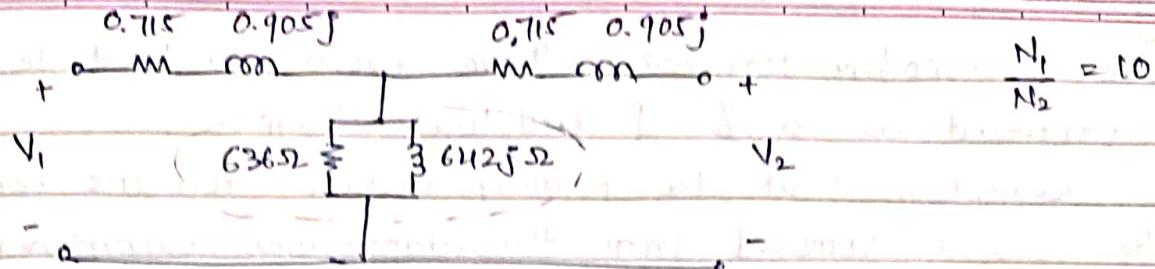

load at full-rated power = 50 kVA at 0.8 pf lag

$$V_2 = 2400 \angle 0^\circ \text{ (scaled up)}$$

$$10^3 \times 50 / \sqrt{3} = 2400 \angle 0^\circ I^*$$

$$\boxed{I = 20.8 \angle -37^\circ \text{ rated}} \quad (\Delta I \text{ ignored})$$

$$V_1 - (1.43 + j1.81)(20.8 \angle -37^\circ) = 2400$$

$$\begin{aligned} V_1 &= 2400 + (2.3 \times 20.8) \angle 51.69 - 37^\circ \\ &= 2400 + 47.84 \angle 14.69^\circ \\ &= 2400 + 46.27 + j12.13 \end{aligned}$$

$$V_1 = 2446.27 + j12.13 = 2446.3 \angle 4.9 \times 10^{-3}^\circ$$

$$\boxed{V_1 = 2446.3 \text{ V}}$$

$$\text{Voltage regulation} = \left( \frac{2446.3 - 2400}{2400} \right) \times 100 = 1.93\%$$

$$\text{efficiency} = \left( \frac{2400}{2446.3} \right) \times 100 = 98.11\%$$

M2 "shorter"

$$\text{From S.C. test} \Rightarrow |Z_{eq, H}| = \frac{48}{20.8} = 2.31 \Omega \quad R_{eq, H} = \frac{617}{20.8^2} = 1.42 \Omega$$

$$X_{eq, H} = 1.82 \Omega$$

at full-load operation,

$$I_H = \frac{50000}{2400} = 20.8 \text{ A}$$

$$P_{output} = P_{load} = (0.8) 50000 = 40,000 \text{ W}$$

$$P_{output} = (coce) P_{full}$$

$$P_{winding} = I_H^2 R_{eq, H} = 617 \text{ W}$$

$$P_{winding} = P_{sc}$$

$$\text{core loss, from O-C test} \Rightarrow P_{core} = 186 \text{ W}$$

$$P_{core-loss} = P_{oc}$$

$$P_{loss} = P_{sc} + P_{oc} = 803 \text{ W} \Rightarrow P_{input} = P_{output} + P_{loss}$$

$$\boxed{\text{efficiency} = \left( \frac{P_{out}}{P_{out} + P_{sc} + P_{oc}} \right) \times 100 \%}$$

## Regulation

- change in secondary terminal voltage from no-load to full-load and expressed as a % of full-load voltage
- under assumption that the primary voltage remains constant as the load is removed from the transformer secondary.


$$\text{Regulation} = \left( \frac{|V|_{FL} - |V|_{NL}}{|V|_{NL}} \right) \times 100$$

↓  
(same as rated)


(Rated + IZ)
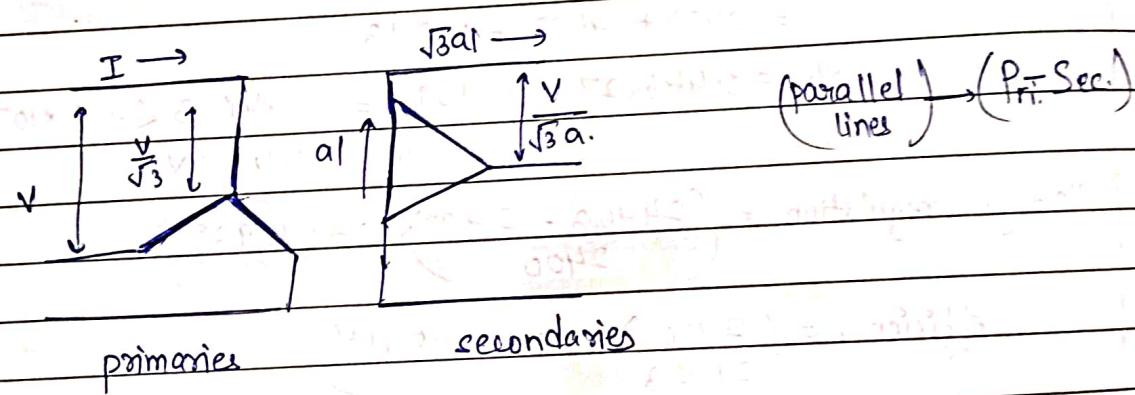
## THREE-PHASE TRANSFORMERS


- connect 3 single-phase transformer  
(Y-Δ Δ-Δ Y-Y Δ-Y)



- core-type and shell-type

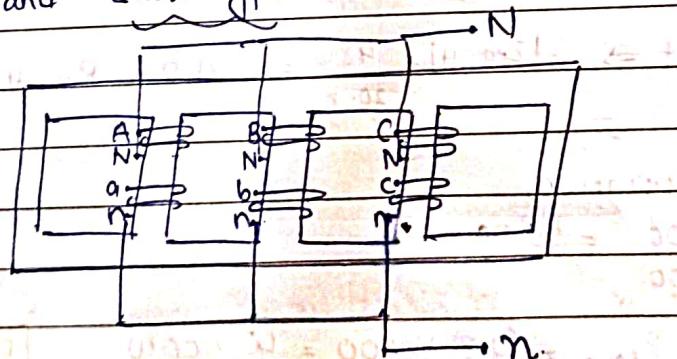

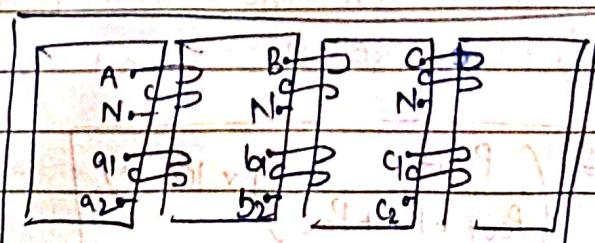
windings in the same side of the core are in the same phase




$V_{AN} \rightarrow V_{a_1 a_2}$  $V_{BN} \rightarrow V_{b_1 b_2}$  $V_{CN} \rightarrow V_{c_1 c_2}$ 

$$\text{in } Y : V_{LL} = V_{LN} \sqrt{3} \angle 30^\circ ; I_{LL} = I_\phi$$
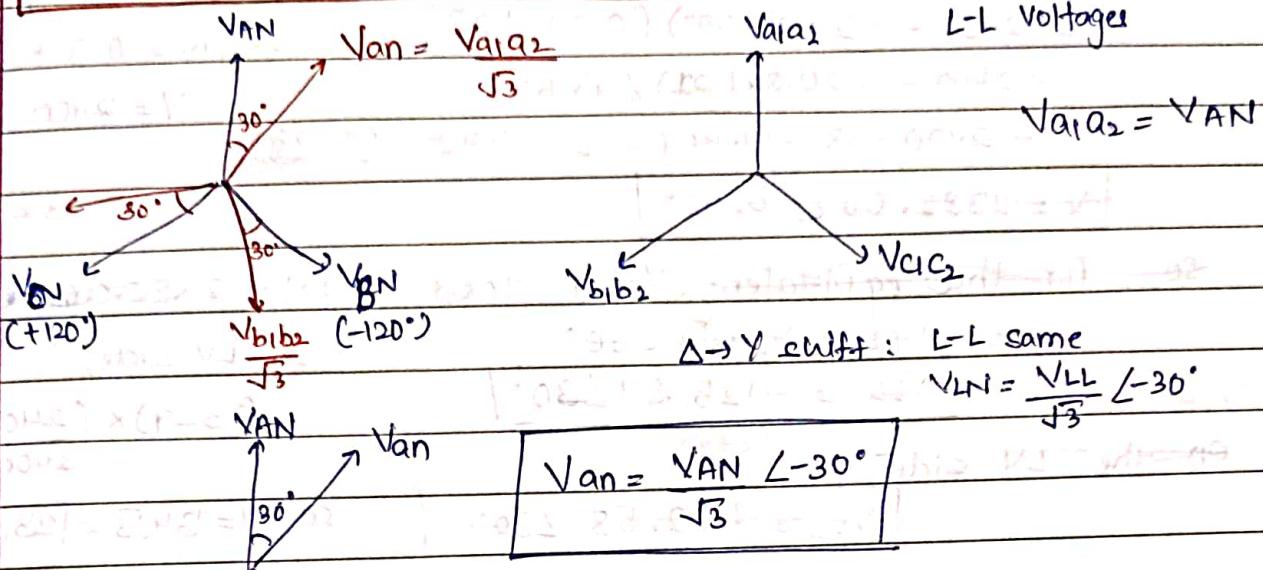
$$\text{in } \Delta : V_{LL} = V_\phi \angle 0^\circ ; I_{LL} = I_\phi \sqrt{3} \angle -30^\circ$$



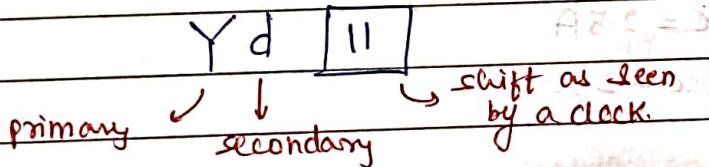
if  $N_{a_1 a_2} = N_{AN} \Rightarrow V_{AN} = V_{a_1 a_2}$  i.e.  $V_{AN} = \sqrt{3} V_{an} \angle 30^\circ$



e.g.- 3 single-phase 50 KVA 2400-240 V transformers,  $Y-\Delta$  connected;  
 3 phase 150 KVA step-down bank to step down voltage at load end of a feeder whose  $Z = 0.15 + j1.00 \Omega/\text{phase}$ .  
 Voltage at sending end is 4160 L-L. on secondary side, the transformer supply a balanced load through a feeder with  $Z = 0.0005 + j0.0020 \Omega/\text{phase}$ . Find L-L voltage at load end when load draws rated current from transformer at  $\text{pf} = 0.8$  lag.

Ans.) Single-phase; HV side.
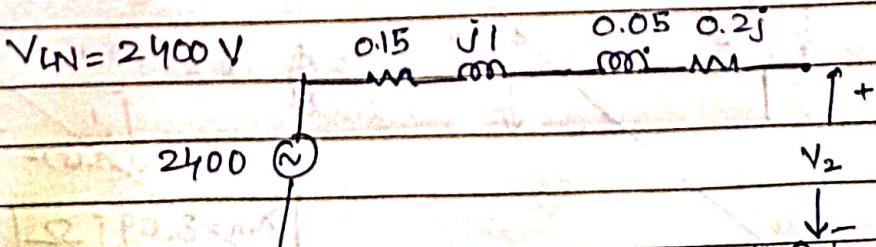
$$V_{LL} = 4160 \angle 0^\circ \quad V_{LN} = 4160 \angle 0^\circ \quad \frac{1}{\sqrt{3}}$$



at load end  $\Rightarrow$  full load,  $\text{pf} = 0.8$

rated current on HV side  $= \frac{50 \times 10^3}{100} = 500 \text{ A}$

$\therefore$  rated current  $= \frac{50000}{2400} = 20.8 \angle -37^\circ$

LV feeders impedance on HV side  $= \left( \frac{2400}{240\sqrt{3}} \right)^2 (0.0005 + j0.001) = 0.15 + j0.60 \Omega$

$\therefore V = 2400 - (20.8 \angle -37^\circ) (0.15 + j0.60)$

$= 2400 - (20.8 \angle -21^\circ) \angle 43.5^\circ$

$= 2400 - 18 - 17.46j = 2382 - 17.46j$

$\therefore V = 2382.06 \angle -0.42^\circ$

so, for the equivalent  $\gamma$  on load,  $V_{LN} = 2382.06 \angle 10^\circ$

so,  $V_{LL} = V_{LN}\sqrt{3} \angle 30^\circ$

$\therefore V_{LL} = 4125.84 \angle 30^\circ$

on LV side,

$(2329) \times \left( \frac{240}{2400\sqrt{3}} \right) = 12 \Omega$

on the LV side,

$\therefore V_{LL} = 412.58 \angle 30^\circ$

so,  $V = 134\sqrt{3} = 233V$

line-to-line

e.g.  
for and  
(sc Test)

20 kVA, 8000/240 V, 60 Hz

$V_{OC} = 240V$

$V_{SC} = 489V$

$I_{OC} = 7.133A$


$I_{SC} = 2.5A$

$P_{OC} = 400W$

$P_{SC} = 240W$

A)

short  
open-circuit Test. (LV side).

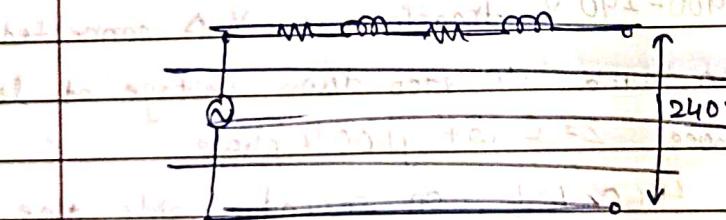

$Z_{ll} = \frac{V_{ll}}{I_{ll}} = 33.65 \Omega$

$\frac{400}{(7.133)^2} = R_{ll} = 7.87 \Omega$

$(33.65)^2 = (7.87)^2 + (X_{ll})^2 \quad (X_{ll}) = 32.71 \Omega$

B Open-circuit Test

(HV side)


$Z_{OC} = 33.65 \Omega$

$R_{OC} = \frac{400}{(7.133)^2} = 7.87 \Omega$

$X = \frac{1}{(33.65)^2} - \frac{1}{(7.87)^2}$

$X_m = 8.09 \Omega$

### Open-circuit test

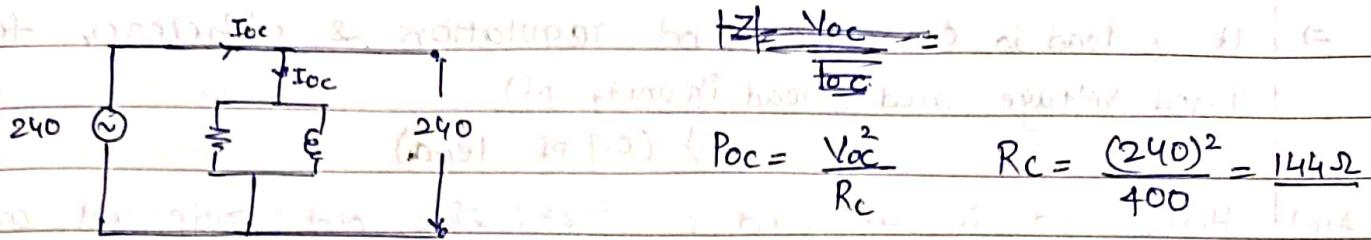

$$P_{oc} = \frac{V_{oc}^2}{R_C} \quad R_C = \frac{(240)^2}{400} = 144\Omega$$


$$Z_{oc} = \frac{(R)(jX)}{(R+jX)} = \frac{V_{oc}}{I_{oc}}$$

$$|Z_{oc}| = \frac{|V_{oc}|}{|I_{oc}|} = 33.65\Omega$$

$$\frac{1}{Z} = \frac{1}{R} - \frac{j}{X} \quad \left| \frac{1}{Z} \right|^2 = \sqrt{\frac{1}{R^2} + \frac{1}{X^2}}$$

$$\frac{1}{(33.65)^2} = \frac{1}{(144)^2} + \frac{1}{X^2} \Rightarrow X = 34.63\Omega$$

### Short-circuit Test

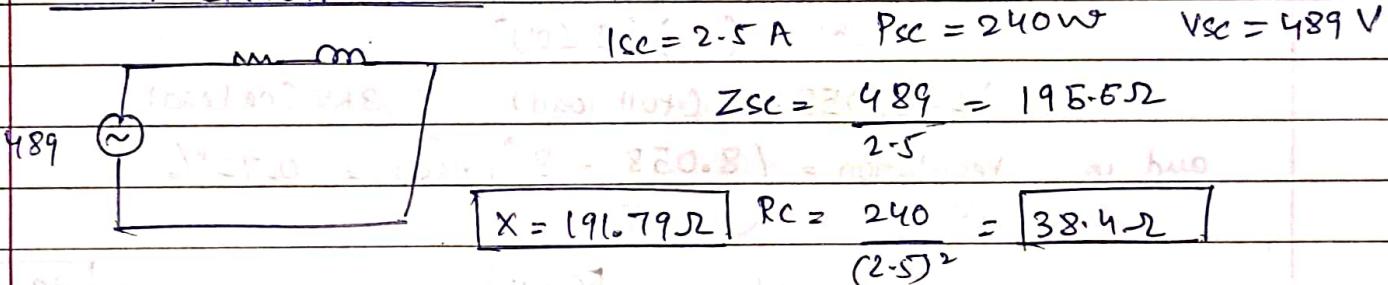

$$Z_{sc} = \frac{V_{sc}}{I_{sc}} = \frac{489}{2.5} = 195.6\Omega$$

$$X = 195.6\Omega \quad R_C = \frac{240}{(2.5)^2} = 38.4\Omega$$

e.g. The nameplate on a 50 MVA, 60 Hz single-phase transformer indicates that it has a voltage rating 8 KV : 78 KV.

Open-circuit test  $\rightarrow$  8 KV, 62.1 A, 206 KW (LV side)

short-circuit test  $\rightarrow$  674 V, 6.25 KA, 187 KW (LV side)

Ans.)

s.c.  $|Z_{eq, LV}| = \frac{|V_{sc, L}|}{|I_{sc, L}|} = 107.8 \text{ m}\Omega \quad X_{eq, LV} = \sqrt{Z_{LV}^2 - R_{LV}^2} = 107.7 \text{ m}\Omega$

~~Psc~~  $|R_{eq, LV}| = \frac{P_{sc}}{I_{sc}^2} = 4.78 \text{ m}\Omega \quad (Z_{eq})_{LV} = (4.8 + 108j) \text{ m}\Omega$

~~Psc~~  $|I_{sc}|^2$

~~Psc~~  $R_{C, LV} = \frac{V_{oc}^2}{P_{oc}} = 311\Omega \quad Z = V_{oc}i = 128.82\Omega$

~~Psc~~  $P_{oc} = I_{oc}^2 R_C$


~~Psc~~  $X_m = 90^\circ \text{ reactance angle} = 141.5^\circ \text{ (approximate value)}$

~~Psc~~  $\sqrt{\left(\frac{1}{Z}\right)^2 - \left(\frac{1}{R}\right)^2} = \sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_m}\right)^2}$

⇒ If a load is connected, find regulation & efficiency for rated voltage and load (unity pf)

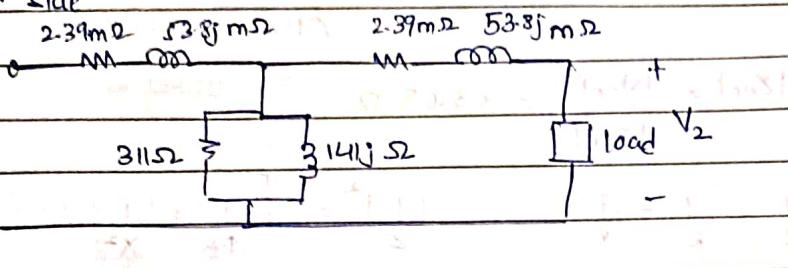ii) (0.9 pf load)

Ans) Here, load is connected on 78 KV side but referred on the 8 KV side.



$$\text{rated Low-voltage current, } I_{\text{rated}} = \frac{50 \times 10^6}{8 \times 10^3} = 6.25 \text{ KA}$$

$$\text{and so, } V_L = |V_{\text{load}} + Z_{\text{eq}, L} \cdot I_{\text{rated}}| = 8 \text{ KV} + ( ) (I \angle 0^\circ)$$

$$V_L = 8.058 \text{ KV (full load)} \quad 8 \text{ KV (no load)}$$

$$\text{and so, regulation} = \left( \frac{8.058 - 8}{8} \right) \times 100 = 0.72\%$$

$$\gamma_{\text{eff.}} = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{50 \times 10^6}{50 \times 10^6 + (187 + 206) \times 10^3} = 99.2\%$$

$$\Rightarrow (ii) I_2 = 6.25 \angle 25.8^\circ$$

### 3-PHASE TRANSFORMERS


⇒ carry out computations on a single-phase (per-phase Y, L-N) basis

$$Z_Y = \frac{1}{3} Z_\Delta$$

e.g.) The 3 phase-transformer of earlier example are A-A connected and supplied with 2400 V (line-to-line) 3-phase feeder with reactance 0.8052/phase. At its sending end, it is connected to the secondary terminals of a 3-phase Y-Δ transformer with rating 500 kVA, 24 KV : 2400 V (line-to-line). The equivalent impedance of the sending-end transformer is 0.17 + j0.92 Ω/phase referred on 2400 V side. The voltage at primary terminals of sending-end transformer is 24 KV (line-to-line).

A 3-phase short circuit occurs at the 240V receiving-end terminals of the 2400V receiving-end transformers. Find

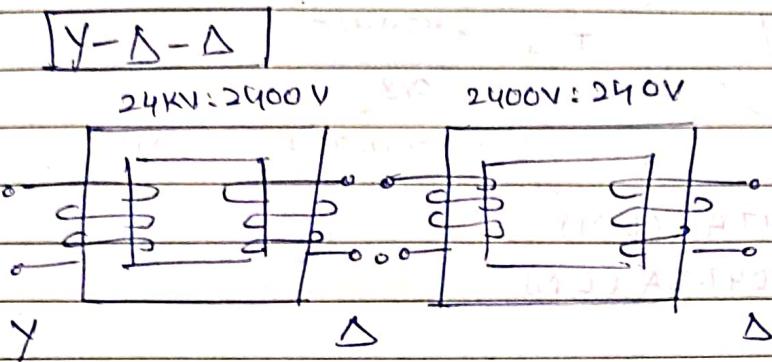- i) steady-state 1sc in 2400V feeder phase wires, primary and secondary windings of receiver-end transformers and at the 240-V terminals.




i)  $Y - \Delta$  transformer

on the 24kV ( $L-L$ ) side,

$$Z = \left( \frac{24 \times 10^3}{24 \times 10^3} \right)^2 (0.17 + 0.92j) \Omega/\text{phase}$$


$$Z = (17 + 92j) \Omega$$
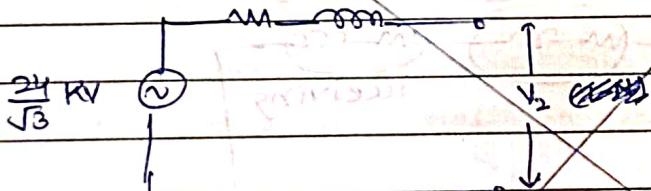
$$I_{\text{rated}} = \frac{500 \times 10^3}{24 \times 10^3} = 20.8 \text{ A}$$



$$I = \frac{V_2'}{0.8j}$$

short circuit  
on 240V  
side

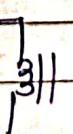

short circuit

For the  $\Delta - \Delta$  transformer,

$$I = \frac{V}{0.8j}$$

current has  
a phase of  
 $90^\circ$

$$\text{so, } V'(L-L) = 10V \quad I'(L-L) = \frac{V}{0.8j}$$


$$V'(L-N) = \frac{10V}{\sqrt{3}}$$

$$I'(L-N) = \frac{V}{0.8j}$$

$$\frac{10^3 \times 24}{\sqrt{3}} - (20.81)(17 + 92j) = 13502.81 + -j1913.6 \\ = 13637.73 \angle 8.02^\circ$$

$$\sqrt{2}(L-L) = 13637\sqrt{3}$$


$V_2 = 2362.14 \text{ V}$  | input to the second transformer  
(L-L)

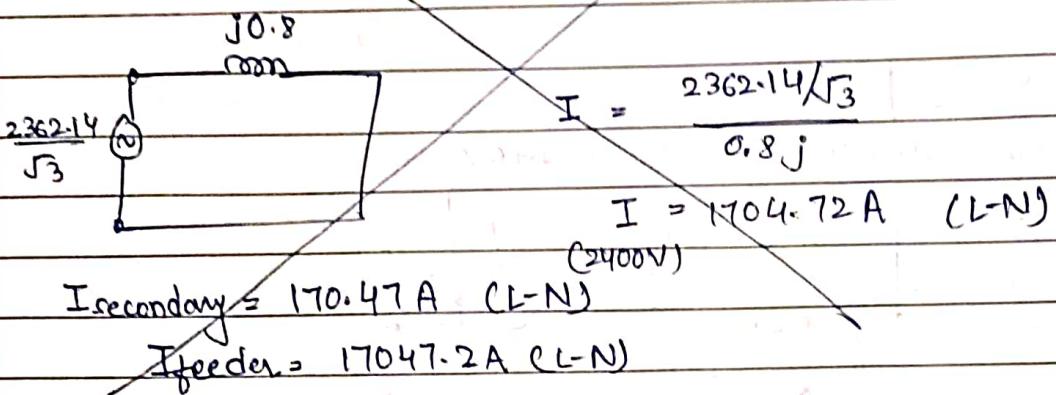
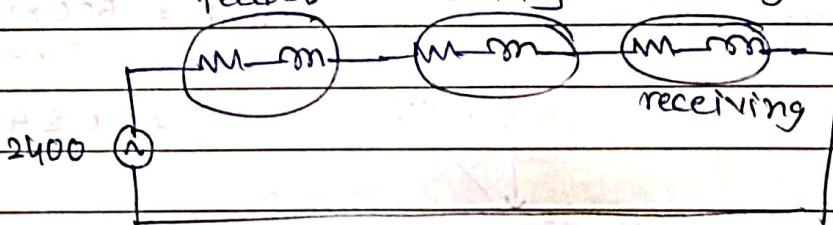
# all references to  $2400 \text{ V side}$

$$\text{source voltage} = 2400 \text{ (LN)} = \frac{13637.73}{\sqrt{3}} \text{ V}$$

single-phase equivalent  $\Delta-\Delta$  has  $Z = 1.42 + j1.82 = 0.47 + j0.61 \Omega$



$$\text{so, } Z = (0.47 + 0.61j) + (0.8j) + (0.17 + 0.92j) \\ = 0.64 + 2.33j$$

$$|Z| = 2.42 \Omega/\text{phase}$$

$$\text{in } 2400 \text{ V branch (feeder)} \quad I = \frac{2400}{\sqrt{3}} = 572 \text{ A}$$

$$2.42$$


$$\text{so, receiving-end winding current} = \frac{572}{\sqrt{3}} = 330 \text{ A}$$

Amperes

$$\text{and in } 240 \text{ V winding} = 330 \text{ A}$$

$$\text{phase current} = 330\sqrt{3} = 572 \text{ A}$$

M	T	W	T	F	S	S
Page No.:	YOUVA					
Date:						

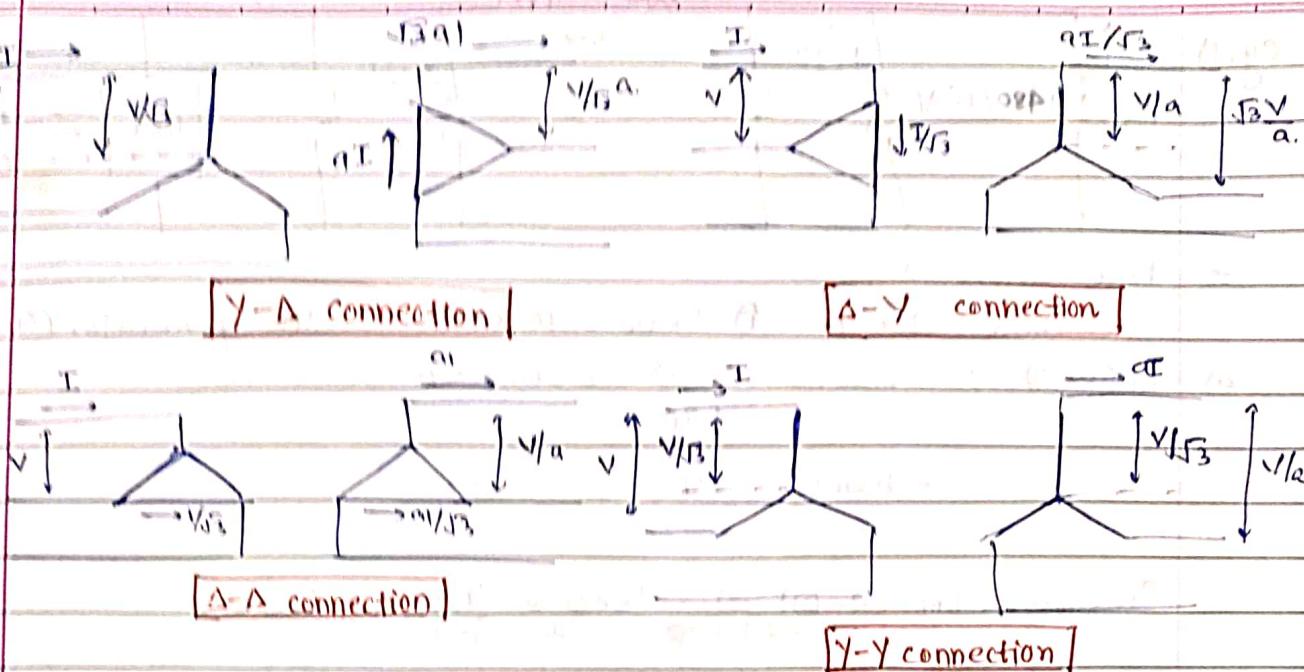

### PER-UNIT SYSTEM

- No need for explicit voltage-level conversions at every transformer in the system.
- per unit (pu) system of measurements.

- $\text{Quantity per unit} = \frac{\text{Actual value}}{\text{Base value of quantity}}$  → Value in V, Amp, etc.
- select ② base quantities to define a given p.u. system  
Voltage → power (or apparent power)

Single phase  $\Rightarrow S_{base} = V_{base} I_{base}$  ( $P_{base}, Q_{base}$  or  $S_{base}$ )


$$Z_{base} = \frac{V_{base}}{I_{base}} \quad (R_{base}, X_{base} \text{ or } Z_{base})$$

$$Y_{base} = \frac{I_{base}}{V_{base}} \quad Z_{base} = \frac{(V_{base})^2}{S_{base}}$$

- A base apparent power and voltage are selected at a specific point in the system.
- Transformer has no effect on the base apparent power of the system, since  $S_{in} = S_{out}$ ,  $V_{base}$  changes acc. to trans. ratio.

R-(I)

R-(II)

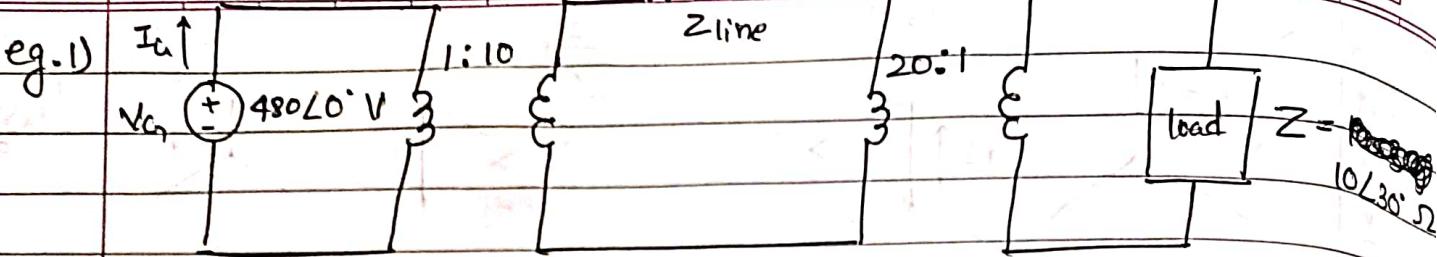I<sub>load</sub> $\Rightarrow$  base values  $\rightarrow$ 

$$V_{base} = 480 V \quad S_{base} = 10 \text{ kVA} \text{ at the generator (G)}_1$$

a)  $G_1 (R-1) \Rightarrow I_{base1} = \frac{10 \times 10^3}{480} = 20.83 A$

$$Z_{base1} = \frac{480}{20.83} = 23.04 \Omega$$

Transmission line (R-2)  $\Rightarrow V_{base2} = \frac{480}{2} = 240 V$

$$S_{base2} = \frac{10}{2} \text{ kVA (same)}$$


$$I_{base2} = 2.083 A \quad Z_{base2} = 230.4 \Omega$$

Load (R-3)  $\Rightarrow V_{base3} = \frac{4800}{20} = 240 V \quad S = 10 \text{ kVA}$

$$I_{base3} = 41.67 A \quad Z_{base3} = 5.76 \Omega$$
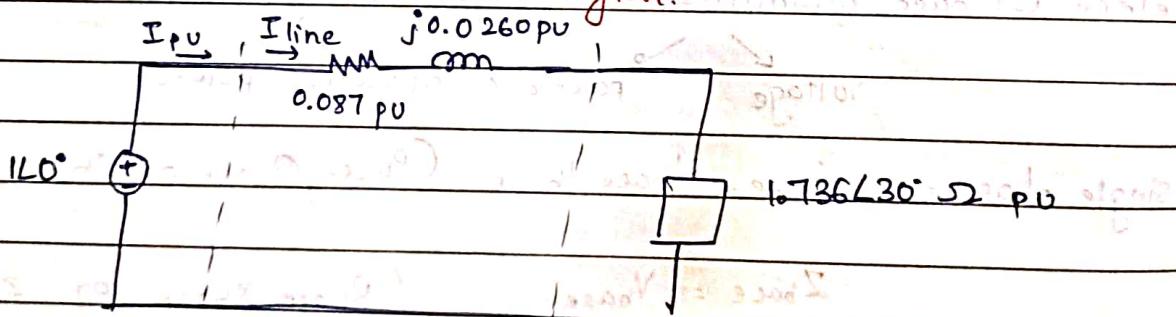
### CONVERTING TO PER-UNIT EQUIVALENT SYSTEM

divide each component by its base value in that region.



$$I_{G1,pu} = I_{line,pu} = I_{load,pu} = I_{pu}$$

$\Rightarrow$  Now,  $I_{pu} = 1.00^\circ$

$$(0.087 + 0.0260j) + (1.503 + j0.868)$$

$$I_{pu} = 0.569 \angle -30.6^\circ \text{ pu}$$

so,  $I_{load} = I_{load,pu} \times I_{base3} = (0.569 \times 41.67) \angle -30^\circ$

$$P_{pu,load} = I_{pu}^2 / R = (0.569)^2 \times (1.503) = 0.487$$


$$\text{so, } P_{\text{load}} = P_{\text{pu}} \times S_{\text{base3}} = 4870 \text{ W}$$

d) Per unit power lost in transmission line =  $(0.569)^2 \times 0.087$

$$\text{so, } P = 0.00282 \times 10 \times 10^3 = 28.2 \text{ W}$$

⇒ If more than one machine and one transformer are included in a single power system, the base can be chosen arbitrarily BUT the entire system must have the same base.
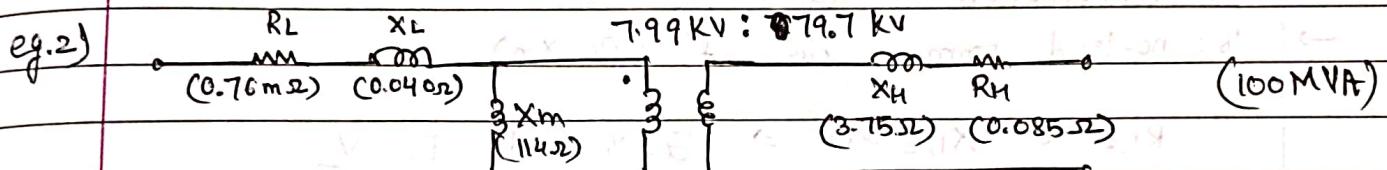
$$(P, Q, S)_{\text{pu on base-2}} = (P, Q, S)_{\text{pu on base1}} \times \frac{S_{\text{base1}}}{S_{\text{base2}}}$$



LV side and HV side

$$S_{\text{base}} = 100 \text{ MVA}$$

$$V_{\text{base}} = 7.99 \text{ KV}$$

$$V_{\text{base}} = 79.7 \text{ KV}$$

$$I_{\text{base}} = \frac{100 \text{ MVA}}{7.99 \text{ KV}} = 12515.65 \text{ A}$$

$$Z_{\text{base}} = \frac{(79.7)^2}{100} = 635 \Omega$$

$$Z_{\text{base}} = \frac{(7.99)^2}{100 \text{ MVA}} = 0.635 \Omega$$

$$R_L \rightarrow 0.0012 \text{ pu} \quad X_L \rightarrow 0.063 \text{ pu} \quad X_m = 179.53 \text{ pu}$$


$$X_H \rightarrow 0.06 \text{ pu} \quad R_H \rightarrow 0.0013 \text{ pu}$$

per-unit turns ratio =  $\left( \frac{7.97}{79.7} \right) : \left( \frac{79.9}{79.9} \right) = 1:1$

$\downarrow V_{\text{base}}$

(no need of transformer in b/w)

## PHASORS

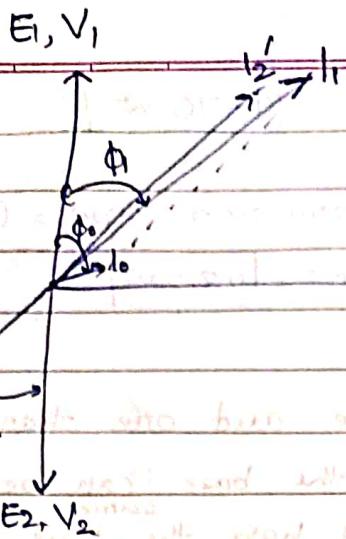


- mutual flux  $\phi$  taken as reference phasor
- EMF  $E_1$  induced in primary leads  $\phi$  by  $90^\circ$ ,  $E_2$  drawn on for convenience
- $I_0$ : no-load primary current ( $R_c, X_m$ )
- (AIM 2001)
- $R_{1,2} \approx 0, X_{1,2} \approx 0 \Rightarrow E_1 = V_1$  and  $E_2 = V_2$
- load impedance on secondary is lagging by  $\cos(\phi_2)$   
i.e.  $Z_L = |Z_L| \angle \phi_2$
- (b) → secondary current on primary side  
 $I_1 = I_0 + I_2'$  → total current → lags  $V_1$  by  $\phi_1$
- ⇒ including  $R_2$  and  $X_{12}$   

$$V_2 = E_2 - I_2 Z_2 = E_2 - I_2 R_2 - I_2 j X_{12}$$

$$\Rightarrow E_2 = V_2 + I_2 R_2 + I_2 j X_{12}$$

$$V_1 = E_1 + I_1 R_1 + I_1 j X_1$$

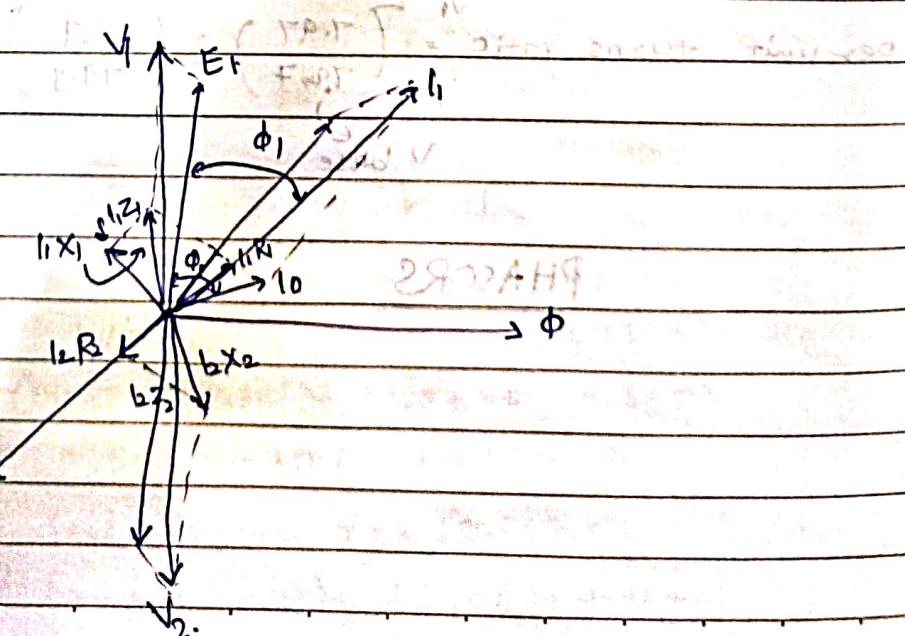

M	T	W	T	F	S
Page No.:					YOUVA
Date:					

also, voltage regulation =  $\frac{I_1 (\text{Reg} \cos \phi_2 + X_{\text{eq}} \sin \phi_2)}{V_1}$

(load with lagging pf, cos  $\phi_2$ )

=  $I_1 (\text{Reg} \cos \phi_2 - X_{\text{eq}} \sin \phi_2)$  (leading pf)  $\frac{V_1^2 (1 + I_2^2)}{V_1^2 (1 + I_2^2) + I_2^2 R_{\text{eq}} \cos \phi_2}$

### MAXIMUM CORE EFFICIENCY

DEFINITION AND FORMULAE OF MAX. EFF.

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{V_2 I_2 \times \text{pf}}{V_2 I_2 \times \text{pf} + P_c + I_2^2 R_{\text{eq}}}$$

$$= V_2 \cos \phi$$

$$V_2 \cos \phi + \frac{P_c + I_2^2 R_{\text{eq}}}{I_2} = \text{constant}$$

$$\frac{d}{dI_2} (V_2 \cos \phi + \frac{P_c + I_2^2 R_{\text{eq}}}{I_2}) = 0$$

$$\Rightarrow -\frac{P_c}{I_2} + \frac{R_{\text{eq}}}{I_2^2} = 0 \quad \text{i.e. } P_c = I_2^2 R_{\text{eq}}$$

max. efficiency when variable power due to core loss = constant

$$(P_{\text{out}} - \text{loss}) = (P_{\text{in}} + I^2 R) \quad (\text{H + E.C.})$$

"constant" factor will remain same in all cases

condition holds true for all types of cores & conditions

number of ampere turns remains constant

current flowing through coil

$$(A \times V + B) \times I = C$$

$$T = \frac{C}{A \times I^2}$$

$$T = \frac{C}{(B + V)^2}$$

$$T = \frac{C}{(B + V)^2} \quad \text{current flowing through coil}$$