

Q.1

$$v = 100 \cos(240\pi t + 45^\circ) \text{ mV.}$$

$$1) \quad \omega = 240\pi = 754 \text{ rad/sec.}$$

$$f = \frac{\omega}{2\pi} = 120 \text{ Hz}$$

$$T = 8.33 \text{ msec.}$$

$$2) \quad T = 8.33 \text{ msec. } (T = 1/f)$$

$$3) \quad v_m = 100 \text{ volts.}$$

$$4) \quad v(0) = 100 \cos(240\pi \times 0 + 45^\circ)$$

$$= 100 \cos 45^\circ$$

$$v(0) = 50\sqrt{2} \text{ mV.}$$

$$5) \quad \phi = 45^\circ$$

$$\phi = 45 \times \frac{\pi}{180} = \pi/4 \text{ radian.}$$

6) Smallest positive value of  $t$  at which  $v=0$

$$0 = 100 \cos(240\pi t + 45^\circ)$$

$$\cos^{-1} 0 = 240\pi t + 45^\circ$$

$$90^\circ = 240\pi t + 45^\circ$$

$$t = \frac{45^\circ}{240\pi}$$

$$t = \frac{45 \times \pi}{240 \times 180} = 1.041 \text{ msec.}$$

7) Smallest positive value of  $t$  at which  $dv/dt = 0$

$$\frac{dv}{dt} = -100 \sin(240\pi t + 45^\circ) 240\pi$$

$$0 = -100 \sin(240\pi t + 45^\circ) 240\pi$$

$$\sin^{-1} 0 = 240\pi t + 45^\circ$$


$$0 = 240\pi t + 45^\circ$$

$$t = \frac{45 \times \pi}{240\pi \times 180}$$

$$t = -1.04 \text{ msec.}$$

Ans.

Q.2.

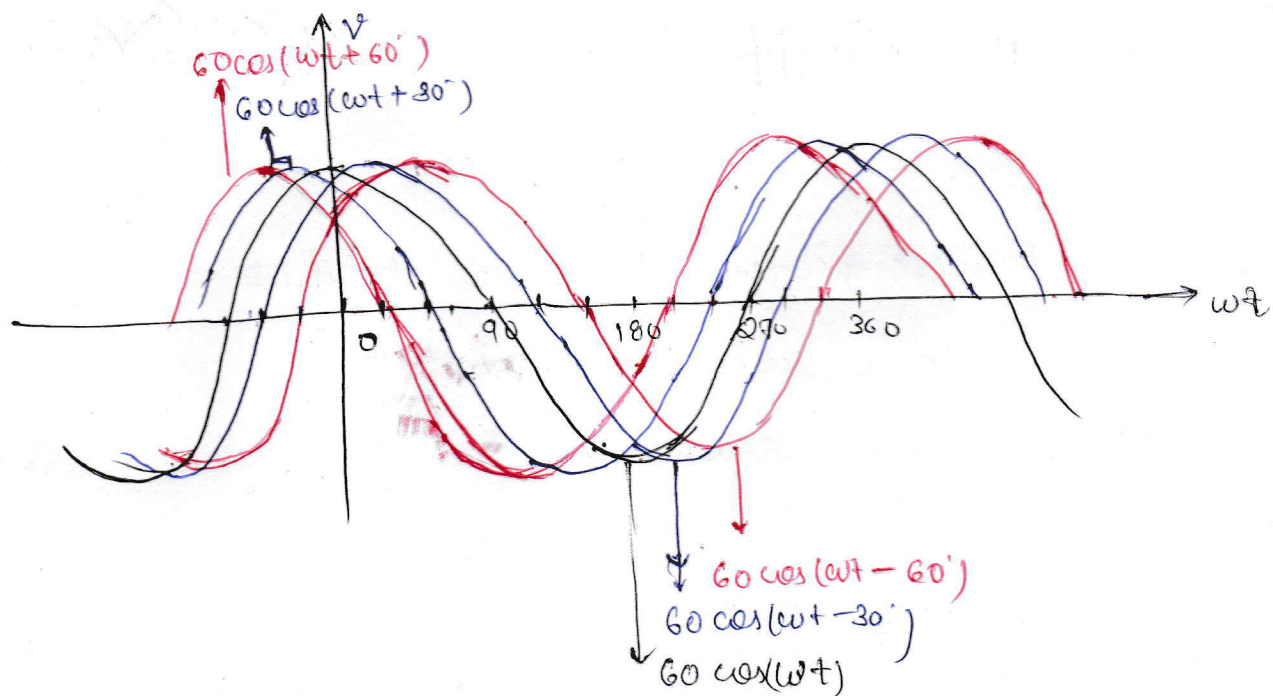

- a) Voltage function is shifting to the left as  $\phi$  becomes more +ve.
- b) Direction of shift will towards right if  $\phi$  changes from 0 to  $-30^\circ$ .

Q.3

$$v(t) = 170 \cos(120\pi t - 60^\circ) \text{ V}$$

1)  $v_m = 170$

2) frequency in Hz  $\rightarrow$

$$\omega = 120\pi$$

$$f = \frac{\omega}{2\pi}$$

$$= \frac{120\pi}{2\pi} = 60 \text{ Hz.}$$

3) frequency in radian per sec.

$$\omega = 120\pi = 377 \text{ rad/sec.}$$

4) Phase angle in radians

$$\phi = 60^\circ \Rightarrow \frac{60 \times \pi}{180}$$

$$= \pi/3 \text{ radian.}$$

5) Phase angle in degree

$$\phi = 60^\circ$$

6) Period  $T = 1/f = 16.67 \text{ msec.}$

7) The first time after  $t=0$  that  $v = 170 \text{ V.}$

$$\Rightarrow \text{after } 16.67 \text{ msec.}$$

8) Sinusoidal function is shifted right by  $125/18 \text{ ms.}$

$$\phi/\omega = \frac{125}{18} \times 10^{-3}$$

$$\phi = \frac{125}{18} \times 10^{-3} \times 120\pi \times \frac{180}{\pi}$$

$$= 150^\circ$$

Expression for  $v = 170 \cos(120\pi t - 60 - 150)$

$$v = 170 \cos(120\pi t - 210^\circ) \text{ V.}$$

9)  $v(t) = 170 \sin(120\pi t)$

$$= 170 \cos(120\pi t - 90^\circ)$$

Means  $+90^\circ$  shift is require.

$$t = \frac{90 \times \pi}{120\pi \times 180} = 1.388 \text{ msec.}$$

10)  $v(t) = 170 \cos 120\pi t$

-  $60^\circ$  shift is require

$$t = \frac{60 \times \pi}{120\pi \times 180} = 2.77 \text{ msec.}$$

$$Q.4 \quad a) \quad y = 10 \cos(300t + 45^\circ) + 500 \cos(300t - 60^\circ)$$

$$y = 10 \angle 45^\circ + 500 \angle -60^\circ \rightarrow \text{Phasor form.}$$

$$y = 483.85 \angle -48.48^\circ$$

$$y = 483.85 \cos[300t - 48.48^\circ]$$

$$b) \quad y = 250 \cos(377t + 30^\circ) - 150 \sin(377t + 140^\circ)$$

$$= 250 \cos(377t + 30^\circ) - 150 \cos[377t + 140^\circ - 90^\circ]$$

$$= 250 \angle 30^\circ - 150 \angle 50^\circ$$

$$= 120.5 \angle 4.804^\circ$$

$$= 120.5 \cos[377t + 4.804^\circ]$$

$$c) \quad y = 60 \cos(100t + 60^\circ) - 120 \sin(100t - 125^\circ) + 100 \cos(100t + 90^\circ)$$

$$= 60 \cos(100t + 60^\circ) - 120 \cos[100t - 125^\circ - 90^\circ]$$

$$+ 100 \cos(100t + 90^\circ)$$

$$= 60 \angle 60^\circ - 120 \angle -215^\circ + 100 \angle 90^\circ$$

$$= 152.87 \angle 32.98^\circ$$

$$= 152.87 \cos(100t + 32.94^\circ)$$

$$d) \quad y = 100 \cos(\omega t + 40^\circ) + 100 \cos(\omega t + 160^\circ) + 100 \cos(\omega t - 80^\circ)$$


$$= 100 \angle 40^\circ + 100 \angle 160^\circ + 100 \angle -80^\circ$$

$$= 0 \angle 0^\circ$$

$$y = 0 \cos(\omega t + 0^\circ)$$

Q.5

Given

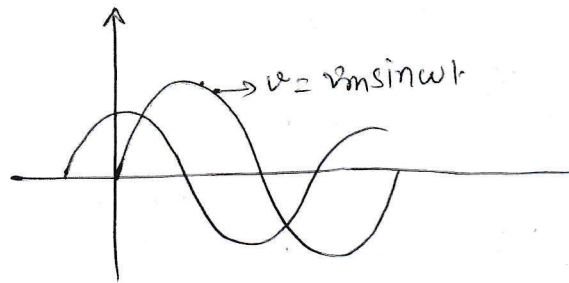

$$v = 2.5 \sin \omega t \text{ mV} \quad f = 40 \text{ kHz} \quad \omega = 80\pi \text{ rad/sec.}$$

$$i_m = 125.67 \mu\text{A}$$

$$i = \frac{cdv}{dt}$$

$$i = c \frac{d}{dt} 2.5 \sin \omega t$$

$$i = c \cdot 2.5 \cdot \omega \cos \omega t$$

$$i = 200\pi \cdot c \cos 80\pi \times 10^3 t = 200\pi \cdot c \sin (80000\pi t + 90^\circ)$$

1) frequency of current  $\omega = 80\pi \text{ K rad/sec.}$  — (1)

2) Phase angle  $\phi = 90^\circ$  leading.

3) Capacitive Reactance  $X_c = \frac{v}{I} = \frac{2.5 \times 10^{-3}}{125.67 \times 10^{-6}} = 19.89 \approx 20 \Omega.$

4) Capacitor  $C = \frac{1}{X_c \times \omega} = \frac{1}{20 \times 80\pi \times 10^3}$

$$\approx 0.200 \mu\text{F}$$

OR. compare eq<sup>n</sup> (1) with  $i_m$

$$125.67 = 200\pi \times 10^3 \times C$$


$$\boxed{C = 0.200 \mu\text{F}}$$

5) Impedence of capacitor

$$Z = -jX_c$$

$$= -j20 \Omega$$

Q.6. 1) frequency domain equivalent ckt-

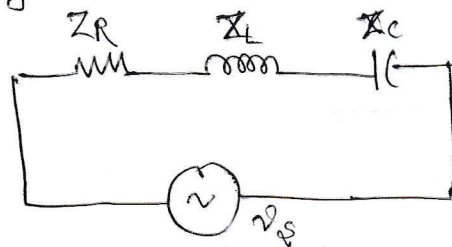

Here  $\omega = 8000$


$$Z_R = 400 \Omega$$

$$Z_L = j\omega L = j \times 8000 \times 87.5 \times 10^{-3}$$

$$= 700j$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \times 8000 \times 312.5 \times 10^{-9}}$$

$$= -400j$$

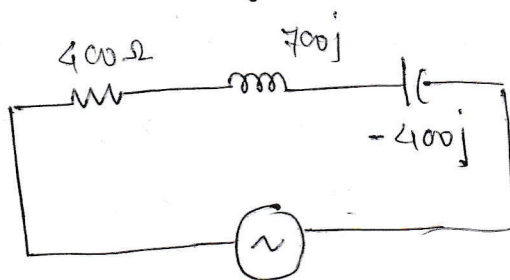

$$v_s = 500 \cos(8000t + 60^\circ)$$

2) Phasor current

$$\tilde{i} = \frac{500 \angle 60^\circ}{400 + j700 - 400j}$$


$$\tilde{i} = 1 \angle 23.13^\circ \text{ A.} \quad \underline{\underline{\text{Ans.}}}$$

3)

$$i = \cos(8000t + 23.13^\circ) \text{ A.}$$



Q7

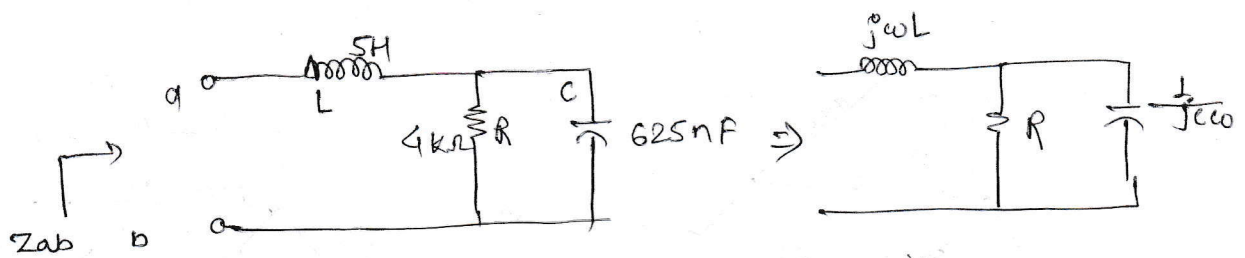

1. frequency at which  $Z_{ab}$  is purely resistive.

$$\begin{aligned}
 Z_{ab} &= j\omega L + R \parallel \frac{1}{j\omega C} \\
 &= j\omega L + \frac{R \times \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = j\omega L + \frac{R}{j\omega RC + 1} \times \frac{1-j\omega R}{1-j\omega R} \\
 &= j\omega L + \frac{R - j\omega CR^2}{1 + \omega^2 R^2 C^2}
 \end{aligned}$$

Compare Imag part and equal zero.  $\left[ \begin{array}{l} Z_{ab} \text{ will be Real if} \\ \text{Imag part will be zero} \end{array} \right]$

$$0 = j\omega L - \frac{j\omega CR^2}{1 + \omega^2 R^2 C^2}$$

$$L = \frac{CR^2}{1 + \omega^2 R^2 C^2}$$

$$1 + \omega^2 R^2 C^2 = \frac{CR^2}{L}$$

$$\omega^2 = \frac{CR^2}{L} - 1 = \frac{(625 \times 10^{-9}) \times (4000)^2}{5} - 1$$

$$= 201$$

$$\omega^2 = 160000$$






$$\boxed{\omega = 400} \text{ rad/sec.}$$

$$\begin{aligned}
 2) \quad Z_{ab} &= j\omega L + \left( R \parallel \frac{1}{j\omega C} \right) \\
 &= j400 \times 5 + \left[ 4000 \parallel \frac{1}{j \times 400 \times 625 \times 10^{-9}} \right] \\
 &= 2000j + 2000 - 2000j
 \end{aligned}$$

$$Z_{ab} = 2000 \Omega$$

$$\boxed{Z_{ab} = 2k \Omega}$$

Q.8.

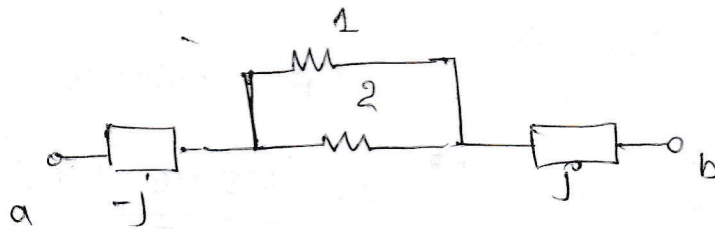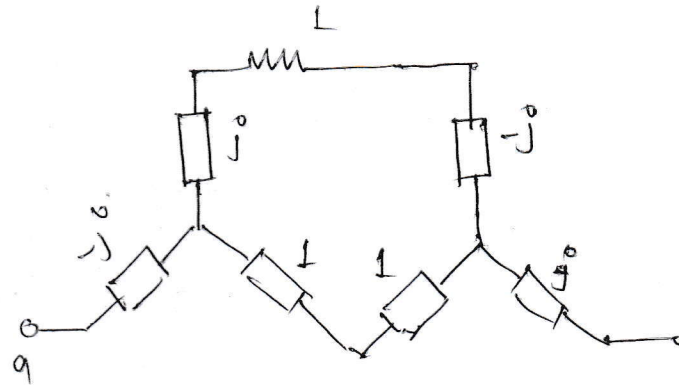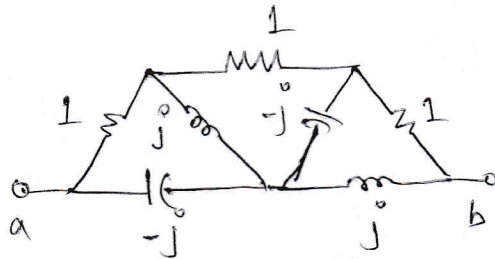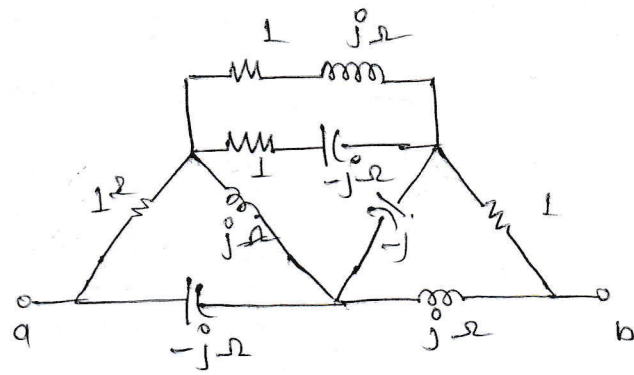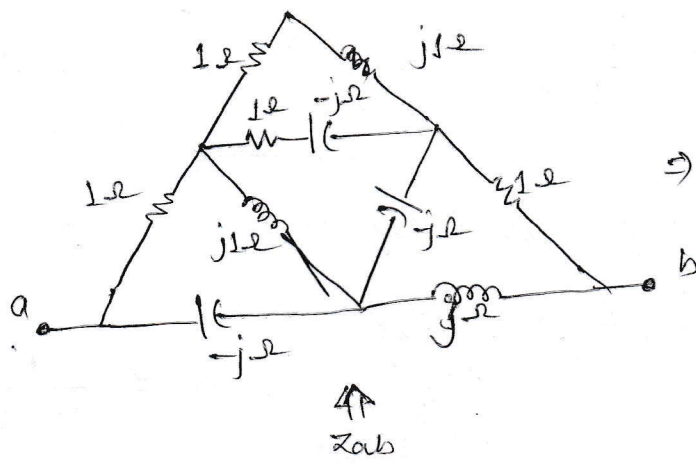


$$Z_{ab} = -j + (1 \parallel 2) + j$$




$$\boxed{Z_{ab} = \frac{2}{3} \Omega}$$



Q.9.

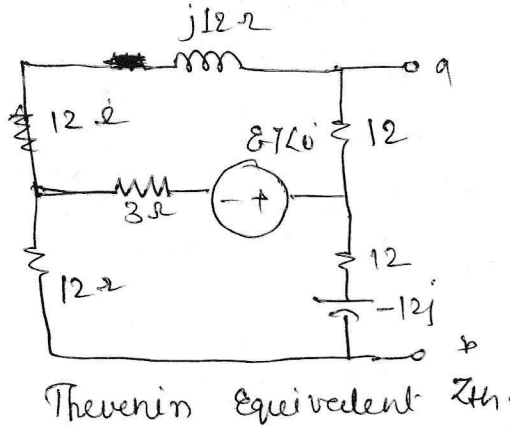


$\Rightarrow$

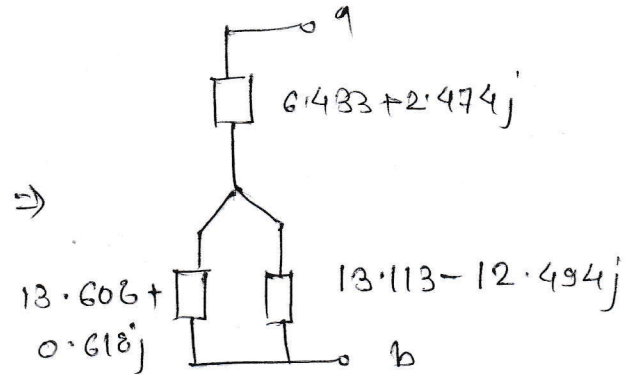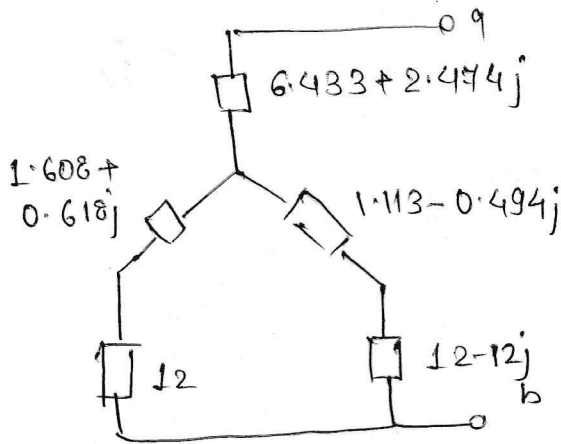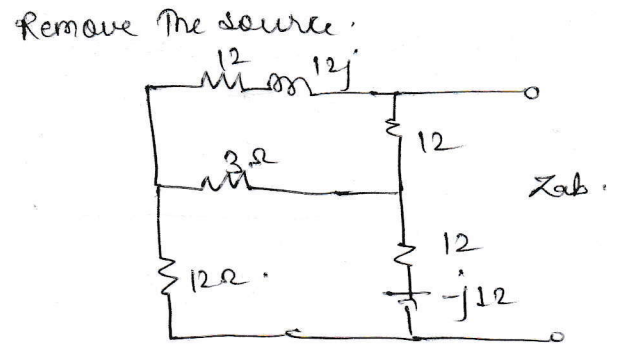

$$Z_{th} = 14.5 - 2.91 \times 10^{-4}j$$
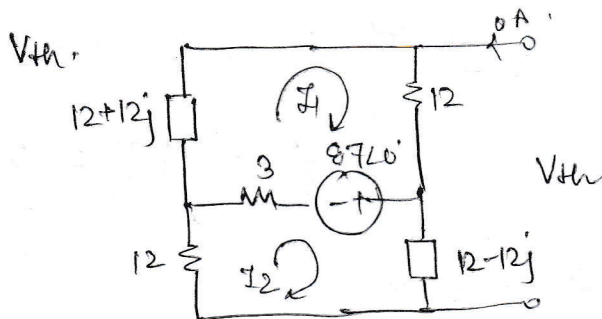
$$Z_{th} = 14.5 \angle -1.15 \times 10^{-3} \text{ } \Omega$$



$$(12 + 12j)I_1 + 12I_1 + 87 + 3(I_1 - I_2) = 0$$

$$(27 + 12j)I_1 - 3I_2 = -87 \quad (1)$$

$$(27 - 12j)I_2 - 3I_1 = 87 \quad (2)$$

$$I_1 = \frac{3I_2 + 87}{27 + 12j}$$

Put value of  $I_1$  on eq<sup>n</sup>(2)

$$(27 - 12j)I_2 + \left( \frac{3I_2 + 87}{27 + 12j} \right) \times (-3I_2) = 87$$


$$I_2 = 2.618 + 1.208j \text{ A}$$

$$I_1 = -2.39 + 1.2j \text{ A}$$



$$V_{th} = 12I_1 + I_2(12 - 12j)$$

$$V_{th} = 17.112 - 2.52j$$
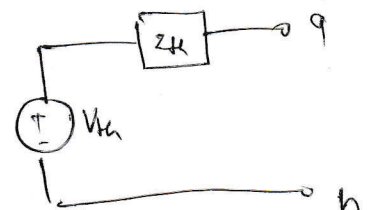
$$V_{th} = 17.3 \angle -8.38^\circ \text{ V}$$



Q.10.

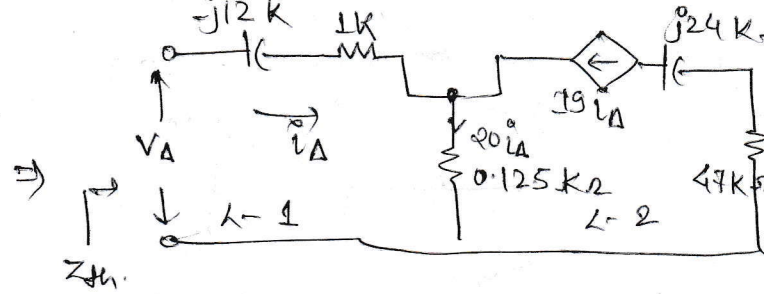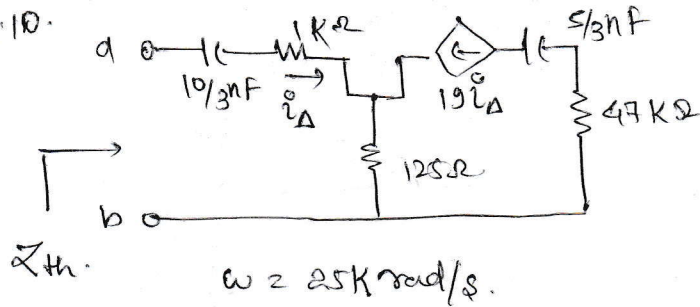

for thevenin equivalent  $Z_{th} = \frac{V_A}{I_A}$

Apply KVL at loop 1

$$V_A = (1 - j12) I_A + 0.125 \times 20 I_A$$


$$Z = \frac{1}{1 - j12}$$

$$V_A = (3.5 - 12j) I_A$$

$$\frac{V_A}{I_A} = 3.5 - 12j \text{ K}\Omega$$

$$\boxed{Z_{th} = 3.5 - 12j \text{ K}\Omega}$$

Q.11.

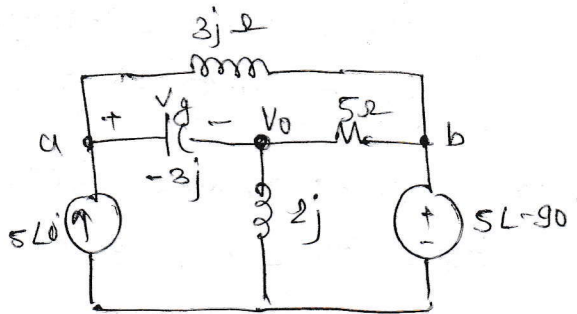

Apply KCL  $\rightarrow$  at node  $V_0$ .

$$\frac{V_0 - V_a}{-3j} + \frac{V_0 - 5L-90}{5} + \frac{V_0}{2j} = 0$$

$$V_0 \left[ \frac{1}{5} - \frac{1}{6}j \right] = \frac{V_a}{-3j} + 1L \quad \text{--- (1)}$$

KCL at node a

$$\frac{V_a - V_0}{-3j} + \frac{V_a - 5L-90}{3j} = 5$$

$$\frac{V_0}{3j} = 5 + \frac{5L-90}{3j}$$

$$\boxed{V_0 = 10j} \quad \text{--- (2)}$$

put value of  $V_0$  on eq<sup>n</sup> (1) ~

$$V_a = 9 - 5j^0$$


$$\text{So } V_g = V_a - V_0$$

$$= 9 - 5j - 10j$$


$$= 9 - 15j$$

$$\boxed{V_g = 17.5L - 89} \text{ V.}$$

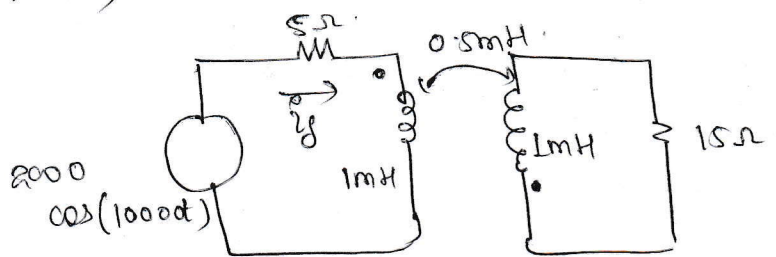Q.12. 1) Steady state expression for current  $i_g$  &  $i_L$ .



$$\omega = 10000 \text{ rad/sec.}$$

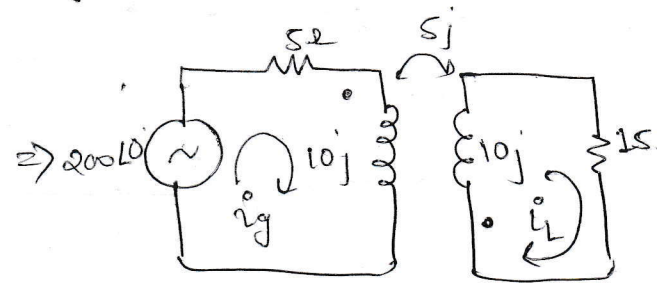

Apply KVL at both loop.

$$2000 = (5 + j10) i_g + j5 i_L \quad (1)$$

$$0 = (15 + j10) i_L + j5 i_g \quad (2)$$

$$i_L = \frac{j5 i_g}{15 + j10} \quad (3)$$

By solving eq<sup>n</sup> (1) & (2) we get.

$$i_g = 5.88 - 16.47j = 17.5 \angle -70.34^\circ$$

$$i_g = 17.5 \cos(10000t - 70.34^\circ) \text{ A.}$$

$$i_L = 4.70 - 1.176j$$

$$i_L = 4.85 \angle -14^\circ$$

$$i_L = 4.85 \cos(10000t - 14^\circ)$$

2) Coefficient of coupling.

$$k = \frac{M}{\sqrt{L_1 L_2}} = \frac{0.5}{\sqrt{1 \times 1}} \Rightarrow \boxed{k = 0.5}$$

3) Energy Stored in the magnetically coupled coil

at  $t = 50\pi \text{ ms}$ .

$$i_g = 17.50 \cos[10000 \times 50\pi \times 10^{-6} - 70.34] = 17.50 \cos(90 - 70.34) = 16.48 \text{ A.}$$

$$i_L = 4.85 \cos(90 - 14) = 4.733 \text{ A.}$$

Total Energy in coupled coil

$$W = \frac{1}{2} L_1 i_g^2 + \frac{1}{2} L_2 i_L^2 + M i_g i_L$$

$$\boxed{W = 146.15 \text{ mJ}}$$

at  $t = 100\pi$


$$i_g = 17.50 \cos(180 - 70.34) = -5.887 \text{ A.}$$

$$i_L = 4.85 \cos(180 - 14) = -4.7 \text{ A.}$$

Total Energy -

$$W = \frac{1}{2} L_1 i_g^2 + \frac{1}{2} L_2 i_L^2 + M i_g i_L \Rightarrow \boxed{W = 42.20 \text{ mJ}}$$

Q.13.

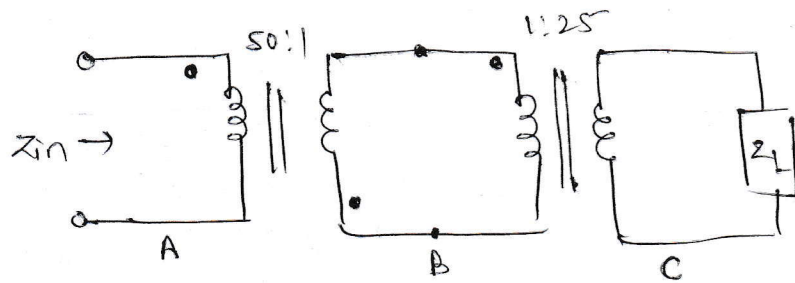

$$Z_L = 200 + j150 \Omega$$

$$n = \frac{N_2}{N_1}$$

$$Z_B = \frac{Z_L}{n^2} \quad \left[ Z_B = \left( \frac{N_1}{N_2} \right)^2 Z_L \right]$$

$$= \frac{200 + j150}{(25)^2}$$

$$Z_B = 0.32 + 0.24j$$

$$Z_A = \frac{Z_B}{n^2}$$

$$= \frac{0.32 + 0.24j}{(1/50)^2}$$

$$Z_A = 800 + 600j \Omega$$

$$\boxed{Z_{in} = 800 + 600j} \Omega$$