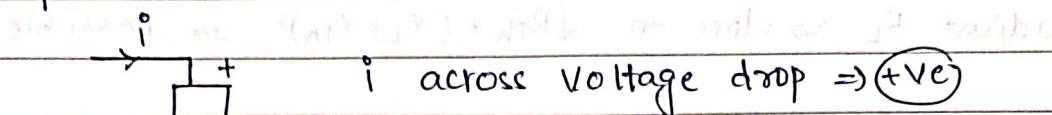


## SIGN CONVENTION

→ components in which  $i$  enters through +ve terminal ( $V$ )

$$P = +ve \quad \tau = +ve$$




~~For nodes after load~~  $i$  across Voltage rise  $\Rightarrow -ve$

$$P = -ve \quad \tau = -ve$$

Power source:  $P < 0 \rightarrow$  delivering

$P = +ve \rightarrow P > 0 \rightarrow$  absorbing


## Maximum Power Transfer Theorem

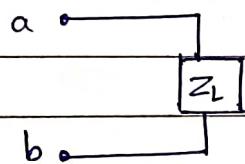

$Z_L$  that results in max. average power to the terminals a and b

$$Z_L = Z_{TH}^*$$

$$Z_{TH} = R_{TH} + j X_{TH}$$

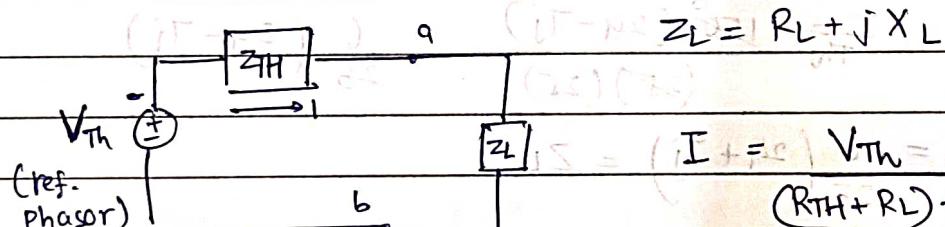

$$Z_L = R_L + j X_L$$

$$(I+e) V_{TH} = (R_{TH} + R_L + j(X_{TH} + X_L))$$

$$(P_{avg})_{\text{to load}} = |I|^2 R_L = \frac{|V_{TH}|^2 R_L}{(R_{TH} + R_L)^2 + (X_{TH} + X_L)^2}$$

~~2)  $V_{TH}, R_{TH}, X_{TH} \rightarrow \text{fixed}$~~

$$\frac{\partial P}{\partial X_L} = 0 \quad \frac{\partial P}{\partial R_L} = 0$$

$$X_L = -X_{TH} \quad R_L = \sqrt{R_{TH}^2 + (X_L + X_{TH})^2}$$

~~on combining both of them,~~

$$Z_L = Z_{TH}^*$$

~~When  $Z_L = Z_{TH}^*$ ,  $I = \frac{V_{TH}}{2R_L}$~~

$$(P_{max.})_{\text{load}} = \frac{|V_{TH}|^2 R_L}{4 R_L^2}$$


$$P_{max.} = \frac{|V_{TH}|^2}{4 R_L} = \frac{1}{8} \left( \frac{V_m^2}{R_L} \right)$$

$\Rightarrow$  adjust  $x_L$  as close to  $-x_{Th}$  as possible

$\downarrow$   
adjust  $R_L$  as close to  $\sqrt{R_{Th}^2 + (x_L + x_{Th})^2}$  as possible

$\Rightarrow$  If magnitude of  $Z_L$  can be varied but not its phase angle,

$$|Z_L| = |Z_{Th}|$$

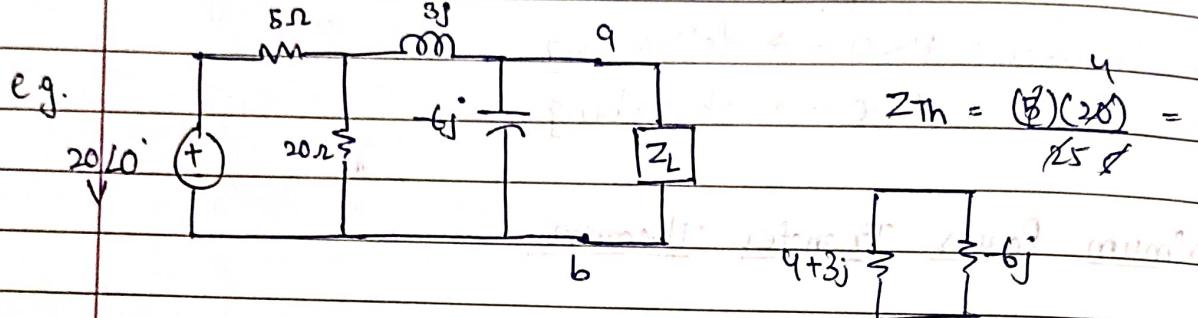

$$\frac{Z}{Z_{Th}} = \frac{4 - 3j}{25} + \frac{j}{6}$$


$$= \frac{24 - 18j + 25j}{150} \Rightarrow \frac{24 + 7j}{150} = \frac{1}{Z}$$

$$Z_{Th} = \frac{6}{(25)(25)} (24 - 7j) = \frac{6}{25} (24 - 7j)$$

$$Z_{Th}^* = \frac{6}{25} (24 + 7j) = Z_L$$

and, (max. power)  $_{avg.} = \frac{1}{4} \frac{|V_{Th}|^2}{R_L} = \frac{1}{4} \frac{(19.2)^2}{R_L} = 8W$

### DELTA - TO - WYE TRANSFORMATIONS

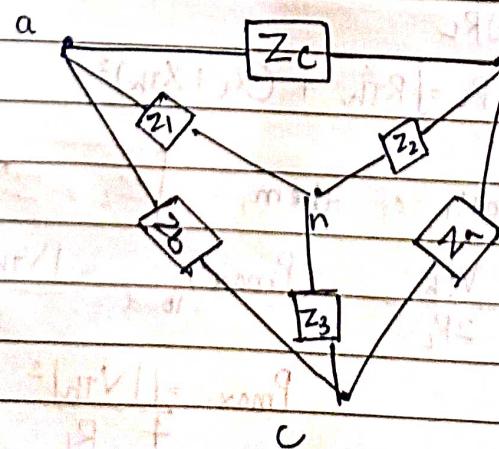

$$Z_1 = \frac{-Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c}$$


$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

$$Z_a = \underline{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1} \quad Z_C = \underline{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}$$

$$Z_b = \underline{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}$$

$$Z_1 + Z_2 + Z_3 = 12 + 24j + 18 - 24j = 12 + 24j = 12\angle 53^\circ$$


e.g.

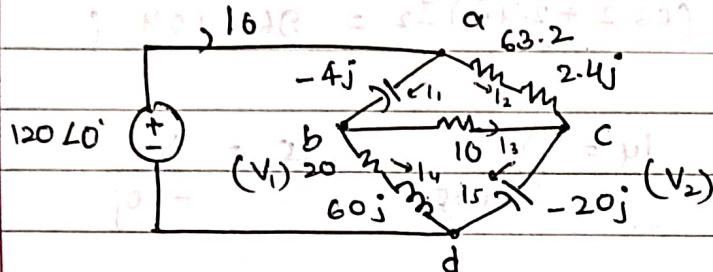

Find  $I_0, \dots, I_5, V_1, V_2$

$\Delta \leftrightarrow Y$  transformation
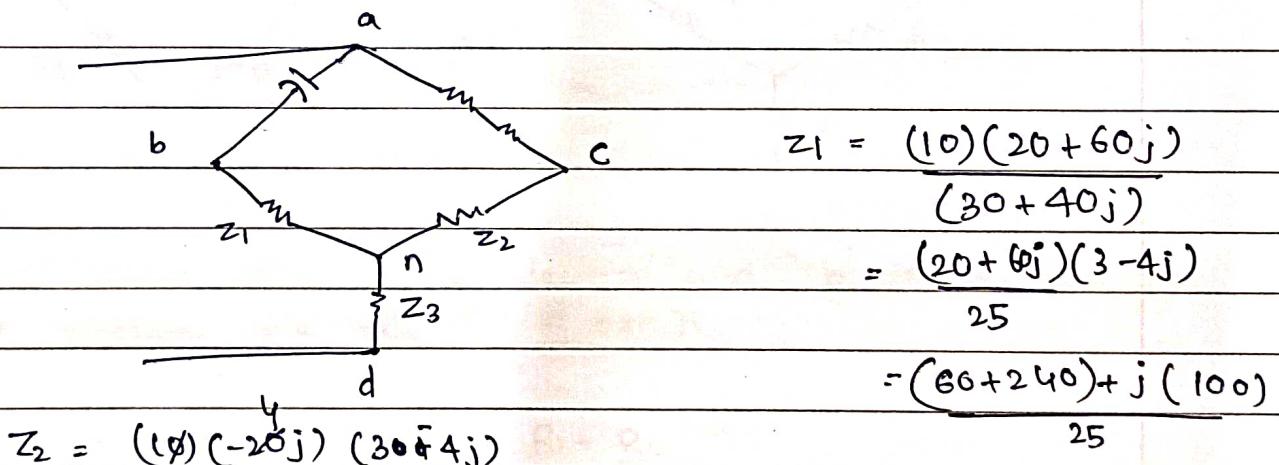
$$\begin{matrix} \swarrow & \searrow \\ \text{upper} & \text{lower} & (\text{check denominator}) \\ \times & \checkmark (30+40j) \end{matrix}$$



$$z_3 = \frac{(-2j)(20+60j)(3-4j)}{25}$$


$$= (-2j)(12+4j) = \boxed{8-24j}$$

$$Z_{abn} = -4j + 12 + 4j = 12\angle 0^\circ$$

$$Z_{acn} = 63.2 + 2.4j = 65.2\angle 3.2^\circ$$

$$I = \frac{120}{18-24j} = 120 \angle -53^\circ$$
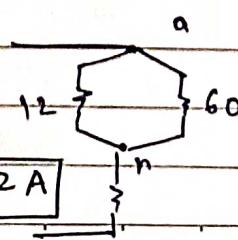
$$I = 4 \angle 53^\circ = \boxed{2.4 + j3.2 A}$$



$$Z_{an} = \frac{(12)(60)}{72} = 10\angle 0^\circ$$

$$Z_{net} = 18 - 24j$$

$$12I_1 + 12I_2 = \frac{5}{6} I_2 \quad I_1 + I_2 = I_0 \quad I_1 = \frac{5I_0}{6}$$

$$I_2 = \frac{I_0}{6}$$

$$V_1 = 120\angle 0^\circ - (4j)I_1 = \frac{328}{3} + 8j$$

$$V_2 = 120\angle 0^\circ - (53.2 + 2.4j)I_2 = 96 - 104j$$

$$I_3 = \frac{V_1 - V_2}{10} \quad I_4 = \frac{V_1}{20+60j} \quad I_5 = \frac{V_2}{-20j}$$

After rearranging & add

$$(50\theta + 5c)(0i) = 15 \quad (50\theta + 5c)N = 15$$

$$(50\theta + 5c)N = 15$$

$$(50\theta + 5c)(0i) = 15$$

$$(50\theta + 5c)(0i) = 15$$

$$(50\theta + 5c)(0i) = 15$$

$$[i\theta + c] = 15$$

$$(i\theta + c)(i\theta - c) = 225$$

$$[i\theta - c] = 225 - [i\theta + c](i\theta - c) = 225$$

$$(i\theta - c)(i\theta + c)(i\theta - c) = 225$$

$$[i\theta - c] = (i\theta + c)(i\theta - c) = 225$$

$$225 = i\theta^2 + 2ic\theta - c^2 \quad 225 = i\theta^2 + 2ic\theta + c^2 - 2c^2$$




$$V^2 = i\theta^2 + 2ic\theta - c^2$$

$$50i^2 = (50\theta)^2 = 2500\theta^2 \quad 2500\theta^2 = 225 - 2c^2 \quad 2500\theta^2 = 225 - 2c^2$$

$$50\theta^2 = 45 - 2c^2 \quad 50\theta^2 + 2c^2 = 45 \quad 50\theta^2 + 2c^2 = 45$$

## THREE PHASE CIRCUITS

### Delta-To-Wye Transformations

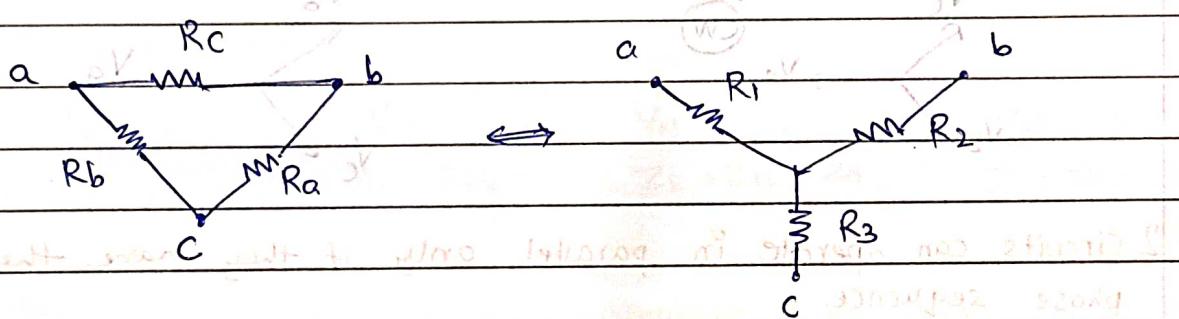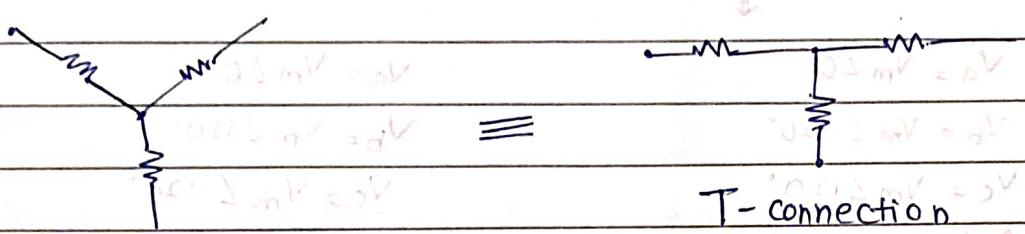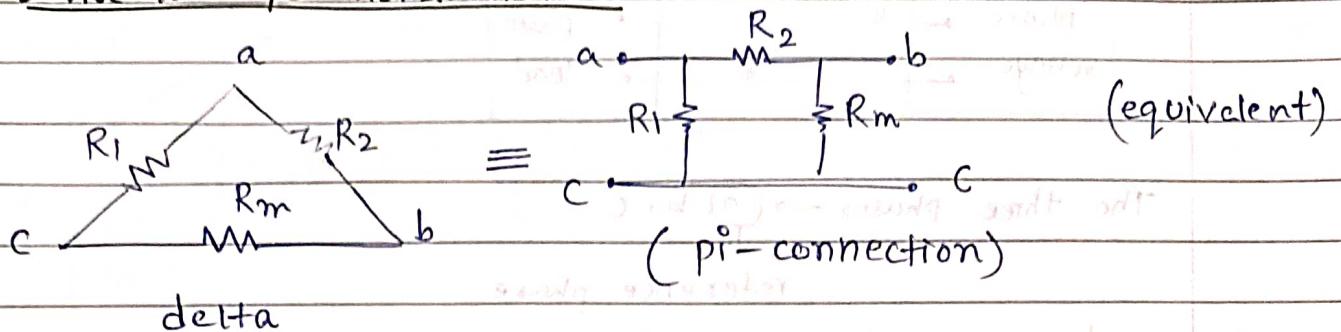

The resistance b/w terminals 'a' and 'b' must be the same whether we use  $\Delta$  or  $\text{Y}$  to be balanced.

$$R_{ab} = \frac{R_c(R_a + R_b)}{R_c + R_a + R_b} = R_1 + R_2$$

$$R_{bc} = \frac{R_a(R_b + R_c)}{R_a + R_b + R_c} = R_2 + R_3$$

$$R_{ac} = \frac{R_b(R_a + R_c)}{R_a + R_b + R_c} = R_1 + R_3$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} \quad R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

### Three phase line

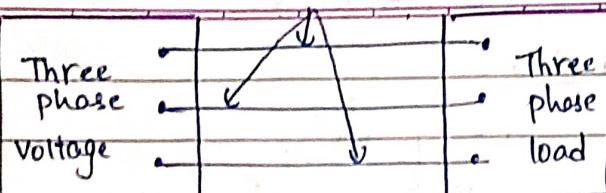

The three phases  $\rightarrow$  a, b, c

reference phase

b phase  $\rightarrow$  2 cases

$$V_a = V_m \angle 0^\circ$$

$$V_b = V_m \angle -120^\circ$$


$$V_c = V_m \angle 120^\circ$$

$$V_a = V_m \angle 0^\circ$$


$$V_b = V_m \angle 120^\circ$$

$$V_c = V_m \angle -120^\circ$$

(abc or POSITIVE phase sequence)

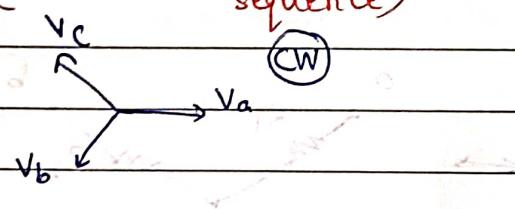


(acb or NEGATIVE phase sequence)

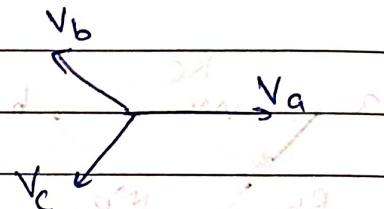


- # 2 circuits can operate in parallel only if they have the same phase sequence.

balanced set of voltages:  $V_a + V_b + V_c = 0$  (phase voltages)

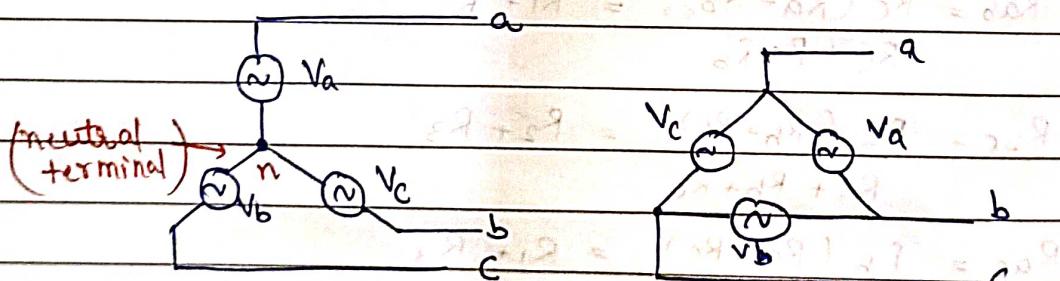also,  $V_a + V_b + V_c = 0$  (instantaneous)



### WYE-WYE CIRCUIT ANALYSIS

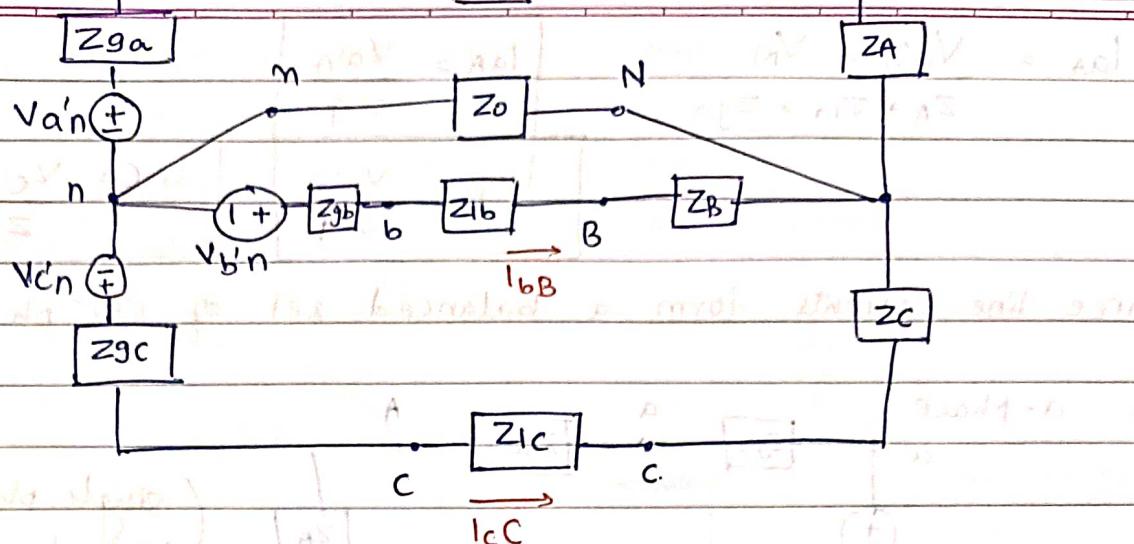

$Z_{ga}, Z_{gb}, Z_{gc} \rightarrow$  internal impedances

~~$Z_A, Z_B, Z_C \rightarrow$~~  line impedances

$Z_A, Z_B, Z_C \rightarrow$  load impedances

( $n \rightarrow$  reference)

$$\frac{V_N - V_a'n}{Z_0} + \frac{V_N - V_b'n}{Z_A + Z_{1a} + Z_{ga}} + \frac{V_N - V_c'n}{Z_B + Z_{1b} + Z_{gb}} + \frac{V_N - V_c'n}{Z_C + Z_{1c} + Z_{gc}} = 0$$

balanced  $3\phi \Rightarrow$  Voltage sources form a balanced set circuit

$\Rightarrow$  impedance of each phase of voltage is same

$\Rightarrow$  impedance of each line is same

$\Rightarrow$  impedance of each phase load is same.

So,

$$V_N \left( \frac{1}{Z_0} + \frac{3}{Z_\phi} \right) = \frac{V_a'n + V_b'n + V_c'n}{Z_\phi} \Rightarrow [V_N = 0] \quad (\text{balanced } 3\phi \text{ circuit})$$

$$Z_\phi = Z_A + Z_{1a} + Z_{ga}$$

$$= Z_B + Z_{1b} + Z_{gb} = 0.2\Omega + 0.2\Omega = 0.4\Omega$$

$$= Z_C + Z_{1c} + Z_{gc} = 0.2\Omega + 0.2\Omega = 0.4\Omega$$

$\Rightarrow$  There is NO P.D. diff. source neutral and line neutral, and so, current in neutral conductor ( $Z_0$ ) = 0

$\rightarrow$  perfect short circuit and  $V_N = 0$ .

$$I_{AA} = \frac{V_{A'n} - V_N}{Z_A + Z_{1a} + Z_{2a}}$$


$$I_{AA} = \frac{V_{A'n}}{Z\phi}$$

$$I_{BB} = \frac{V_{B'n}}{Z\phi}$$

$$I_{CC} = \frac{V_{C'n}}{Z\phi}$$


Three line currents form a balanced set of 3-phase.

For a-phase

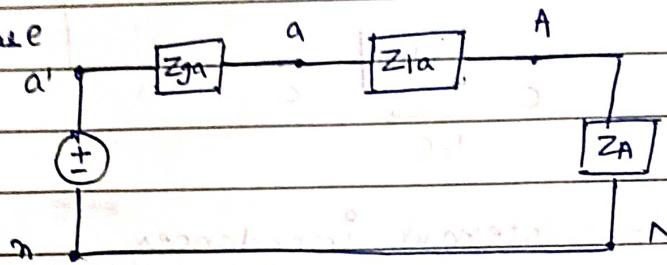

Here, current in neutral conductor is  $I_{AA}$ , not same as  $(I_0 = I_{AA} + I_{BB} + I_{CC})$

### LOAD TERMINALS

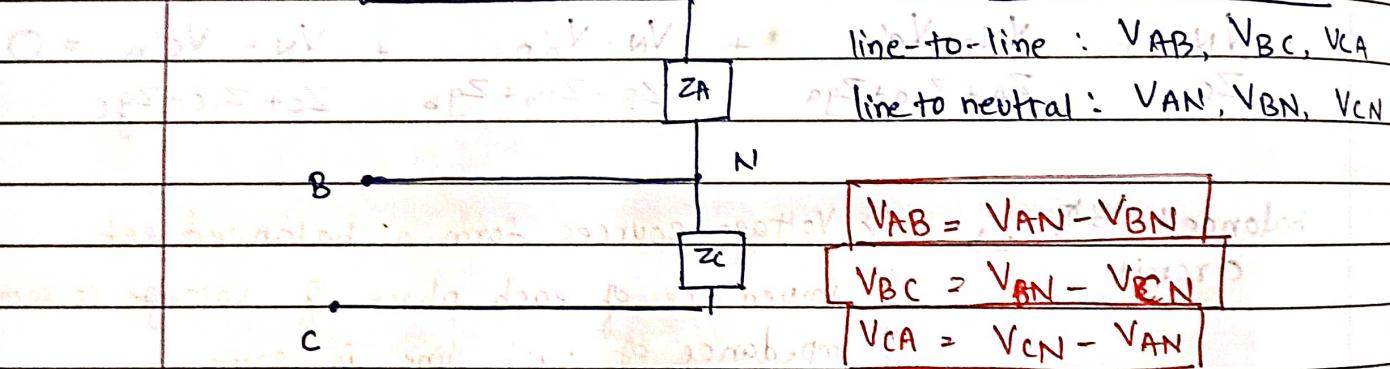

Assuming (using N)

$$V_{AN} = V_\phi L 0^\circ$$

$$V_{BN} = V_\phi L -120^\circ + 0^\circ V = (\underline{V_\phi L} \angle -120^\circ) V$$

$$V_{CN} = V_\phi L 120^\circ + 0^\circ V$$

-ve seq.  
↓  
(lag by 30°)

$$V_{AB} = V_\phi L 0^\circ - V_\phi L 120^\circ = \sqrt{3} V_\phi \angle 30^\circ$$

$$V_{BC} = V_\phi L -120^\circ - V_\phi L 120^\circ = \sqrt{3} V_\phi \angle -90^\circ$$

$$V_{CA} = V_\phi L 120^\circ - V_\phi L 0^\circ = \sqrt{3} V_\phi \angle 150^\circ$$

- 1) The magnitude of L-to-L voltages is  $\sqrt{3} \times (L\text{-to}\text{-}N)$  voltage.
- 2) L-to-L voltages form a set of balanced 3-Φ voltages.
- 3) L-to-L voltages lead L-to-N voltages by  $30^\circ$ .


(~~Phase-to-phase lead phase current by 30°~~)

Line voltage: Voltage across a pair of lines

Phase voltage: voltage across a single phase

Line current: current in a single line

Phase current: current in a single phase

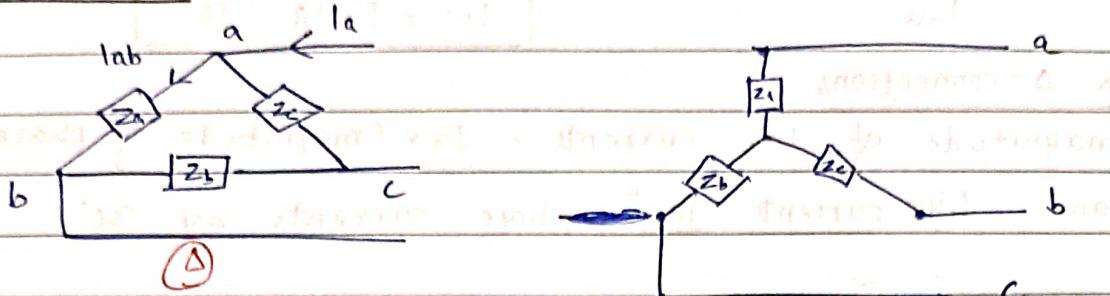

phase voltage  $\equiv$  line voltage

phase current  $\equiv$  line current

~~→~~ +ve sequence  $\rightarrow$  -ve sequence  
(abc) ~~→~~ (acb)

Interchange (b and c)

in all parameters

$\Rightarrow$  L-to-L voltages lag by  $30^\circ$  from L-to-N

### ~~WYE-DELTA CIRCUIT~~


use delta to wye transformation

(IMP.)

$$Z_\Delta = 3 Z_Y$$


$$Z_Y = \frac{Z_\Delta}{3}$$

after the  $\Delta-Y \Rightarrow$

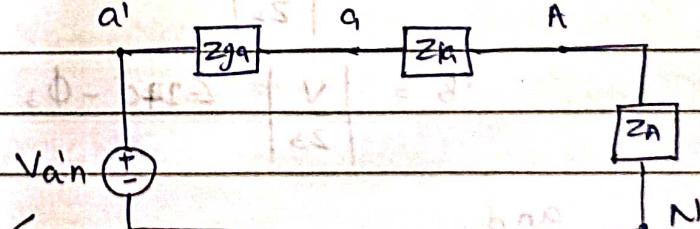

use it to find line currents,  $I_{AA}$ ,  $I_{BB}$ ,  $I_{CC}$

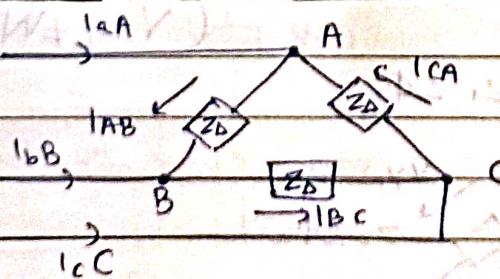Line currents v/c Phase currents in  $\Delta$ -config.




+ve phase sequence

$$I_{AB} = I_\phi \angle 0^\circ$$

$$I_{BC} = I_\phi \angle -120^\circ$$

$$I_{CA} = I_\phi \angle 120^\circ$$

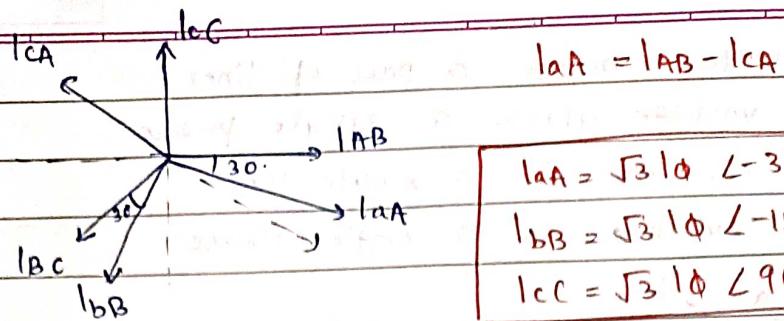


In  $\Delta$ -connections

- ⇒ i) magnitude of line currents =  $\sqrt{3} \times$  (magnitude of phase currents)  
and ii) Line currents "lag" phase currents by  $30^\circ$

### UNBALANCED CIRCUITS

A)

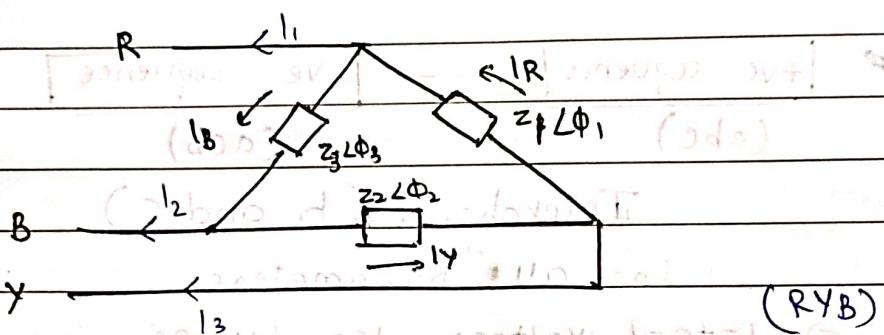

So,

$$I_R = \frac{V_{RY}}{Z_1 \angle \phi_1} = \left| \frac{V}{Z_1} \right| \angle -\phi_1$$


$$I_Y = \left| \frac{V}{Z_2} \right| \angle -120^\circ - \phi_2$$

$$I_B = \left| \frac{V}{Z_3} \right| \angle -240^\circ - \phi_3$$

and


$$I_L = I_R - I_B \quad (\text{phasor difference})$$

B) 4-wire star-connected load

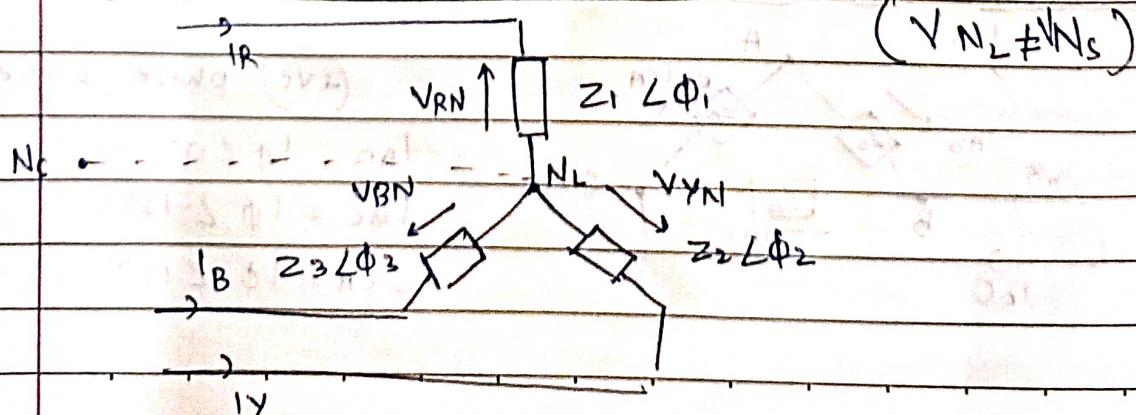


M1)  $\Delta$ -conversion  $\rightarrow$  line currents in the  $\Delta$  are same as in the  $\Delta$

M2) Millman's method

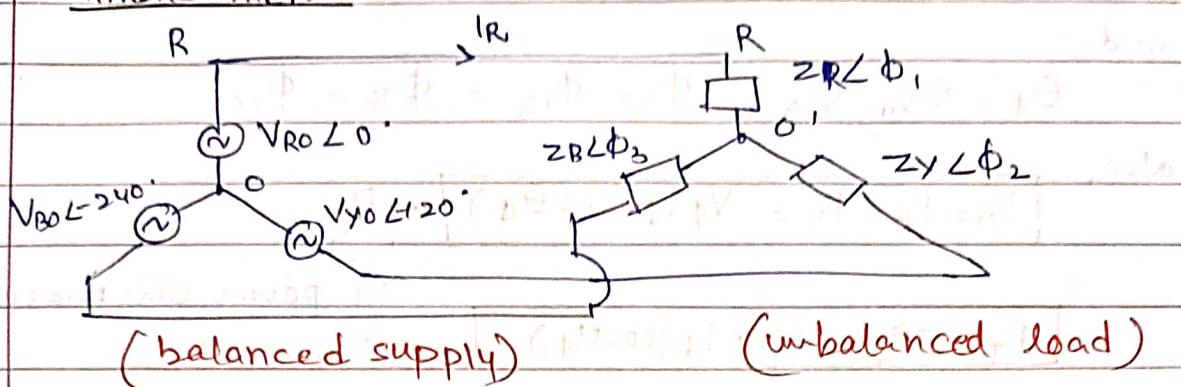

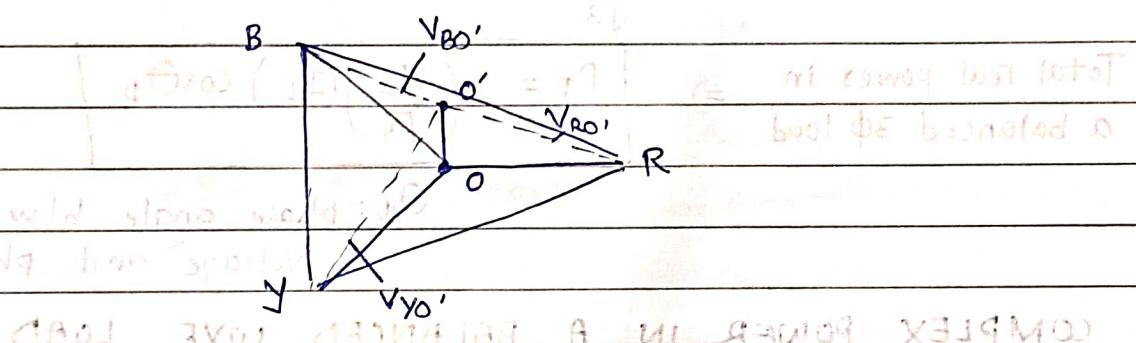supply and load have the same line voltages, equal in magnitude and displaced by  $120^\circ$



$$V_{O0'} = V_{R0} Y_R + V_{Y0} Y_Y + V_{B0} Y_B$$

$$Y_R + Y_Y + Y_B$$


and  $V_{R0} = V_{R0'} + V_{O0'}$

i.e.,  $V_{R0'} = V_{R0} - V_{O0'}$

### POWER CALCULATIONS
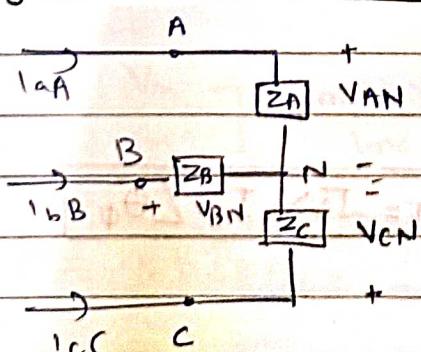
#### Average

$\Rightarrow$  Average Power in a Balanced Wye Load



$$P_A = |V_{AN}| |I_{AN}| \cos(\theta_{V_A} - \theta_{I_A})$$

$$P_B = |V_{BN}| |I_{BN}| \cos(\theta_{V_B} - \theta_{I_B})$$

$$P_C = |V_{CN}| |I_{CN}| \cos(\theta_{V_C} - \theta_{I_C})$$

as  $|L \rightarrow N|$  voltage is same

$$V_\phi = |V_{AN}| = |V_{BN}| = |V_{CN}|$$

$$I_\phi = |I_{aA}| = |I_{bB}| = |I_{cC}|$$

and

$$\theta_\phi = \theta_{VA} - \phi_{iA} = \phi_{VB} - \phi_{iB} = \phi_{VC} - \phi_{iC}$$

also,

$$P_A = P_B = P_C = V_\phi I_\phi (\cos \theta_\phi) = P_\phi$$

avg. power per phase

$$P_T = 3P_\phi = 3V_\phi I_\phi (\cos \theta_\phi)$$

definition  $V_L$  and  $I_L$  one line voltages and currents,

$$I_\phi = I_L \quad V_L = V_N = V_B$$

Total real power in  
a balanced 3 $\phi$  load  $\Rightarrow$

$$P_T = 3 \left( \frac{V_L}{\sqrt{3}} \right) (I_L) \cos \theta_\phi$$

$\theta_\phi$ : phase angle b/w phase voltage and phase current

$\Rightarrow$  COMPLEX POWER IN A BALANCED WYE LOAD

$$Q_\phi = V_\phi I_\phi \sin \theta_\phi$$

Total complex power  
in a balanced 3 $\phi$  load  $\Rightarrow$

$$Q_T = (\sqrt{3} V_L I_L) \sin \theta_\phi$$

For a balanced load, complex power,

$$S_\phi = V_{AN} I_{aA}^* = V_{BN} I_{bB}^* = V_{CN} I_{cC}^*$$

$$S_\phi = V_\phi I_\phi^*$$


$$S_\phi = P_\phi + j Q_\phi$$

$$S_T = 3 S_\phi$$

$$S_T = \sqrt{3} V_L I_L \angle \theta_\phi$$

## BALANCED DELTA LOAD

similar to Y-connected load

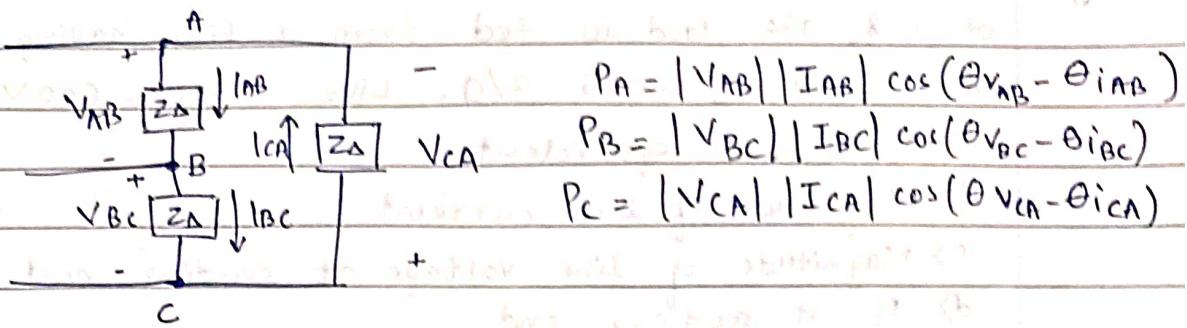

$$|V_{AB}| = |V_{BC}| = |V_{CA}| = V_\phi \quad \text{and} \quad |\phi| \quad \text{and} \quad \theta_\phi$$

$$P_A = P_B = P_C = P_\phi = V_\phi I_\phi \cos \theta_\phi$$

IMP: avg. power per phase =  $(\text{RMS phase voltage}) \times (\text{RMS phase current}) \times (\cos(\text{angle b/w phase V and I}))$

$$P_T = 3 V_\phi I_\phi \cos \theta_\phi$$

$$= 3 V_L \left( \frac{I_L}{\sqrt{3}} \right) \cos \theta_\phi$$

$$\boxed{P_T = \sqrt{3} V_L I_L \cos \theta_\phi}$$

and similarly,

$$Q_T = \sqrt{3} V_L I_L \sin \theta_\phi$$

$$S_T = \sqrt{3} V_L I_L \angle \theta_\phi$$

## INSTANTANEOUS POWER IN 3-PHASE CIRCUITS

V<sub>AN</sub> → inst. L-to-N voltage

$$\text{reference} = (100\angle 0^\circ + 0\angle 0^\circ) \text{ V} = (P.D.)$$

$$P_A = V_{AN} i_{AA} = V_m I_m \cos \omega t \cos(\omega t - \theta_\phi)$$

$$P_B = V_m I_m \cos(\omega t - 120^\circ) \cos(\omega t - 120^\circ - \theta_\phi)$$

$$P_C = V_m I_m \cos(\omega t + 120^\circ) \cos(\omega t + 120^\circ - \theta_\phi)$$


V<sub>m</sub> → max. amp. of phase voltage and  
I<sub>m</sub> → line current (or phase)

$$15\angle 0^\circ + 14\angle 0^\circ = (5 + 15)\angle 0^\circ = 20\angle 0^\circ$$

$$(200\angle 0^\circ + 200\angle 0^\circ) P_T = P_A + P_B + P_C = \boxed{200 \frac{V_m I_m (\cos \theta_\phi)}{2\pi f}}$$

Eg. A balanced 3φ load requires 480 kW at a lagging pf of 0.8. The load is fed from a line having impedance of  $0.005 + j 0.025 \Omega/\phi$ . Line voltage = 600 V

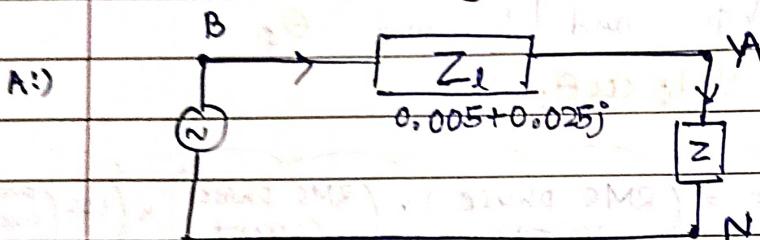- a) Single-phase equivalent
- b) Magnitude of line current
- c) Magnitude of line voltage at sending end
- d) Pf at sending end.



$$P_{load} = 480 \angle -37^\circ - 3\text{P}\phi$$

$$\text{P}\phi = 160 \left( \frac{4}{5} \angle 37^\circ \right)$$

$$P_{load} = 160 \text{ KW} \quad \text{at } 0.8 \text{ pf} \quad \frac{3}{4} = Q \quad Q = 120$$

$$P_{load} = 160 + 120j$$

$$V_{Line-N} = 600 \angle 0^\circ \quad (\text{assuming A is reference-node})$$

$$P = VI^*$$

$$(160 + 120j) \times 1000 = \frac{6000}{\sqrt{3}} \cdot (I^*)$$

$$I^* = \frac{\sqrt{3}}{600} (1600 + 1200j) = 577.35 \angle 37^\circ$$

$$I_L = 577.35 \angle -37^\circ \quad \text{--- (1)}$$

$$I_L Z = \sqrt{V_A N}$$

$$Z = \frac{\sqrt{V_A N}}{I_L} = \frac{600 \angle 0^\circ}{577.35 \angle -37^\circ}$$

$$V_B = I_L (Z_L + Z) = V_{AN} + I_L Z_L$$

$$= 600 \angle 0^\circ + (577.35 \angle -37^\circ) (0.005 + j 0.025)$$

$$V_B = 357.51 \angle 1.57^\circ$$

(50V with phase)

$$P_{\text{sending}} = V_B I_L^* = (357.51 \angle 1.5^\circ) (577.35 \angle 37^\circ) = 206.41 \angle 38.44^\circ$$

$$\text{pf} = \cos(37+1.5^\circ) = \cos(38.44^\circ)$$

$\text{pf}$  = angle b/w  $V_{\text{source}}$  and  $I_{\text{A.A.}} (I_L)$

$\theta = 38.44^\circ$


also,  $V_{\text{line}}$  at the sending end,

$$\sqrt{3} V_L I_L^* = 3 \times 206.41 \angle 38.44^\circ$$

$$|V_L| = 619.23 \text{ V}$$

$$\theta = 38.44^\circ$$

## TWO-WATTMETER METHOD

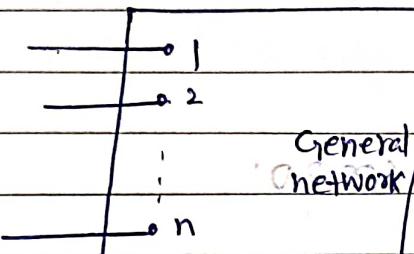

We need  $n-1$  currents

and  $n-1$  voltages as we have one terminal as a reference.

$$\text{so, } P_T = V_1 I_1 + V_2 I_2 + \dots + V_{n-1} I_{n-1}$$


(Assume  $V_n = 0$ )

→ so, for a 3 conductor circuit, we need only two wattmeters

→ 4-conductor circuit (incl. neutral)

- ③ if unbalanced
- ② if balanced

(no current in neutral line.)

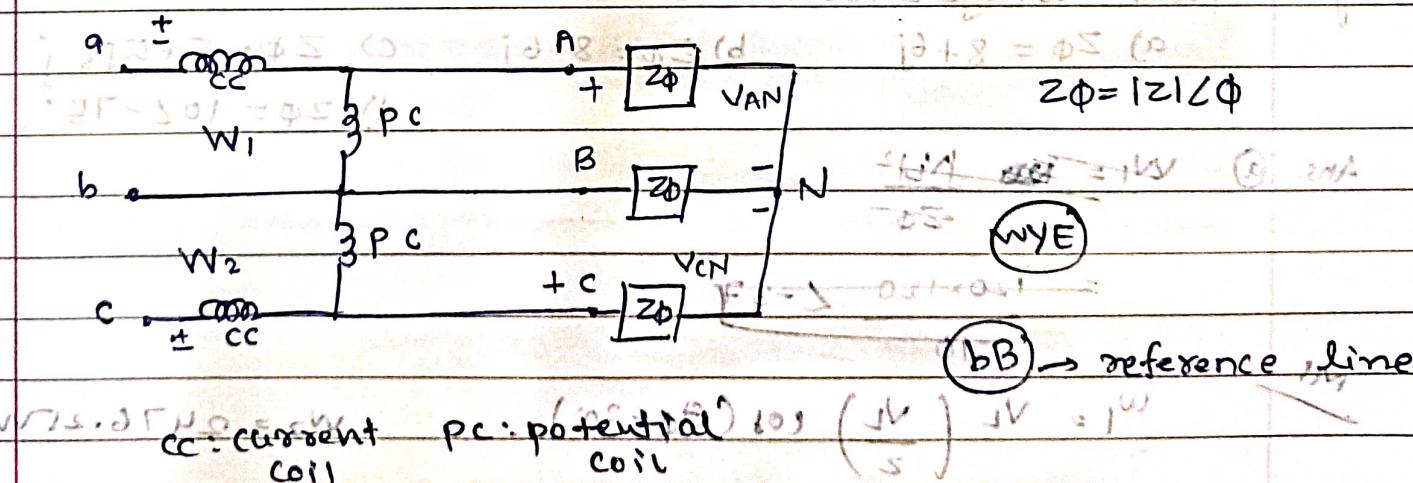

cc: current coil  
pc: potential coil

→  $I$  drawn by pc is negligible compared to line current measured by the cc.

→ the phase sequence

(angle b/w  $V_{AB}$ )and  $I_{AA} = I_A \angle 0^\circ$ 

$$W_1 \rightarrow |V_{AB}| |I_{AA}| \cos \theta_1$$

$$= V_L |I_L| \cos \theta_1 (\angle -30^\circ) \cos 0^\circ$$

$$W_2 \Rightarrow V_L |I_L| \cos \theta_2$$

For a +ve phase sequence,

θ: phase angle b/w phase voltage and phase current

$$V_{EF} \cdot P1\theta = UV1$$

$$\theta_1 = \theta + 30^\circ = \theta_\phi + 30^\circ$$

$$\theta_2 = \theta - 30^\circ = \theta_\phi - 30^\circ$$

$$W_1 = V_L |I_L| \cos(\theta_\phi + 30^\circ)$$

$$W_2 = V_L |I_L| \cos(\theta_\phi - 30^\circ)$$

$$P_T = 2V_L |I_L| \cos \theta_\phi \cos 30^\circ$$

$$P_T = \sqrt{3} V_L |I_L| \cos \theta_\phi$$

⇒ 1) if pf > 0.5 → both  $W_1, W_2$  read (+ve)2) if pf = 0.5 → one  $W$  reads 0° and other 180°3) if pf < 0.5 → one  $W$  reads negative

4) reversing phase sequence / interchanges reading of two wattmeters.

Observed in (S)

Observed in (E)

e.g. - phase voltage = 120V and

a)  $Z_\phi = 8 + j6$

b)  $Z_\phi = 8 - j6$

c)  $Z_\phi = 5 + 5j3$

$\phi = 67^\circ$

120V

d)  $Z_\phi = 10L - 75^\circ$

Ans. a)  $V_A = \sqrt{V_L^2 + Z_\phi^2}$ 

$$= \frac{120 \times 120}{Z_\phi}$$

$$= \frac{120 \times 120}{8 + j6}$$

$$= 14400 \angle -37^\circ$$

$$= 120 \angle -37^\circ$$

Ans. a)  $P = \frac{V_A^2}{Z_\phi}$ 

$$W_1 = V_L \left( \frac{V_A}{Z_\phi} \right) \cos(\theta_\phi + 30^\circ)$$

$$W_2 = 2476.25W$$

$$= \frac{(120\sqrt{3})120}{14400} \cos(36.87 + 30^\circ)$$

$$= 979.75W$$

P	T	W	T	M
AVUD			104° 00' S	
			2100	

2719780 3173671 MAGNETIC

M	T	W	T	F	S	S
Page No.:	YOUVA					
Date:						

M2  $\rightarrow$   $200 \text{ mV} \cdot 21 \text{ A} \approx 20 \text{ A}$   $\rightarrow$   $X_{\text{phase}} = 120 \text{ V}$  + 30 amperes  $\rightarrow$   $200 \text{ V} \cdot 30 \text{ A} = 6000 \text{ W}$

$$Z_0 = 8 + 6j \quad I_{\text{phase}} = 120$$

$$I_{\text{phase}} = \underline{120}$$

$$I_{pw} = 12 \angle -37^\circ$$

$$P_{\text{net}} = 3 \times (120) (12) (\angle 37^\circ)$$

$$= 4320 \angle 37^\circ$$

$$\text{Pr}_{\text{cal}} = 3456 \text{ W}$$

$$W_1 = V_L |L| \cos(\theta_\phi + 30^\circ)$$

$$W_2 = V_L I_L \cos(\theta_\phi - 30^\circ)$$

$$W_1 + W_2 = \sqrt{3} V_L I_L \cos \theta \phi$$

## (Two-wattmeter)

## method